


# EEL3701


## Menu

- State Machine Design
  - > Design example: Sequence Detector (using Moore Machine)
  - > Design example: Sequence Detector (using Mealy Machine)
  - > Implementation



University of Florida, EEL 3701 – File 17  
© Drs. Schwartz & Arroyo

1

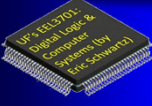

# EEL3701

## Classical Design

**[Example]** Design a Sequence Detector/Acceptor to accept  $X = 010^*1$  where  $0^* = \{ \lambda(\text{nil}), 0, 00, 000, 0000, \dots \}$


- Thus, Sequence  $\{011\}$ ,  $\{0101\}$ ,  $\{01001\}$ ,  $\{010001\}$  are acceptable, but  $\{0111\}$  is not. Z is the output; X and CLK are the inputs.

$X = 010001010 \dots$   
 $Z = 000001010 \dots$   
 $\text{CLK} = 123456789 \dots$


- **STEP 1: State Diagram** - This comes in two flavors:
  - (1) Moore Machine - Outputs depend **only** on present state
  - (2) Mealy Machine - Outputs depend on state **and** present inputs

University of Florida, EEL 3701 – File 17  
© Drs. Schwartz & Arroyo

2

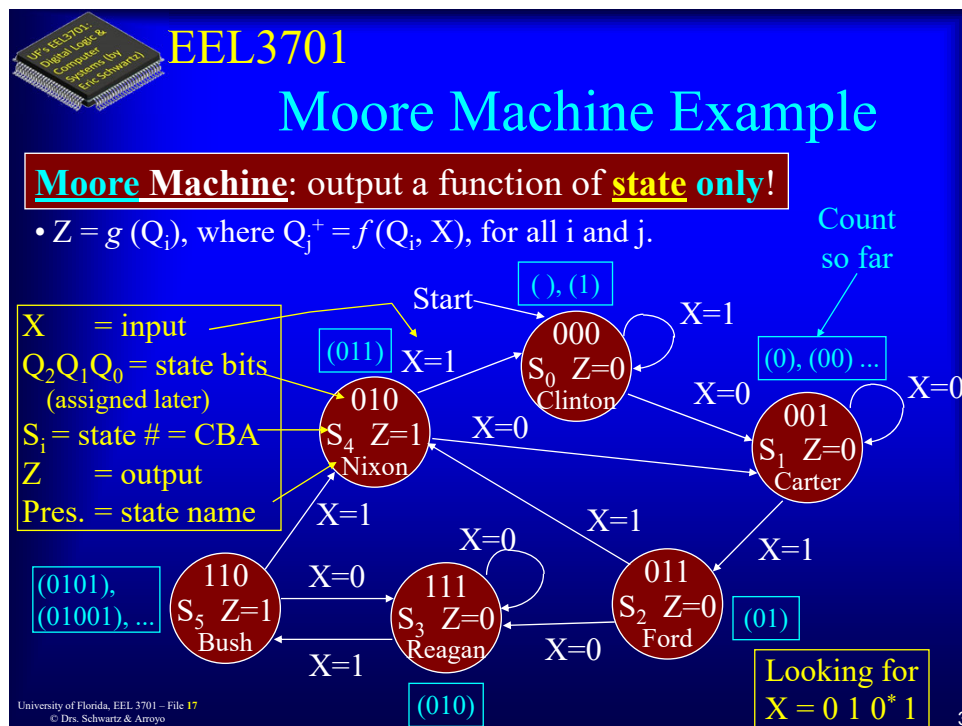

3

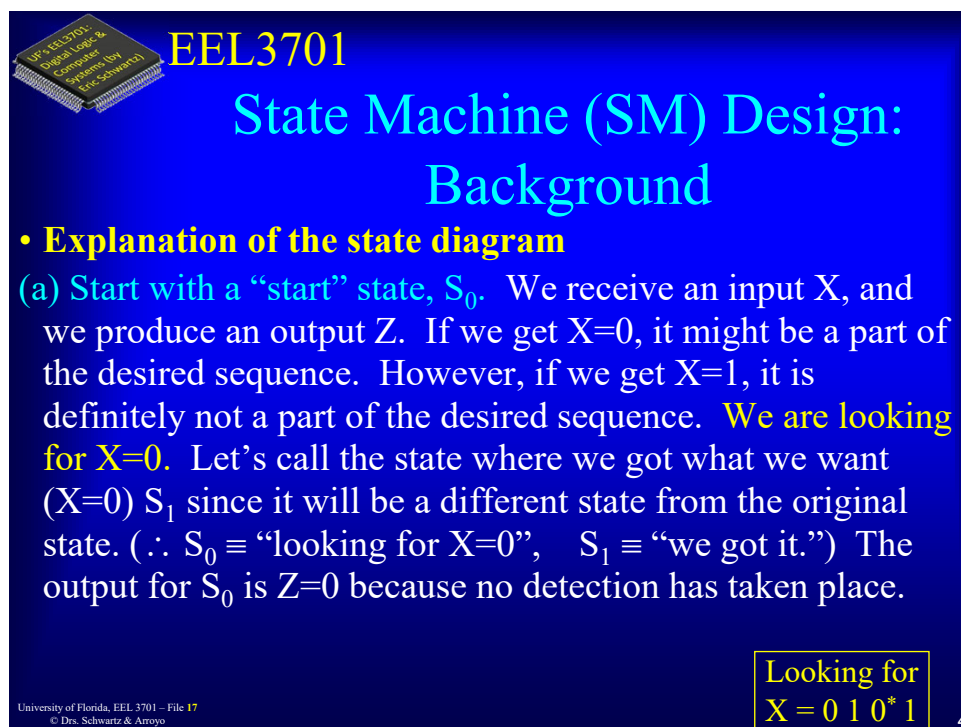

4



## EEL3701

# SM Design: Background

- **Explanation of the state diagram**


(b) Now in state  $S_1$ . We are looking for a 1. If we get it, we might be detecting the sequence. However, if we get a 0, we stay at the state where we are looking for a 1. Call the state where we got the 1 we are looking for  $S_2$ . The output for  $S_1$  is 0 since we've not detected all of the sequence yet.

(c) From  $S_2$ , if we get a 1, we succeed in detecting  $\{011\}$ . Call this state  $S_4$  (success!). If we get a 0, we might still succeed in detecting a part of  $\{010.....01\}$ . Call this state  $S_3$ . The output so far is still 0.

Looking for  
 $X = 0\ 1\ 0^* 1$

University of Florida, EEL 3701 – File 17  
© Drs. Schwartz & Arroyo

5

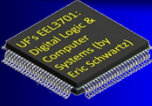

## EEL3701

# SM Design: Background


- **Explanation of the state diagram**

(d) From  $S_3$ , if we get a 0, we might still be working on  $\{010.....01\}$  so stay there. If we get a 1, we detected one of the good guys so go to  $S_5$  (success again!). Why not  $S_4$ ?  $S_4$  was for  $\{011\}$ , but now we have a sequence of intervening 0's followed by a 1. This is not  $\{011\}$ . **Treat them separately!** Output is 0 because no sequence has been detected.

Looking for  
 $X = 0\ 1\ 0^* 1$

University of Florida, EEL 3701 – File 17  
© Drs. Schwartz & Arroyo

6

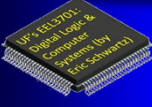

## EEL3701

# SM Design: Background

- **Explanation of the state diagram**


(e) From  $S_5$ , if we get a 0, we can go back to  $S_3$  because we would be detecting  $\{0101\}$  or  $\{010.....01\}$ . If we get a 1, there was no intervening zeros, we have  $\{011\}$  (success! go to  $S_4$ ). Output is 1 since we detected in  $S_5$  the pattern  $\{010.....01\}$ .

(f) From  $S_4$ , that is “after  $\{011\}$  is received,” another 1 sends us to “looking for the 1<sup>st</sup> zero,” that is  $S_0$ . A 0 sends us to “looking for a 1 after the 1st zero was detected,” that is,  $S_1$ . Output is 1 since we detected  $\{011\}$ .

Looking for  
 $X = 0\ 1\ 0^* 1$

University of Florida, EEL 3701 – File 17  
© Drs. Schwartz & Arroyo

7

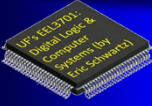

## EEL3701

# SM Design: Background


- We are  $\therefore$  finished with the state diagram since we have gone through all the possibilities. “Designing” is an *art with science*. It is not totally recipe-driven.
- **STEP 2:** Assign State Identifiers using binary patterns and/or names.

Since we have 6 states, we need 3 bits (3 FF's) to represent the  $[(2^2=4) < 6 \leq (2^3=8)]$  possibilities.

Looking for  
 $X = 0\ 1\ 0^* 1$

University of Florida, EEL 3701 – File 17  
© Drs. Schwartz & Arroyo

8

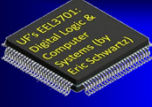

## EEL3701 SM Design: Background

- Make a state assignment table.

**Important  
State bits**


Present State	Names	$Q_2$	$Q_1$	$Q_0$	Next State(s)
$S_0$	Clinton	0	0	0	$(S_0) S_1$
$S_1$	Carter	0	0	1	$(S_1) S_2$
$S_2$	Ford	0	1	1	$S_3 S_4$
$S_3$	Reagan	1	1	1	$(S_3) S_5$
$S_4$	Nixon	0	1	0	$S_0 S_1$
$S_5$	Bush	1	1	0	$S_3 S_4$

*- Turns out that the assignment of bits has an effect on the complexity of the hardware realization. The details are beyond the scope of EEL 3701.*

Looking for  
 $X = 0\ 1\ 0^* 1$


University of Florida, EEL 3701 – File 17  
© Drs. Schwartz & Arroyo

9

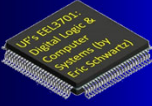

## EEL3701 SM Design: Background


- **Heuristic** -- Try to pick the state assignments so that only 1 bit changes from one state to the next state (the same used in Gray Code). This is not always possible, but we can often get close.
- You typically start by assigning  $S_0$  to an arbitrary pattern, say, 000 and pick from that point on.
- This is **NOT** required in 3701, but you will likely see it if you take EEL4712.

 **NOTE:** Using the Gray Code-like table, we do not use code 100 or 101 because we had only 6 states out of 8 patterns (000 ~ 111). These codes, 2 leftovers, cannot happen.  
 $\therefore$  They are “Don’t Cares” in the K-Maps.


University of Florida, EEL 3701 – File 17  
© Drs. Schwartz & Arroyo

10


10

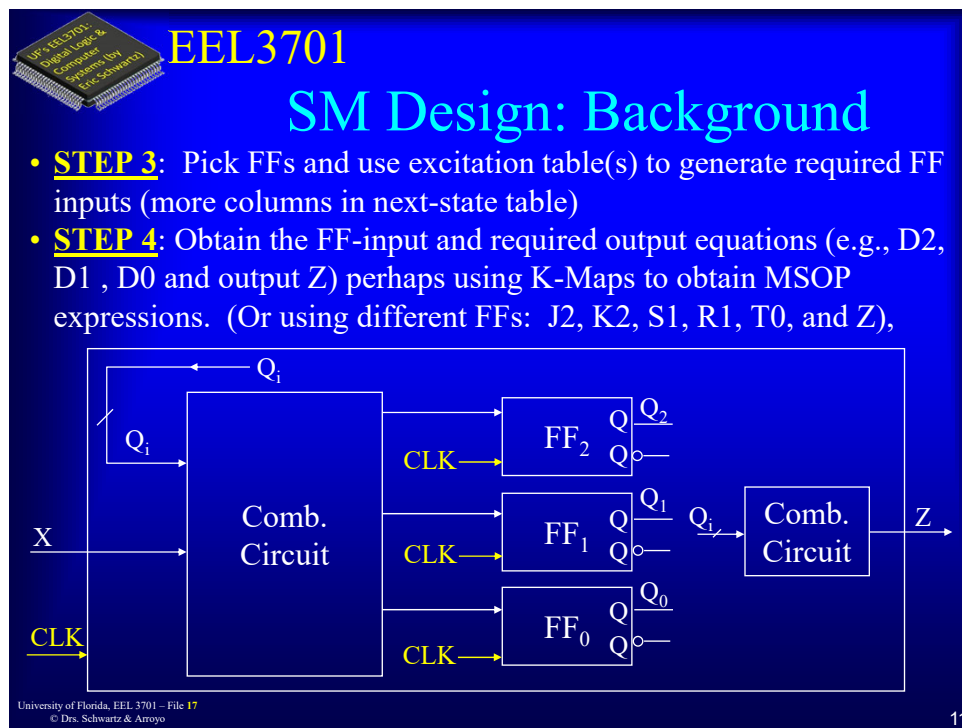


11

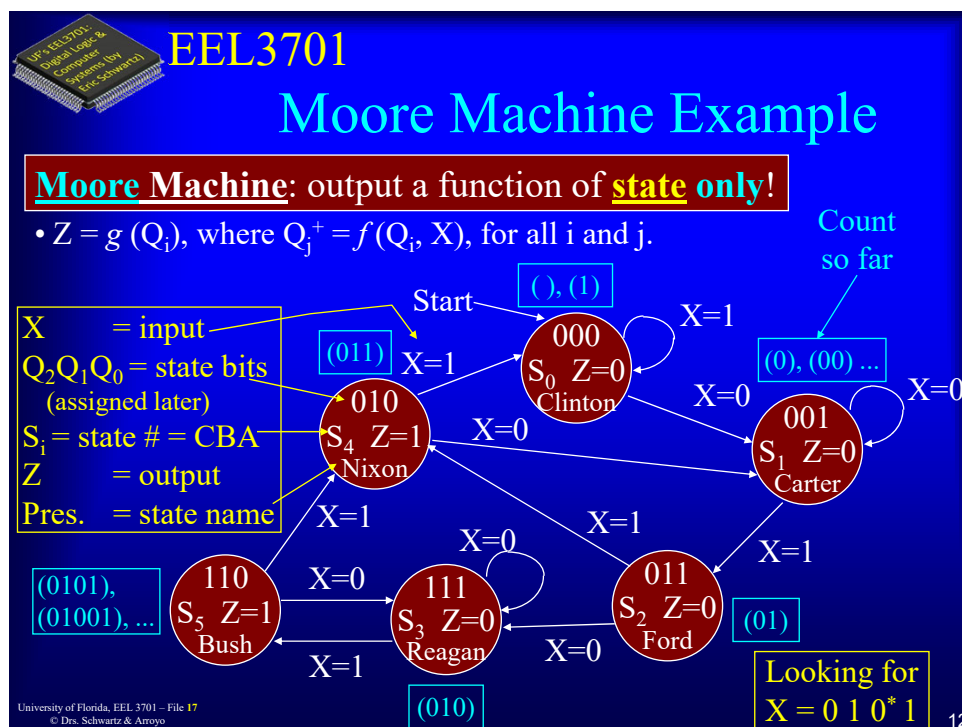


12

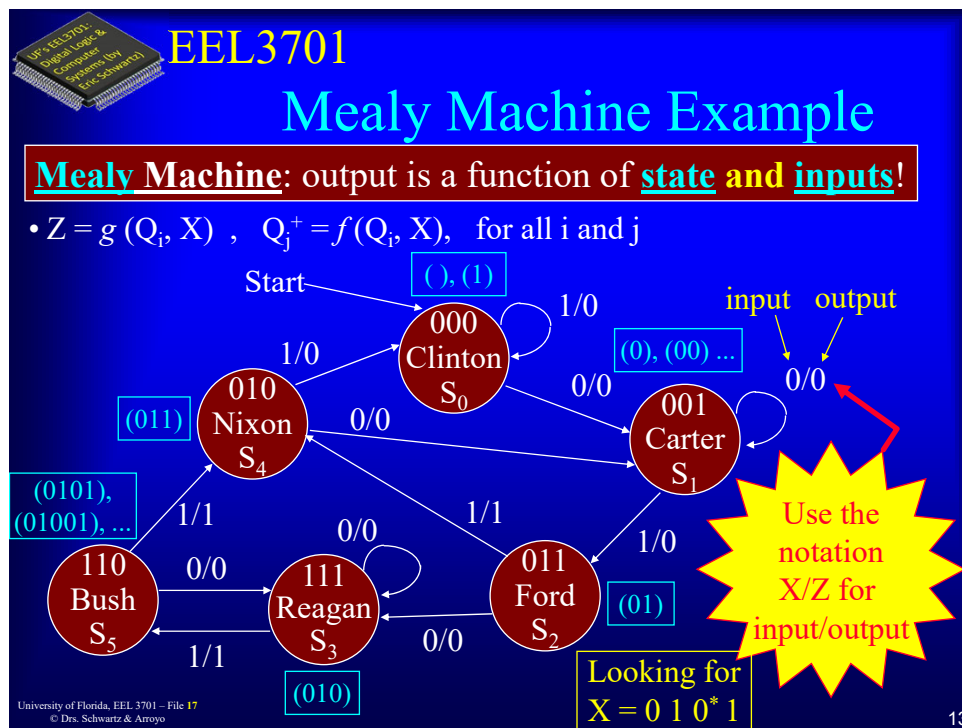


13

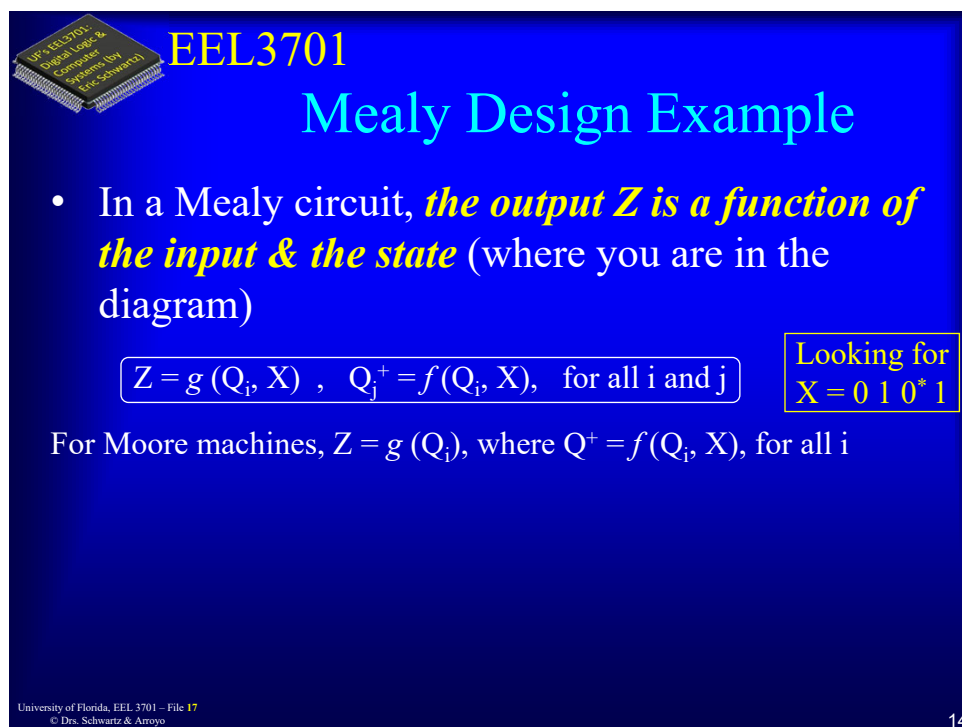

14

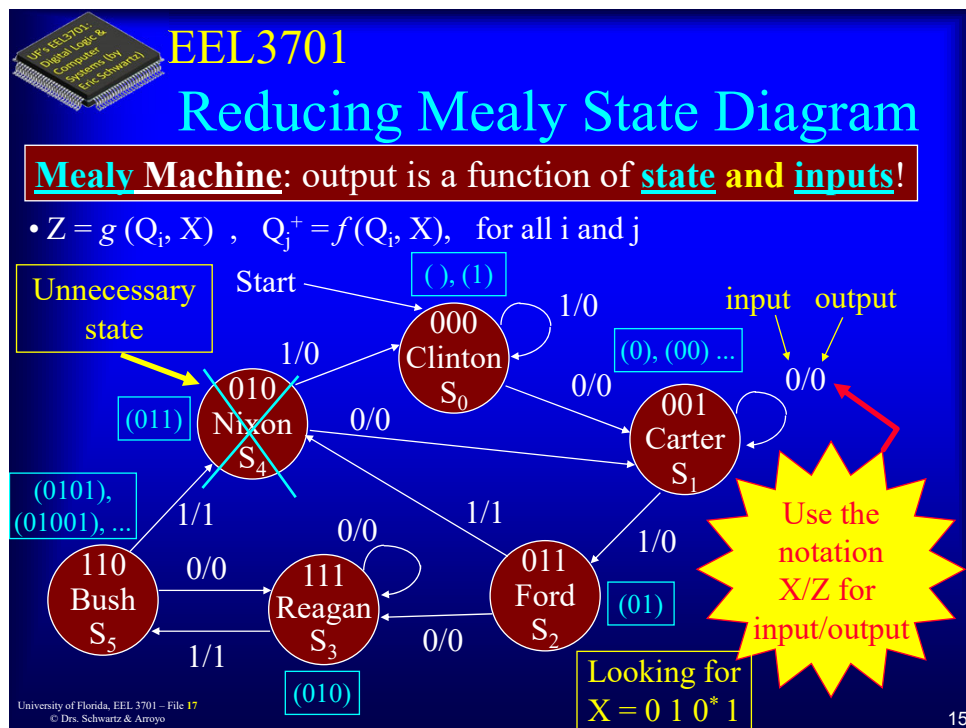


15

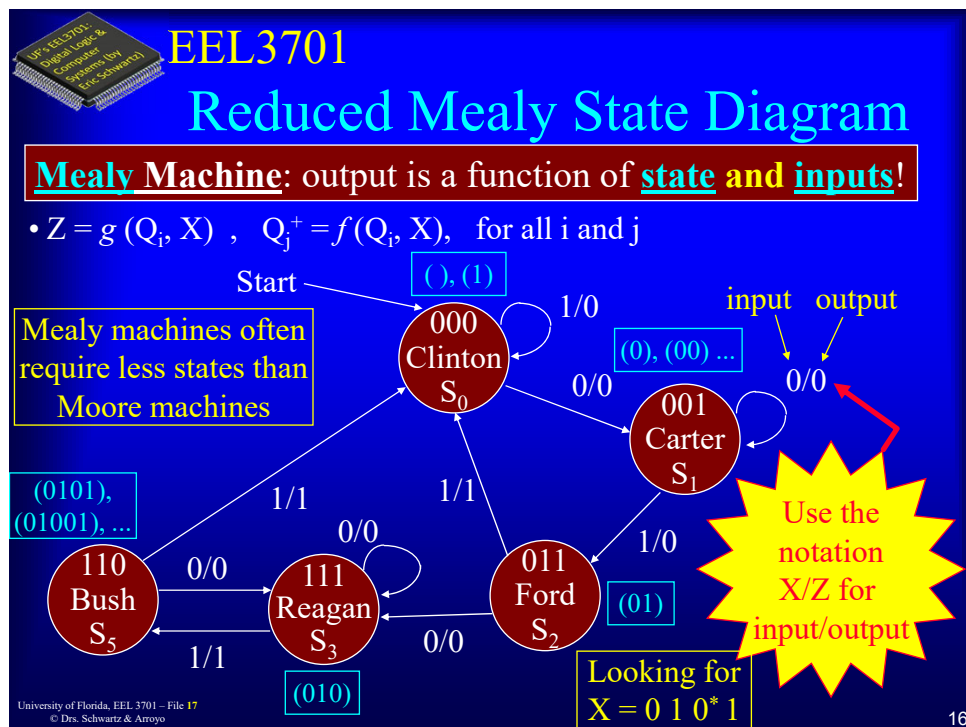


16



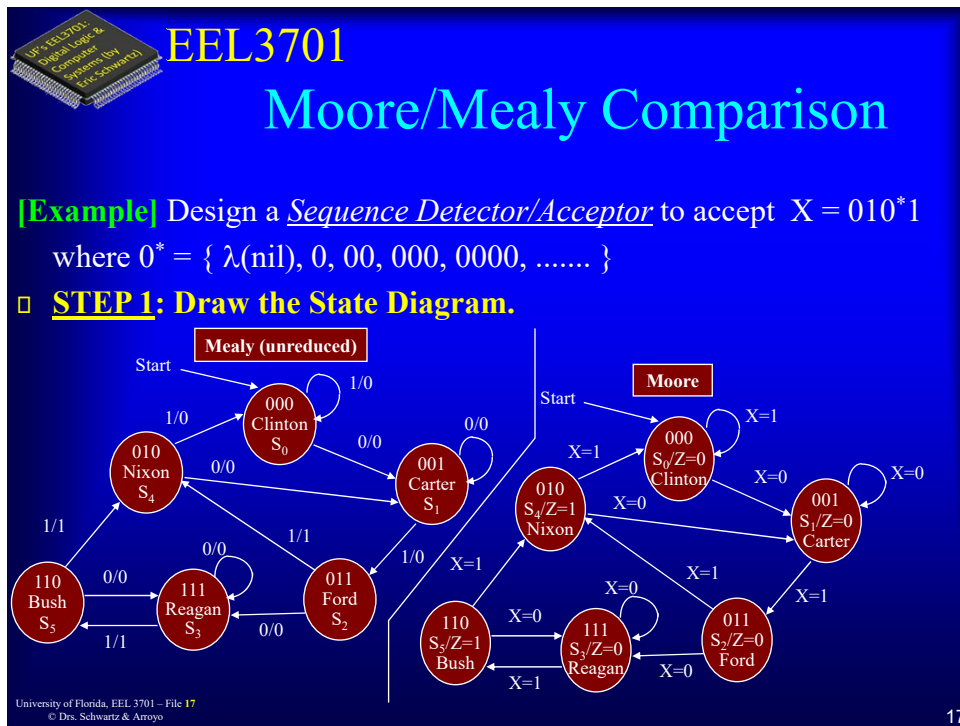

17

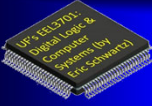 **EEL3701**

## Assigning State Bits

□ **STEP 2: Assign state patterns or Names**

- 6 states require 3-FF's to represent  $Q_2, Q_1, Q_0$ .

States	Names	Names	state bits		
			$Q_2$	$Q_1$	$Q_0$
$S_0$	Clinton	George	0	0	0
$S_1$	Carter	John	0	0	1
$S_2$	Ford	Thomas	0	1	1
$S_3$	Reagan	Abe	1	1	1
$S_4$	Nixon	Teddy	0	1	0
$S_5$	Bush	Franklin	1	1	0

- The above is called a state assignment table and the state numbers, state names, and state bits are **arbitrarily** assigned here

University of Florida, EEL 3701 – File 17  
 © Drs. Schwartz & Arroyo

18

**EEL3701**

## Use Table To Get K-Maps

□ **STEPS 3 & 4: Obtain the next state K-Maps (using D-FFs).**

K-Map for  $D_2=Q_2^+$

States	Current			Next for X=0			Next for X=1		
	$Q_2$	$Q_1$	$Q_0$	$Q_2^+$	$Q_1^+$	$Q_0^+$	$Q_2^+$	$Q_1^+$	$Q_0^+$
$S_0$	0	0	0	0	0	1	0	0	0
$S_1$	0	0	1	0	0	1	0	1	1
$S_4$	0	1	0	0	0	1	0	0	0
$S_2$	0	1	1	1	1	1	0	1	0
unused	1	0	0	X	X	X	X	X	X
unused	1	0	1	X	X	X	X	X	X
$S_5$	1	1	0	1	1	1	0	1	0
$S_3$	1	1	1	1	1	1	1	1	0

Need 4 variable K-Maps because the inputs are: X,  $Q_2$ ,  $Q_1$ ,  $Q_0$  (4 variables).

If I had a longer paper, I'd use a 4-input (16-row) truth table

University of Florida, EEL 3701 – File 17  
© Drs. Schwartz & Arroyo

19

**EEL3701**

## Moore K-Maps

K-Map for  $Q_2^+$

$Q_1Q_0 \backslash Q_2X$	00	01	11	10
00	0	0	X	X
01	0	0	X	X
11	1	0	1	1
10	0	0	0	1

$Q_2^+ = Q_2Q_0 + Q_2/X + Q_1Q_0/X$

K-Map for  $Q_1^+$

$Q_1Q_0 \backslash Q_2X$	00	01	11	10
00	0	0	X	X
01	0	1	X	X
11	1	1	1	1
10	0	0	1	1

$Q_1^+ = Q_2 + Q_1Q_0 + Q_0X$

K-Map for  $Q_0^+$

$Q_1Q_0 \backslash Q_2X$	00	01	11	10
00	1	0	X	X
01	1	1	X	X
11	1	0	0	1
10	1	0	0	1

$Q_0^+ = /Q_1Q_0 + /X$


K-Map for  $Z_{\text{Moore}}$

$Q_1Q_0 \backslash Q_2$	0	1
00	0	X
01	0	X
11	0	0
10	1	1


$Z_{\text{Moore}} = Q_1/Q_0$

University of Florida, EEL 3701 – File 17  
© Drs. Schwartz & Arroyo

20

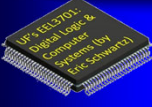 **EEL3701**  
**Implement Design with D-FF's**

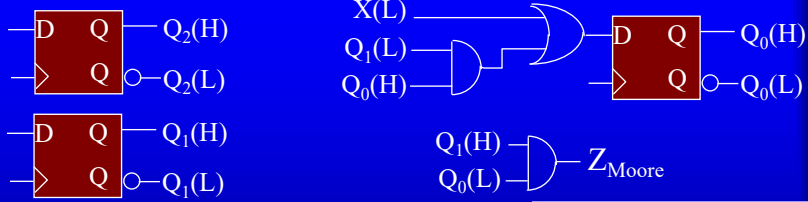□ Chose D-FF so that  $D_i = Q_i$ . (Could have chosen T, JK, or SR FFs.)




**NOTE:** A characteristic of the Moore design is that  $Z \neq f(\text{input})$ , i.e.  $Z = f(\text{state exclusively})$

□ For **this** example, the **Mealy** design is identical except for the output Z. A map for Mealy Z

$$Z_{\text{Mealy}} = Q_2X + Q_1Q_0X$$

University of Florida, EEL 3701 – File 17  
 © Drs. Schwartz & Arroyo

21

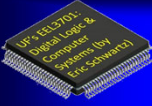 **EEL3701**  
**Synch. Moore Machine Output**

□ Let us apply the same sequence X to the Moore machine. **Note** the output is generated not during the transition from state to state, but “**after**” you arrive at the new state.

□ Recall, in the Moore machine,  $Z = Q_1/Q_0$


□ Obviously (by looking at the circuit) Z will not change until  $Q_0$  changes.  $Q_0$  changes with the CLK (as do all  $Q_i$ 's).

□ The next X comes in, then the CLK, then  $Q_0$  changes to reflect the new X, i.e.,  $Q_0$  (and therefore Z) lags (trails) X by up to 1 clock pulse.

**This is characteristic of Moore Machines!!!**

University of Florida, EEL 3701 – File 17  
 © Drs. Schwartz & Arroyo

22

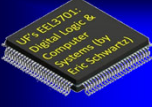 **EEL3701**

## Asynch Mealy Machine Outputs

□ Other than the delay, the two machines solve the same problem!

$X(H)$   
 $Q_1(L)$   
 $Q_0(H)$

$Q_0(H)$   
 $Q_1(H)$   
 $Q_1(L)$   
 $Q_2(H)$

$Z_{Mealy} = Q_2X + Q_1Q_0X$


$Z_{Mealy}$

□ Obviously (by looking at the circuit) Z can change independently of the clock when X changes.  $Q_i$ 's change with the clock.

University of Florida, EEL 3701 – File 17  
© Drs. Schwartz & Arroyo

23

23

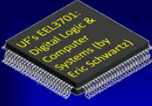 **EEL3701**

# *The End!*

University of Florida, EEL 3701 – File 17  
© Drs. Schwartz & Arroyo

24

24