

EEL3701

Menu

- VHDL
- VHDL: The Entity
- ~~• VHDL: IEEE 1076 TYPE~~
- ~~• VHDL: IEEE 1164 TYPE~~
- VHDL: The Architecture
- Mixed-Logic in VHDL
- VHDL MUX examples


See also example file on web:
Creating graphical components
 (Component_Creation.pdf)



See examples on web-site: (VHDL Examples) **NAnd2a.vhd**, **NAnd2b.vhd**, **Mux2to1*.vhd**,
 * = a-f, **Mux41***

University of Florida, EEL 3701 – File 19
 © Dr. Eric M. Schwartz

1

 


EEL3701 Introduction to VHDL

- Q: What is **VHDL**?
- A: **VHSIC** **H**ardware **D**escription **L**anguage
- Q: What is **VHSIC**?
- A: **V**ery **H**igh **S**peed **I**ntegrated **C**ircuits
- Q: What is VHDL used for?
- A: To describe and test a digital circuit in a high level language environment. When used in conjunction with a router and logic generator a silicon mask can be created.
- A competitor to VHDL is **Verilog**.
 >VHDL is older and more widely used until recently, but ...

University of Florida, EEL 3701 – File 19
 © Dr. Eric M. Schwartz

2

2

 


EEL3701

VHDL Syntax

- VHDL is case insensitive
 - > GOOD = **Good** = good = gOOD
- Everyone has their own conventions; mine follows:
 - > Keyword of VHDL are all lower case
 - > Entity and architecture names are all upper case
 - > Identifiers start with a capital
 - > All new words in a given identifier is again capitalized
- White space (spaces or tabs) is fine anywhere as separators
- The semicolon is a statement terminator
- Two dashes (“--”) indicate a comment follows
- Identifiers must begin with a letter; subsequent characters are alphanumeric or “_”
- No precedence in VHDL; resolves left-to-right; use paren. (except **not** has precedence over logical operators)

University of Florida, EEL 3701 – File 19
© Dr. Eric M. Schwartz

3

 

EEL3701

VHDL: The Entity

```
entity NAND2a is
  port(
    A,B: in bit;
    C: out bit);
end NAND2a;
```

□ The entity is the description of inputs and outputs to a black box




- Example:


```
entity BLACK_BOX is port(
  Clock, Reset: in bit;
  D:           in bit_vector(7 downto 0);
  Q:           out bit_vector(7 downto 0);
  CO:         out bit);
end BLACK_BOX;
```

University of Florida, EEL 3701 – File 19
© Dr. Eric M. Schwartz

4

 

EEL3701

VHDL: The Entity

Entity syntax:


```
entity ENTITY_NAME is port(
  -- optional parameterized components
  Name1: mode type;
  Name2: mode type;
  ...
  NameN: mode type);
end ENTITY_NAME;
```

```
entity NAND2a is
  port(
    A,B: in bit;
    C: out bit);
end NAND2a;
```

- Names can be a list of names separated by commas (as in the NAND2a above right)
- Modes describe data direction flow
- Types indicate the set of values the port name can be assigned

University of Florida, EEL 3701 – File 19
© Dr. Eric M. Schwartz

5

 

EEL3701

VHDL: The Entity: PORT MODE


```
entity NAND2a is
  port(
    A,B: in bit;
    C: out bit);
end NAND2a;
```

- Ports are often associated with pins
- Ports are a special class of something called a *signal*
 - > Ports have a *signal* name, mode and type

```
entity NAND2a is
  port(A,B: in bit; C: out bit);
end NAND2a;
```

University of Florida, EEL 3701 – File 19
© Dr. Eric M. Schwartz

6

 

EEL3701
VHDL: The Entity:
PORT MODE


```
entity NAND2a is
  port(
    A,B: in bit;
    C: out bit);
end NAND2a;
```

Mode possibilities: *in, out, inout, buffer*

- *in* Data goes into the entity (and not out)
- *out* Data goes out of the entity (but not in and is not used internally)
- *inout* Data is bi-directional
- *buffer* Data goes out of the entity and is also **fed back** within the entity

University of Florida, EEL 3701 – File 19
© Dr. Eric M. Schwartz

7

 

EEL3701
VHDL: bit and
bit_vector

```
entity NAND2a is
  port(
    A,B: in bit;
    C: out bit);
end NAND2a;
```

- VHDL is **strongly** typed, *i.e.*, you cannot assign a signal of one type to the signal of another type
- *bit* - a signal that can have the value 0 or 1 (low and high, respectively)
- *bit_vector* - a set of bits

Examples:

```
signal X: bit_vector(0 to 3);      --ascending range
signal Y: bit_vector(3 downto 0); --descending range
X <= "0111"; --double quotes used for vectors
Y <= "1010"; --double dash used for comments
```


The assigned values are (**single quotes used for scalars**):

```
X(0) <= '0'; X(1) <= '1'; X(2) <= '1'; X(3) <= '1';
Y(3) <= '1'; Y(2) <= '0'; Y(1) <= '1'; Y(0) <= '0';
```

Don't use to (use downto)

University of Florida, EEL 3701 – File 19
© Dr. Eric M. Schwartz

8

 

EEL3701 VHDL: Assignment Operator & Quotes

Don't use to (use downto)

```


signal X: bit_vector(0 to 3);      --ascending range
signal Y: bit_vector(3 downto 0); --descending range
X <= "0111"; --double quotes used for vectors
Y <= "1010"; --double dash used for comments
The assigned values are (single quotes used for scalars):
X(0) <= '0'; X(1) <= '1'; X(2) <= '1'; X(3) <= '1';
Y(3) <= '1'; Y(2) <= '0'; Y(1) <= '1'; Y(0) <= '0';

```

- The **<=** is the assignment operator, but also a “less than or equal to symbol”
 - > The context determines which interpretation is necessary
- Signals are wires (nodes) in a design
- Bits in single quotes, *e.g.*, X(0) <= '1'
- Strings in double quotes, *e.g.*, Y<="1010"
- Bit and bit_vector **rarely** used now

University of Florida, EEL 3701 – File 19
© Dr. Eric M. Schwartz

9

 

EEL3701 VHDL: Some IEEE 1076 Types


- Integer
 - > Used for indexing, constants, *etc.*
- Boolean
 - > Take on values of 0 and 1 (low and high)
 - > **No mixed-logic** in VHDL or in the IEEE 1076 standard
- Enumerated
 - > User defined set of possible values
 - > Ex:


```
type Move is (Start, Slow, Fast, Stop);
```

University of Florida, EEL 3701 – File 19
© Dr. Eric M. Schwartz

10

10

 


EEL3701

VHDL: IEEE 1164 TYPE

- IEEE 1164 standard is a multi-valued logic system
- **Nine** values (**not** binary)
- Makes writing VHDL code significantly simpler
- Two types -- **std_logic** and **std_logic_vector** -- replace the old types **bit** and **bit_vector**, respectively
- **std_logic** and **std_logic_vector** are the industry standards for digital design

University of Florida, EEL 3701 – File 19
© Dr. Eric M. Schwartz

11

 

EEL3701

VHDL: IEEE 1164 TYPE

- IEEE 1164 defines the following type:

```


type std_ulogic is ('U', -- Uninitialized
                  'X', -- Forcing unknown
                  '0', -- Forcing 0
                  '1', -- Forcing 1
                  'Z', -- High impedance
                  'W', -- Weak unknown
                  'L', -- Weak 0
                  'H', -- Weak 1
                  '-', -- Don't care
                  );
  
```

same types as std_logic

Only these allowed in VHDL simulator

University of Florida, EEL 3701 – File 19
© Dr. Eric M. Schwartz

12

 


EEL3701 VHDL: IEEE 1164 TYPE

- ‘L’ (weak ‘0’) means floats ‘L’; but an input can easily drive it to high; think “*pull-down*”
- ‘H’ (weak ‘1’) means floats ‘H’; but an input can easily drive it to low; think “*pull-up*”
- The type **std_logic** is a “resolved version” of **std_ulogic**, *i.e.*, a decision is made when a signal is driven from multiple sources
- Do **not** use **std_ulogic** and **std_ulogic_vector**
- **std_logic_vector** is a grouping of **std_logic** (just as **bit_vector** is a grouping of **bit**)
- Must use **std_logic** and **std_logic_vector** if need more than the two values (0 and 1 = low and high, respectively) available with **bit** and **bit_vector**


University of Florida, EEL 3701 – File 19
© Dr. Eric M. Schwartz

13

 

EEL3701 MEMORY_DEV Entity Example

 - Synchronous circuit, *i.e.*, Clk input
- AD (AD0-AD7), tri-state bi-directional
- D (D8-D15), output only
- AS, output also used internally
- OE, input only




```

library ieee;
use ieee.std_logic_1164.all;
entity MEMORY_DEV is port(
  Clk, OE: in      std_logic;
  AD:      inout   std_logic_vector(7 downto 0);
  D:      out      std_logic_vector(15 downto 8);
  AS:      buffer  std_logic);
end MEMORY_DEV;
  
```

University of Florida, EEL 3701 – File 19
© Dr. Eric M. Schwartz

14

 


EEL3701 Architecture

- Architecture describes the function of a particular entity (or entities)
- Two types of architecture: Structural & Behavioral
 - > **Structural architecture:** Connections of previously defined components
 - > **Behavioral architecture:** High level “programming-type” description
 - Assignments: `:=` (for variables), `<=` (for signals and states)
 - Logic Operators: `and`, `or`, `not`, `nand`, `nor`, `xor`, `xnor`
 - Comparisons: `=`, `/=`, `>`, `<`, `<=`, `>=`
 - Constructs: `if-then-else`, `for`, `when-else`, `case`, `with-select`

University of Florida, EEL 3701 – File 19
© Dr. Eric M. Schwartz

15

 

EEL3701 Architecture Syntax

```
entity NAND2a is
  port(
    A,B: in bit;
    C: out bit);
end NAND2a;
```

```
architecture architecture_name of MODEL_NAME is
  -- optional signals defined here
  begin
    ...
    VHDL concurrent statements
    ...
  end architecture_name;
```

Example:


```
architecture behavior of NAND2a is
  signal COut: bit;

  begin
    COut <= A and B;
    C <= not COut;
  end behavior;
```

Your choice of name

University of Florida, EEL 3701 – File 19
© Dr. Eric M. Schwartz

16

 

EEL3701

Architecture Syntax

- Prior to the first architecture line, you may have **library** and **use** statements


```
library ieee;
use ieee.std_logic_1164.all;
entity NAND2b is
  port(
    A,B: in std_logic;
    C:   out std_logic);
end NAND2b;
architecture behavior of NAND2b is
  signal COut: std_logic;
begin
  COut <= A and B;
  C <= not COut;
end behavior;
```

Notice no semicolon following the is (for either entity or architectures)

Signals (if needed) are defined immediately following the architecture statement.

University of Florida, EEL 3701 – File 19
© Dr. Eric M. Schwartz

17

 


EEL3701

A Mixed-Logic Activation-Level Convention

- VHDL does **not** have any built in mixed-logic or activation-level constructs
- My convention follows:
 - > Active-low signals are those with a **_L** ending, e.g., and active-low signal X is represented as X_L
 - > Active-high signals are those without a **_L** ending
 - > The logic equations include only the original signal names with **no** **_L** endings
- Each active-low signal requires an additional signal definition

University of Florida, EEL 3701 – File 19
© Dr. Eric M. Schwartz

18

 

EEL3701

Mixed-Logic Example in VHDL


- My convention follows:
 - > Active-low signals are those with a L ending, e.g., and active-low signal X is represented as X_L
 - > Active-high signals are those without a L ending
 - > The logic equations include only the original signal names with **no** L endings
- Notice that the logic equations do **not** have activation-levels mixed in

```

library ieee; use ieee.std_logic_1164.all;
entity MIX_LOG is port(
    A,B,C_L,D_L: in  std_logic;
    X_L,Y:         out std_logic);
end MIX_LOG;
architecture behavior of MIX_LOG is
    signal X, C, D: std_logic;
begin
    -- Define inputs
    C <= not C_L; D <= not D_L;
    -- Define outputs
    X_L <= not X;
    -- Define logic equations
    -- (No _L in below equations)
    X <= A and B;
    Y <= C or D;
end behavior;
Mixed_Logic.vhd
  
```

University of Florida, EEL 3701 – File 19
© Dr. Eric M. Schwartz

19

 

EEL3701

Example VHDL for an Octal 2-input MUX

```


library ieee; use ieee.std_logic_1164.all;
entity MUX2to1_a is port(
    A, B: in  std_logic_vector(7 downto 0);
    Sel: in  std_logic;
    Y: out std_logic_vector(7 downto 0));
end MUX2to1_a;

architecture behavior of MUX2to1_a is
begin
    Y(0) <= ( B(0) and Sel ) or
             ( A(0) and not(Sel) );
    Y(1) <= ( B(1) and Sel ) or
             ( A(1) and not(Sel) );
    ...
    Y(7) <= ( B(7) and Sel ) or
             ( A(7) and not(Sel) );
end behavior;
Mux2to1a.vhd
  
```

Logical Operators


University of Florida, EEL 3701 – File 19
© Dr. Eric M. Schwartz

20

 

EEL3701

Example VHDL for an Octal 2-input MUX

 

```

library ieee; use ieee.std_logic_1164.all;
entity MUX2to1_b is port(
  A, B:      in  std_logic_vector(7 downto 0);
  Sel:       in  std_logic;
  Y:         out std_logic_vector(7 downto 0));
end MUX2to1_b;


architecture behavior of MUX2to1_b is
  signal Temp: std_logic_vector(7 downto 0);
begin
  Temp <= (Sel, Sel, others=>Sel);
  -- or could use Temp <= (others=>Sel);
  Y <= ( B and Temp ) or
      ( A and (not Temp) ); -- must have same types for and & or
end behavior;

```

Logical Operators and vectors (also use of "others")


University of Florida, EEL 3701 – File 19
© Dr. Eric M. Schwartz
Mux2to1b.vhd
21

21

 

EEL3701

Example VHDL for an Octal 2-input MUX

 

```

library ieee;
use ieee.std_logic_1164.all;
entity MUX2to1_c is port(
  A, B:      in  std_logic_vector(7 downto 0);
  Sel:       in  std_logic;
  Y:         out std_logic_vector(7 downto 0));
end MUX2to1_c;


architecture behavior of MUX2to1_c is
begin
  Y <= B when (Sel='1') else A; --'Y<=' not repeated
end behavior;

```

when

University of Florida, EEL 3701 – File 19
© Dr. Eric M. Schwartz
Mux2to1c.vhd
22

22

 

EEL3701


Example VHDL for an Octal 2-input MUX

```

library ieee;
use ieee.std_logic_1164.all;
entity MUX2to1_d is port(
  A, B:      in  std_logic_vector(7 downto 0);
  Sel:       in  std_logic;
  Y:         out std_logic_vector(7 downto 0));
end MUX2to1_d;

architecture behavior of MUX2to1_d is
begin
  with Sel select
    Y <= B  when '1',
         A  when '0',      -- can remove either this line
                           -- or this line (but ; at end)
end behavior;

```

 


Mux2to1d.vhd

with-select

University of Florida, EEL 3701 – File 19
© Dr. Eric M. Schwartz

23

 


EEL3701

Example VHDL for an Octal 2-input MUX

```

library ieee;use ieee.std_logic_1164.all;
entity MUX2to1_e is port(
  A, B:      in  std_logic_vector(7 downto 0);
  Sel:       in  std_logic;
  Y:         out std_logic_vector(7 downto 0));
end MUX2to1_e;
architecture behavior of MUX2to1_e is
begin
  COMB: process (Sel, A, B) --rerun process if any changes
  begin
    Y <= A;
    if (Sel = '1') then
      Y <= B;
    end if; -- note that "end if" is two words
  end process COMB;
end behavior;

```

 



Mux2to1e.vhd

if-then

University of Florida, EEL 3701 – File 19
© Dr. Eric M. Schwartz

24

   **EEL3701**
Example VHDL for an Octal 2-input MUX



```

library ieee; use ieee.std_logic_1164.all;
entity MUX2to1_e is port(
  A, B:      in  std_logic_vector(7 downto 0);
  Sel:       in  std_logic;
  Y:         out std_logic_vector(7 downto 0));
end MUX2to1_e;
architecture behavior of MUX2to1_e is
begin
  COMB: process (Sel, A, B) --rerun process if any changes
  begin
    if (Sel = '1') then
      Y <= B;
    else
      Y <= A;
    end if; -- note that "end if" is two words
  end process COMB;
end behavior;


```


 Mux2to1f.vhd

if-then-else

University of Florida, EEL 3701 – File 19
 © Dr. Eric M. Schwartz

25

 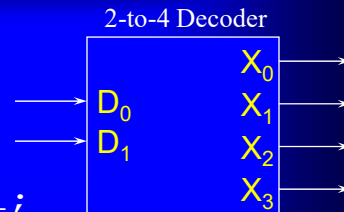 **EEL3701**
Example VHDL for a 2-to-4 Decoder



```

library ieee;
use ieee.std_logic_1164.all;
entity DEC2to4 is port(

```

What would you put here?
 >std_logic (bit) or std_logic_vector (bit_vector)

```


);
end DEC2to4;
architecture behavior of DEC2to4 is
begin

```

What would you put here?
 end behavior;

University of Florida, EEL 3701 – File 19
 © Dr. Eric M. Schwartz


26

 

EEL3701 4-Input MUX

```

library ieee;
use ieee.std_logic_1164.all;
entity MUX41a is port (
    S1, S0:      in    bit;
    D3, D2, D1, D0: in    bit;
    Y:           out   bit
);
end MUX41a;
architecture logic OF MUX41a IS
begin
-- Y = (D0 * /S1 * /S0) + (D1 * /S1 * S0) + (D2 * S1 * /S0) + (D3 * S1 * S0)
-- Y = (D0 * /S1 * /S0) + (D1 * /S1 * S0) +
--      (D2 * S1 * /S0) + (D3 * S1 * S0)
    Y <= (D0 and (not S1) and (not S0)) or
          (D1 and (not S1) and (S0)) or
          (D2 and S1 and (not S0)) or
          (D3 and S1 and (S0)) ;
end logic;
          
```

 


mux41a.vhd

mux41.vhd

mux41b.vhd

University of Florida, EEL 3701 – File 19
© Dr. Eric M. Schwartz

27

 

EEL3701 Making New Components with Quartus

- Compile a VHDL file (.vhd) or a Graphic Design File (.bdf)
- In the same directory, open or create a new BDF file.
- Double-click and the select *Enter Symbol*
- You will find your new part named in the list of libraries
- Just select it and the process is complete!




Component_Creation.pdf

University of Florida, EEL 3701 – File 19
© Dr. Eric M. Schwartz

28

28

 

29