

EEL3701


Menu

- More ASM design examples
- ROMs for ASMs



University of Florida, EEL 3701 – File 20
© Drs. Schwartz & Arroyo

1

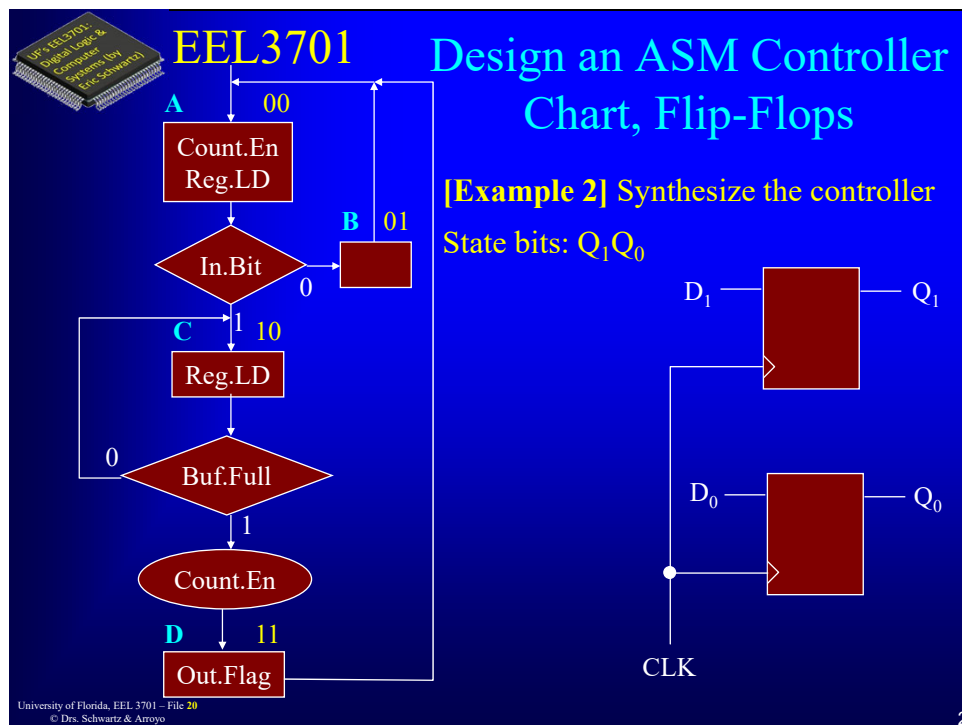

2

EEL3701 Next-State Truth Table

□ To synthesize we need the *next state table*.

In.Bit	Buf.Full	Q ₁	Q ₀	Q ₁ ⁺	Q ₀ ⁺
0	0	0	0	0	1
0	1	0	0	0	1
1	0	0	0	1	0
1	1	0	0	1	0
0	*	0	0	0	1
1	*	0	0	1	0

University of Florida, EEL 3701 – File 20
© Drs. Schwartz & Arroyo

3

3

EEL3701 Complete Next-State Truth Table

- Rearrange the inputs and state bits to allow wild cards but keep in “counting” order.

Q ₁	Q ₀	In.Bit	Buf.Full	Q ₁ ⁺	Q ₀ ⁺	Count.En	Reg.LD	Out.Flag
0	0	0	*	0	1	1	1	0
0	0	1	*	1	0	1	1	0
0	1	*	*	0	0	0	0	0
1	0	*	0	1	0	0	1	0
1	0	*	1	1	1	1	1	0
1	1	*	*	0	0	0	0	1

University of Florida, EEL 3701 – File 20
© Drs. Schwartz & Arroyo

4

4

EEL3701 Complete Next-State Truth Table

• No rearranging or wild cards.

Q1	Q0	In.Bit	Buf.Full	Q1+	Q0+	Count.En	Reg.LD	Out.Flag
0	0	0	0	0	1	1	1	0
0	0	0	1	0	1	1	1	0
0	0	1	0	1	0	1	1	0
0	0	1	1	1	0	1	1	0
0	1	0	0	0	0	0	0	0
0	1	0	1	0	0	0	0	0
0	1	1	0	0	0	0	0	0
0	1	1	1	0	0	0	0	0
1	0	0	0	1	0	0	1	0
1	0	0	1	1	1	1	1	0
1	0	1	0	1	0	0	1	0
1	0	1	1	1	1	1	1	0
1	1	0	0	0	0	0	0	1
1	1	0	1	0	0	0	0	1
1	1	1	0	0	0	0	0	1
1	1	1	1	0	0	0	0	1

University of Florida, EEL 3701 – File 20
© Drs. Schwartz & Arroyo

What size K-Maps do we need? (2 states & 2 inputs)

Note: There are a lot of 0's because, for example, we can only go from B→A. However, the other combinations (B→C, B→B, B→D) cannot occur.

5

EEL3701 Complete Next-State Truth Table

• No rearranging or wild cards.

A3	A2	A1	A0	D4	D3	D2	D1	D0
Q1	Q0	In.Bit	Buf.Full	Q1+	Q0+	Count.En	Reg.LD	Out.Flag
0	0	0	0	0	1	1	1	0
0	0	0	1	0	1	1	1	0
0	0	1	0	1	0	1	1	0
0	0	1	1	1	0	1	1	0
0	1	0	0	0	0	0	0	0
0	1	0	1	0	0	0	0	0
0	1	1	0	0	0	0	0	0
0	1	1	1	0	0	0	0	0
1	0	0	0	1	0	0	1	0
1	0	0	1	1	1	1	1	0
1	0	1	0	1	0	0	1	0
1	0	1	1	1	1	1	1	0
1	1	0	0	0	0	0	0	1
1	1	0	1	0	0	0	0	1
1	1	1	0	0	0	0	0	1
1	1	1	1	0	0	0	0	1


University of Florida, EEL 3701 – File 20
© Drs. Schwartz & Arroyo

2 inputs & 2 state bits, so need 4 address bits or $2^4 = 16$ addresses


2 states bits (FF excitation inputs) & 3 outputs, so need 5 data bits

Need a 16 x 5 ROM


6

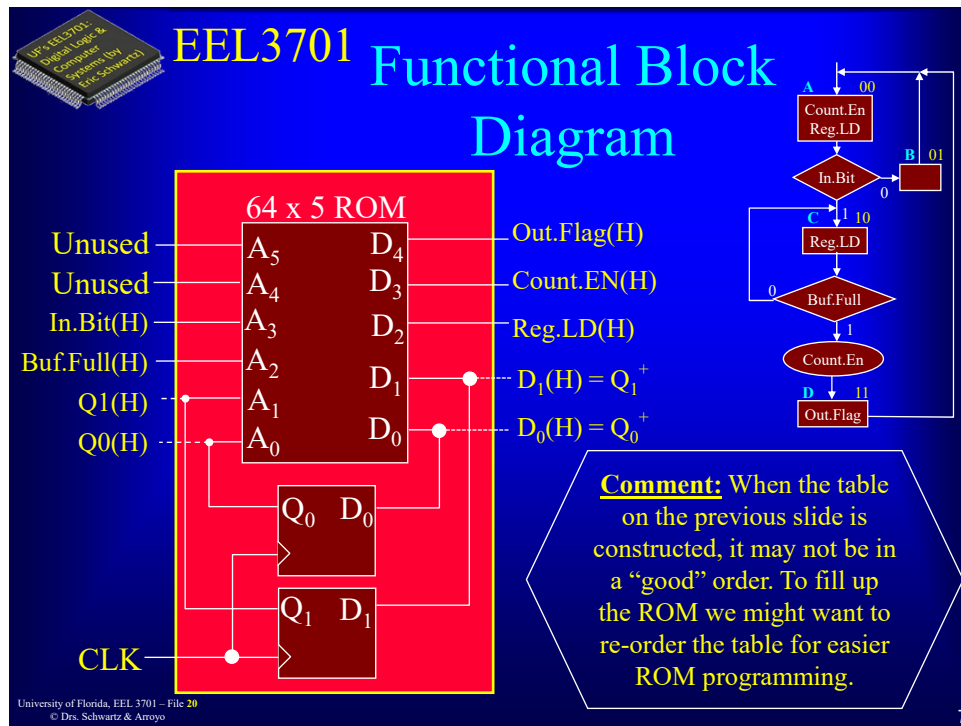


7

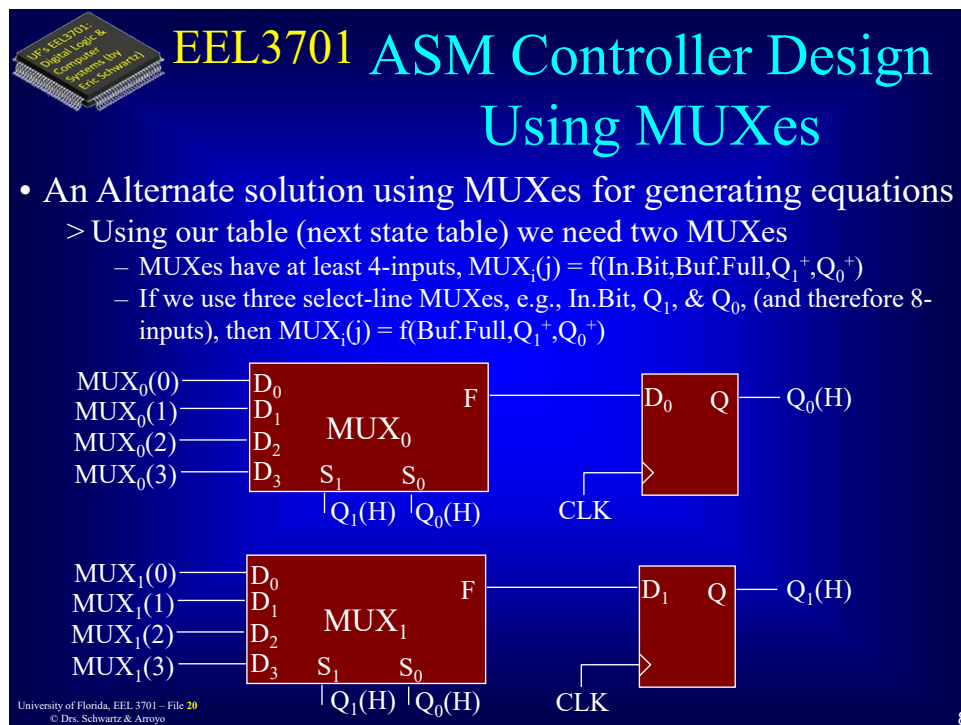


8

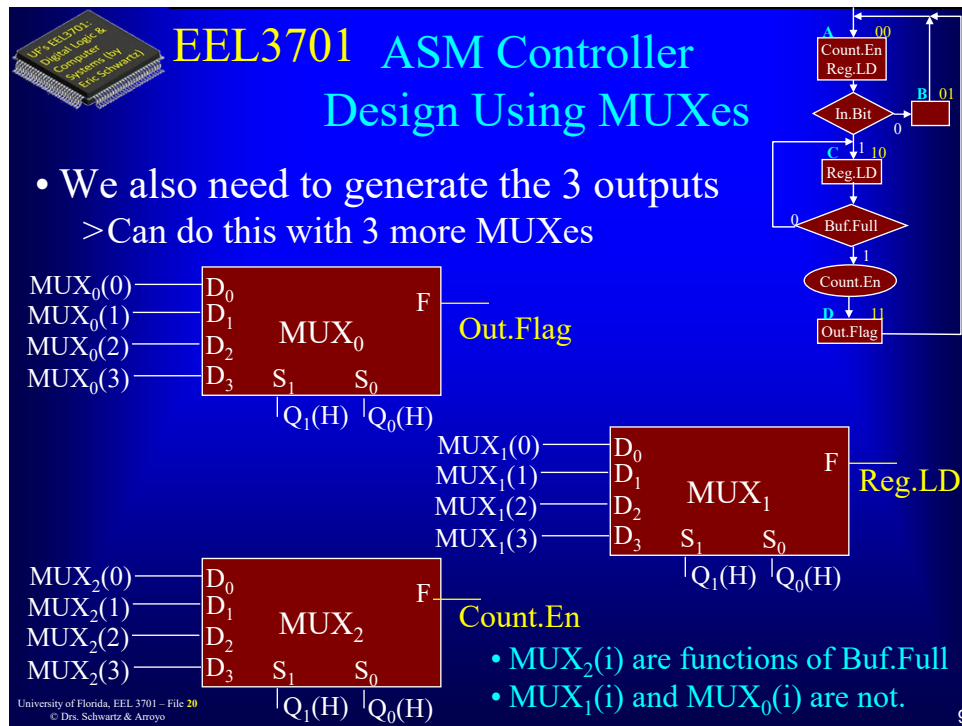

9

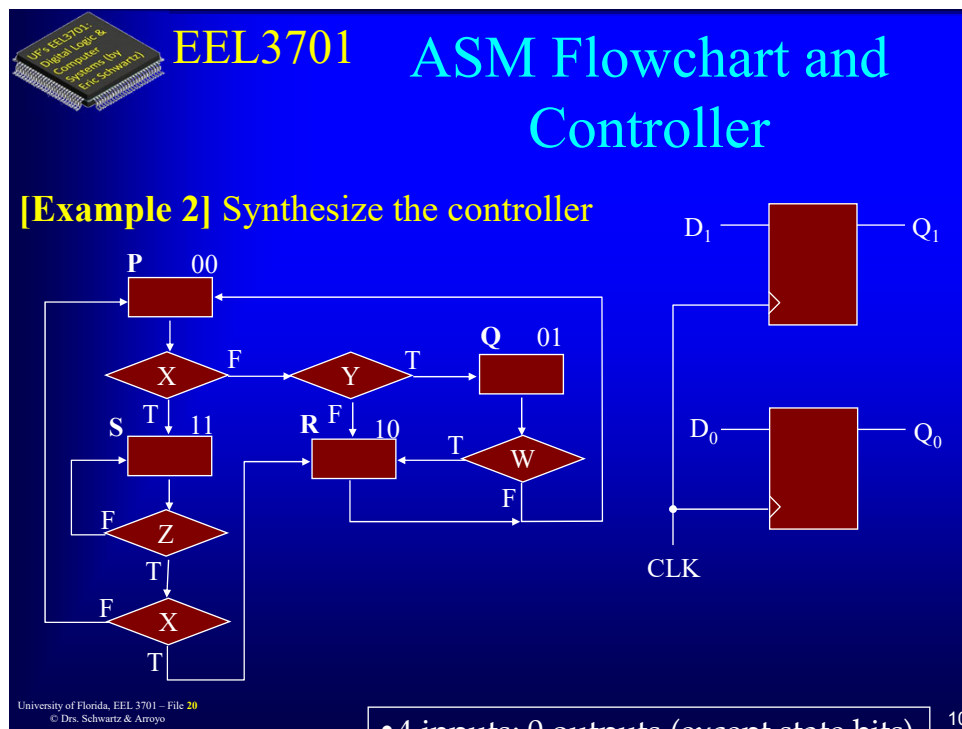

10

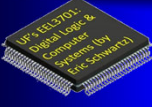 **EEL3701**

Next-State Truth Table

□ To synthesize we need *next state table*.

Current State		Next State		Condition for Transition
Q_1	Q_0	Q_1^+	Q_0^+	
P	0	0	1	$/X \bullet Y$
P	0	0	0	$/X \bullet /Y$
P	0	0	1	X
Q	0	1	0	$/W$
Q	0	1	0	W
R	1	0	0	True
S	1	1	0	$/X \bullet Z$
S	1	1	0	$X \bullet Z$
S	1	1	1	$/Z$


What size K-Map do we need?
(2 states & 4 inputs)

✓


Note: There are a lot of “Don’t Cares” because, for example, we can only go from $R \rightarrow P$. (The other combinations, $R \rightarrow Q$, $R \rightarrow R$, & $R \rightarrow S$, can’t occur.)

University of Florida, EEL 3701 – File 20
© Drs. Schwartz & Arroyo

11

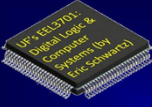
 **EEL3701** MUX Implementation of Controller

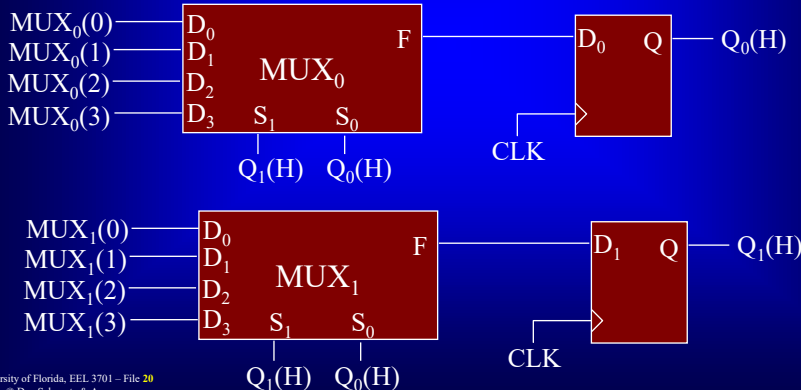- Using our table (next state table) we need two MUXes (with at least 4-inputs), $MUX_i(j) = f(W, X, Y, Z)$



University of Florida, EEL 3701 – File 20
© Drs. Schwartz & Arroyo

12

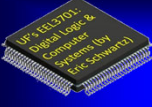
 **EEL3701**

MUX Implementation


- Looking at our table, when at P (00) $Q_0^+ = 1$ when $/X \bullet Y = 1$ or $X = 1$, that is, rows 1 and 3.
- $\therefore \text{MUX0}(0) = /X \bullet Y + X = X + Y$



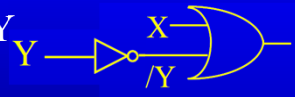- Similarly, for MUX1(0), $Q_1^+ = 1$ in rows 2 and 3.
- $\therefore \text{MUX1}(0) = /X \bullet /Y + X = X + /Y$



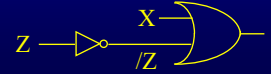- The other equations are straight forward!
- MUX0(1) = 0 MUX1(1) = W
- MUX0(2) = 0 MUX1(2) = 0
- MUX0(3) = /Z MUX1(3) = $X \bullet Z + /Z = X + /Z$




Assume all inputs active-high

University of Florida, EEL 3701 – File 20
© Drs. Schwartz & Arroyo


13

13

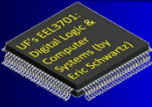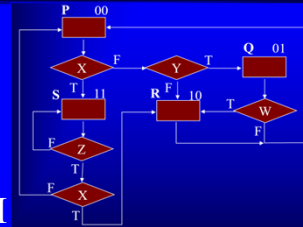 **EEL3701 ROM**

Implementation

- 4 inputs & 2 states
- > So need $2^{2+4} = 2^6 = 64$ inputs for ROM
- > So we need a 64 x 2 ROM



# of Entries	W	X	Y	Z	Q_1^+	Q_0^+	D_3	D_2	D_1	D_0
4	-	0	0	-	0	0	X	X	1	0
4	-	0	1	-	0	0	X	X	0	1
8	-	1	-	-	0	0	X	X	1	1
8	0	-	-	-	0	1	X	X	0	1
8	1	-	-	-	0	1	X	X	1	0
16	-	-	-	-	1	0	X	X	0	0
4	-	0	-	1	1	1	X	X	0	0
4	-	1	-	1	1	1	X	X	1	0
8	-	-	-	0	1	1	X	X	1	1

University of Florida, EEL 3701 – File 20
© Drs. Schwartz & Arroyo

14

14

EEL3701

Functional Block Diagram

The diagram shows a 64 x 4 ROM with inputs W(H), X(H), Y(H), Z(H), Q1(H), and Q0(H) on the left, and outputs D₃, D₂, D₁, and D₀ on the right. The inputs are connected to address lines A₅ through A₀. The outputs are connected to data lines D₃ through D₀. A clock signal (CLK) is connected to the clock inputs of two D flip-flops, Q₀ and Q₁. The output of Q₀ is connected to D₀, and the output of Q₁ is connected to D₁. The outputs of the flip-flops are also connected to the inputs Q1(H) and Q0(H) of the ROM.

The state transition diagram shows a sequence of states: P (00), X (11), S (10), Z (01), and Y (01). The transitions are labeled with inputs and outputs. The diagram includes decision diamonds for X, Y, Z, and W, and a state box for Q (01). The transitions are: P to X (input 00), X to S (input 11), S to Z (input 10), Z to Y (input 01), and Y to Q (input 01). The outputs are: X to S (output 11), Z to Y (output 01), and Y to Q (output 01).

Comment: When the table on the previous slide is constructed, it may not be in a “good” order. To fill up the ROM we might want to re-order the table for easier ROM programming. You will program an ROM in Lab 7.

University of Florida, EEL 3701 – Fall 20
© Drs. Schwartz & Arroyo

15

15

Washing Machine: ROM Realization

• STEP 3 ROM realization

000 001 010 011 100 101

Idle Agitate Drain Rinse Rinse2 SpinIt

STRT SHOT EMP FULL TO

A₀ A₁ A₂ A₃ A₄ A₅ A₆ A₇

256 x 10 ROM

D₀ D₁ D₂ D₃ D₄ D₅ D₆ D₇ D₈ D₉

PUMP FILL AG OHOT STIME SPIN STRTOFF

Q₀ Q₁ Q₂

D₀ D₁ D₂

CLK

Register

Inputs


- STRT (Start from User)
- SHOT (Select Hot from User)
- FULL (Tub Full Indicator)
- EMP (Tub Empty Indicator)
- TO (Timer Out Indicator)

Outputs

- OHOT (Turn On Hot water valve)
- PUMP (Turn On Pump)
- FILL (True: water-in, False: water-out)
- AG (Agitate)
- STIME (Clear & Start Timer)
- SPIN (Spin Dry)
- STRTOFF (Go to Idle State)

University of Florida, EEL 3701 - File 20
© Drs. Schwartz & Arroyo

16

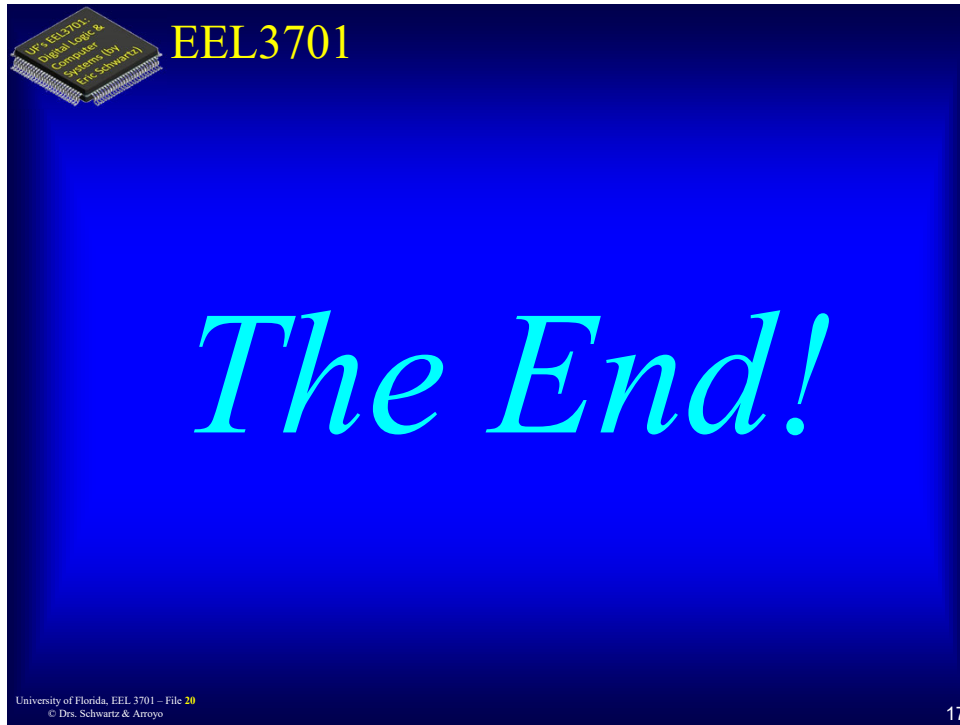

17