
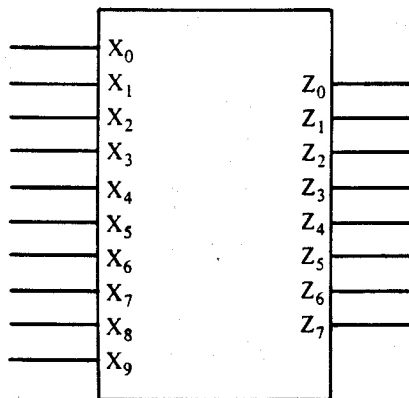


$$Z_i = f(X_0, X_1, X_2, \dots, X_9)$$


 


(a) Functional block diagram





(b) Two-level AND-OR structure



Figure 6.8 Conventional realization of a multiinput and multioutput circuit.

  

(a) AND gates

  


(b) OR gates

  


(c) Inverter

Figure 6.9 Equivalent PLA logic diagrams.

 


(a) Common circuit diagram

 

(b) PLA circuit diagram


Figure 6.10 PLA circuit diagram for Example 6.1.

 

(a) Functional block diagram


X_0	X_1	X_2	X_3	Z_0	Z_1
0	0	0	0	0	0
0	0	0	1	1	0
0	0	1	0	1	1
0	0	1	1	0	0
0	1	0	0	0	0
0	1	0	1	1	1
0	1	1	0	0	1
0	1	1	1	0	0
1	0	0	0	1	0
1	0	0	1	0	0
1	0	1	0	0	0
1	0	1	1	0	0
1	1	0	0	1	1
1	1	0	1	0	0
1	1	1	0	0	1
1	1	1	1	0	0

(b) Truth table


 


(c) PLA realization

Figure 6.11 Illustration for Example 6.2.

 



(a) Functional block diagram

  

(c) Conventional minimization results in a total of nine distinct AND terms

X_0	X_1	X_2	X_3	Z_0
0	0	0	0	1
0	0	0	1	1
0	0	1	0	1
0	0	1	1	0
0	1	0	0	0
0	1	0	1	1
0	1	1	0	0
0	1	1	1	1
1	0	0	0	1
1	0	0	1	1
1	0	1	0	0
1	0	1	1	0
1	1	0	0	1
1	1	0	1	0
1	1	1	0	0
1	1	1	1	1

(b) Truth table

 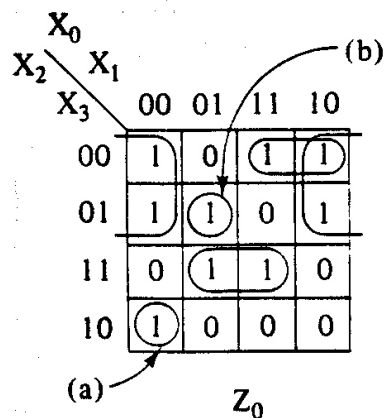

$$Z_0 = \bar{X}_1 \bar{X}_2 + \bar{X}_0 \bar{X}_1 X_2 \bar{X}_3 + \bar{X}_0 X_1 \bar{X}_2 X_3 + X_1 X_2 X_3 + X_0 \bar{X}_2 \bar{X}_3$$


$$Z_1 = \bar{X}_0 \bar{X}_1 X_2 \bar{X}_3 + \bar{X}_0 X_1 \bar{X}_2 X_3 + X_0 \bar{X}_2 \bar{X}_3 + X_1 X_2 \bar{X}_3 + X_0 \bar{X}_1 X_2 X_3$$

(d) Minimization for PLA realization – a total of seven distinct AND terms

Figure 6.12 Illustration for Example 6.3.

$$Z_0 = \bar{X}_1 \bar{X}_2 + \bar{X}_0 \bar{X}_1 X_2 \bar{X}_3 + \bar{X}_0 X_1 \bar{X}_2 X_3 + X_1 X_2 X_3 + X_0 \bar{X}_2 \bar{X}_3$$
 
$$Z_1 = \bar{X}_0 \bar{X}_1 X_2 \bar{X}_3 + \bar{X}_0 X_1 \bar{X}_2 X_3 + X_0 \bar{X}_2 \bar{X}_3 + X_1 X_2 \bar{X}_3 + X_0 \bar{X}_1 X_2 X_3$$



(e) PLA realization

Figure 6.12 (cont.)


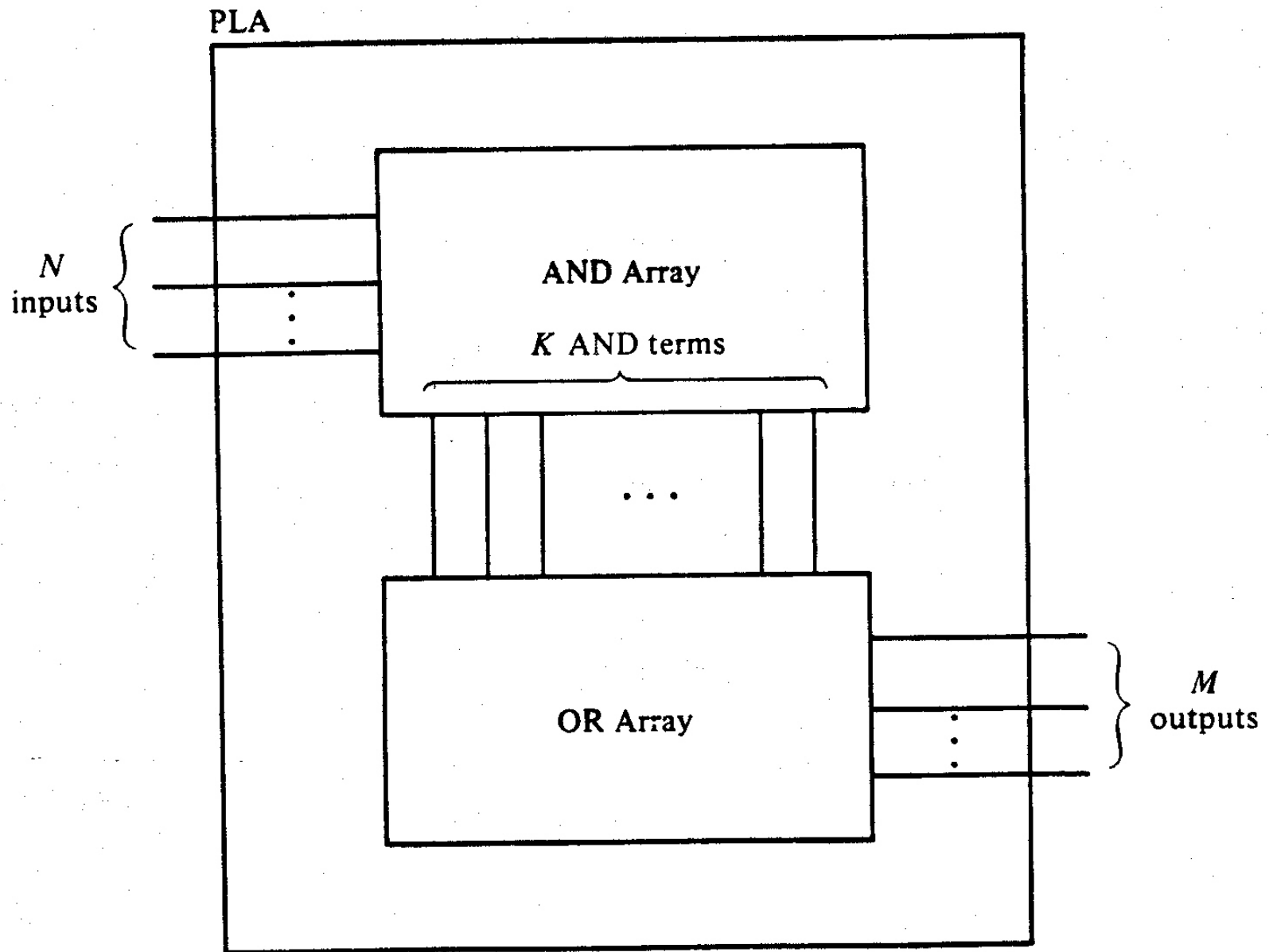


Figure 6.13 PLA with N inputs, M outputs, and K AND terms.

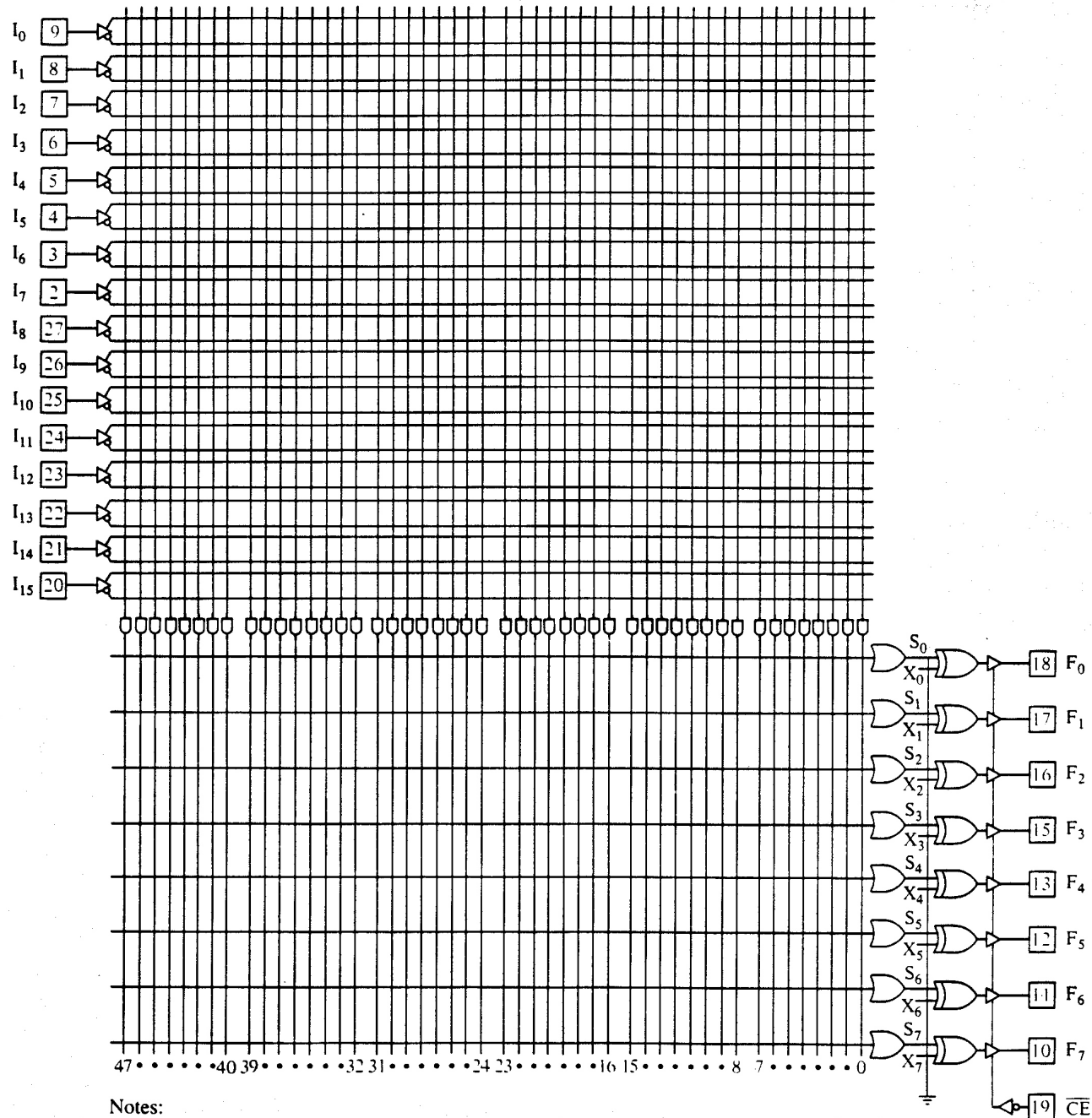

Notes:

1. All AND/XOR gate inputs with a blown link float to a logic 1
2. All OR gate inputs with a blown link float to a logic 0

Figure 6.14 82S100 FPLA. (Courtesy of Signetics Corporation.)

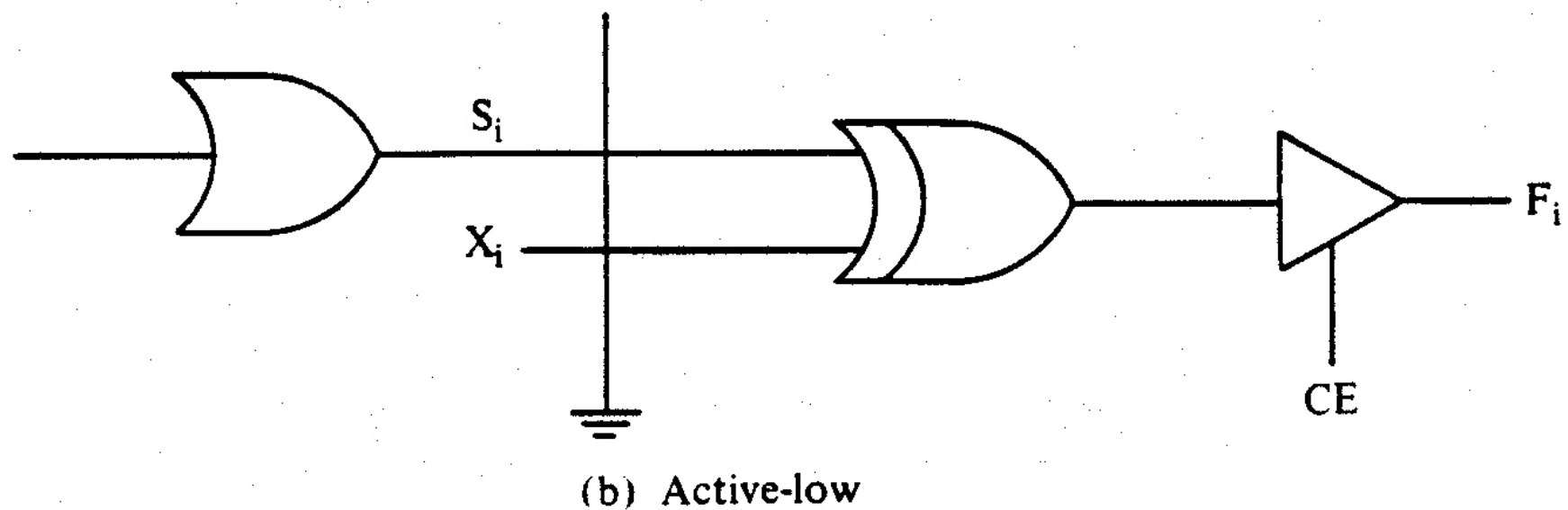
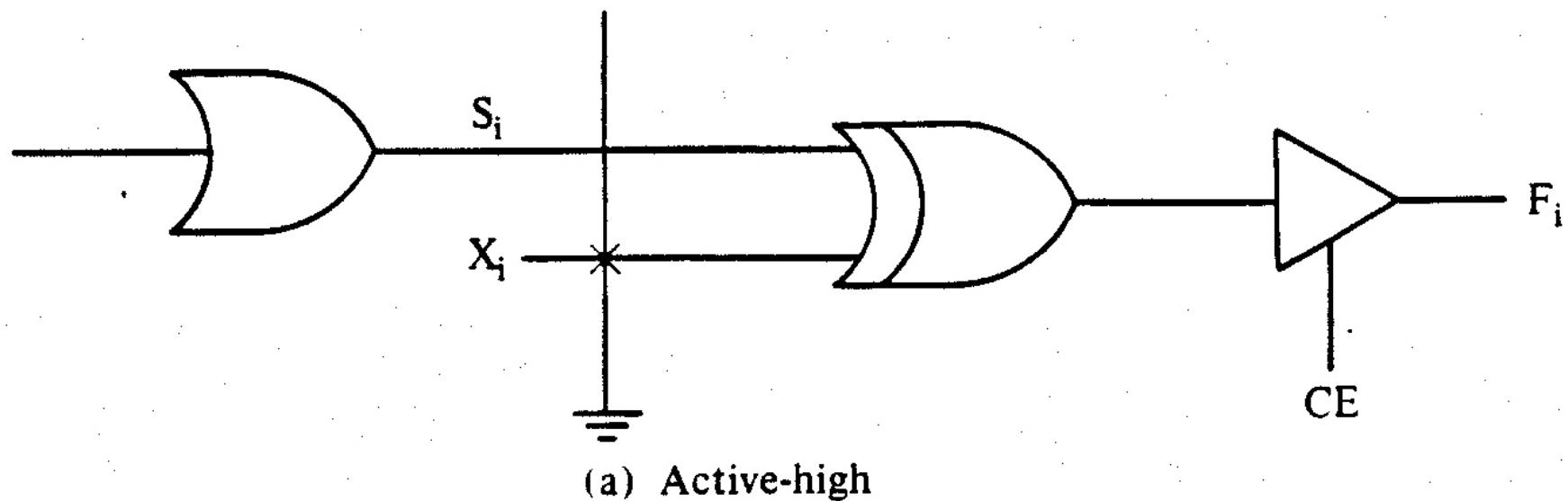


Figure 6.15 Programming the polarity of an FPLA output terminal.



 


Figure 6.16 PAL14H4 realization of $Y = ABC + \bar{A}\bar{B} + \bar{A}BC$ and $Z = \bar{A}\bar{B} + \bar{A}BC + \bar{B}\bar{C}$ from Fig. 6.10(a) of Example 6.1.

 

$$Z = A \cdot \bar{A} \cdot B \cdot \bar{B} = 0$$

(a) All inputs are connected

 


(b) All inputs are disconnected and left floating high


Figure 6.17 PAL shorthand notation.

$$Z_0 = \bar{X}_1 \bar{X}_2 + \bar{X}_0 \bar{X}_1 X_2 \bar{X}_3 + \bar{X}_0 X_1 \bar{X}_2 X_3 + X_1 X_2 X_3 + X_0 \bar{X}_2 \bar{X}_3$$


$$Z_1 = X_0 \bar{X}_2 \bar{X}_3 + \bar{X}_0 X_1 \bar{X}_2 X_3 + X_0 \bar{X}_1 X_2 X_3 + \bar{X}_0 \bar{X}_1 X_2 \bar{X}_3 + X_1 X_2 \bar{X}_3$$

Figure 6.18 PAL16L8 realization of Example 6.3.

 

 

 (a) PAL I/O terminal programmed as an input



(b) PAL I/O terminal programmed as an output

Figure 6.19 Programming of an I/O terminal of a PAL.

 


Figure 6.20 Logic diagram of the PAL16R4.