 


Flip-Flop Creation

Un gated SR



* Design Requirement: $Q \neq \bar{Q}$ always!

① Start w/initial condition
 $Q=0, \bar{Q}=1$
 $S=0, R=0$

- trace through circuit
 you'll notice there is
 no change in $Q \neq \bar{Q}$

①A change $S=1, R=0$
 stabilizes to $Q=1, \bar{Q}=0$

①B change $R=1, S=0$
 stabilizes to $Q=0, \bar{Q}=1$

①C change $S=1, R=1$
 stabilizes to $Q=0, \bar{Q}=0$
 * violates original design
 requirement

① Start initially w/conditions
 $Q=1, \bar{Q}=0$
 $S=0, R=0$
 - trace and you find no change
 in $Q \neq \bar{Q}$

①A change $S=1, R=0$
 stabilizes to $Q=1, \bar{Q}=0$

①B change $R=1, S=0$
 stabilizes to $Q=0, \bar{Q}=1$

①C change $R=1, S=1$
 get $Q=0, \bar{Q}=0$
 * also violates original design
 requirement



SR Characteristic Table

S	R	Q	Q ⁺
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	Not Allowed
1	1	1	Not Allowed


Condensed

S	R	Q ⁺
0	0	Q hold
0	1	0 reset
1	0	1 set
1	1	Not allowed


Gated SR Flip-Flop

  

creat
simple
gated block

 

 Edge Triggered SR F/F out of (2) SR Blocks & inverter on CLK to one of them



① Let $Q=0, \bar{Q}=1$ initially

② Let $S=1$ & $R=0$

- when CLK is low

$S=1, R=0$
passes through SR #1
and set intermediate $Q_I=1$ & $\bar{Q}_I=0$

- when CLK goes high

SR #1 goes into "hold" mode

SR #2 passes Q_I & $\bar{Q}_I$
through such that $Q_{out}=1$
 $\bar{Q}_{out}=0$

Device
can only change
output ($Q_{out}, \bar{Q}_{out}$)
a short time
after CLK goes
high $\therefore$ rising
edge triggered
device.

F/F summary

Abbreviated JK
Next State Table
(also called characteristic
table)

JK	Q^+
00	Q (hold)
01	0 (Reset)
10	1 (set)
11	$\bar{Q}$ (toggle)

"JK - F/F"

Abbreviated Excitation
Table

Q	Q^+	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

Abbreviated Excitation
"D - F/F"

Q	Q^+	D
0	0	0
0	1	1
1	0	0
1	1	1

Abbreviated
Excitation

T - F/F

Q	Q^+	T
0	0	0
0	1	1
1	0	1
1	1	0

Abbreviated
Excitation
SR F/F

Q	Q^+	S	R
0	0	0	X
0	1	1	0
1	0	0	1
1	1	X	0

This table
format
is very useful
in generating
Next State Table
for counters & ASM.
*FUTURE PROBLEMS
TO COME

"Creating Flip Flops from other Flip Flops"

T F/F from a JK F/F?


① Look at char. table for each

J	K	Q^+
0	0	Q
0	1	0
1	0	1
1	1	$\bar{Q}$

→

T	Q^+
0	Q
1	$\bar{Q}$

 
- Notice the cases when $J=K=0 \neq J=K=1$
match the T char. table



D F/F from JK F/F?

JK	Q^+
00	Q
01	0 (clear)
10	1 (set)
11	$\bar{Q}$

D	Q^+
0	0 ← when $J=0, K=1$ (clear)
1	1 ← when $J=1, K=0$ (set)

 

D F/F from SR F/F?


SR	Q^+
00	Q
01	0
10	1
11	n/a

D	Q^+
0	0
1	1

— you try this one...?

How do we create a D F/F with a Run/HOLD signal from a JK F/F?

 - ① start w/char table of new device
‡ Draw block diagram



CLK	R/H	D	Q	Q^+	
↑	0	0	0	0	} Hold mode
↑	0	0	1	1	
↑	0	1	0	0	
↑	0	1	1	1	
↑	1	0	0	0	} Run Mode "Typical" D F/F
↑	1	0	1	0	
↑	1	1	0	1	
↑	1	1	1	1	

② Write char. Table for target F/F

JK	Q+
11	1
10	0
01	0
00	0

③ Write next state using target F/F information

R/H	D	Q	J	K	Q+
1	1	1	1	1	1
1	1	0	1	1	0
1	0	1	0	0	1
1	0	0	0	0	0
0	1	1	1	1	1
0	1	0	1	1	0
0	0	1	0	0	1
0	0	0	0	0	0


what combinations produce the correct $Q \rightarrow Q^+$ transition?

④ Find Equations for J & K inputs (K-maps)

D	Q	Q+
0	0	0
0	1	0
1	0	1
1	1	0

J	K	Q+
0	0	0
0	1	0
1	0	1
1	1	0

$\therefore Q$ is not needed

 

⑤ Final Circuit