

# "World Acclaimed" Wisconsin Bowling Ball Waxer Machine

Controller:


Inputs: Start.H (S)  
Gloss.H (G)

Outputs: Wax.H (W)  
Spin Ball.H (SB)  
HEAT.L (H)  
Buff.L (B)

## Assumptions:


- when the person puts in their quarters, start goes true
- start stays true for the entire process until the state machine returns to state 000.

## Possible Start Signal

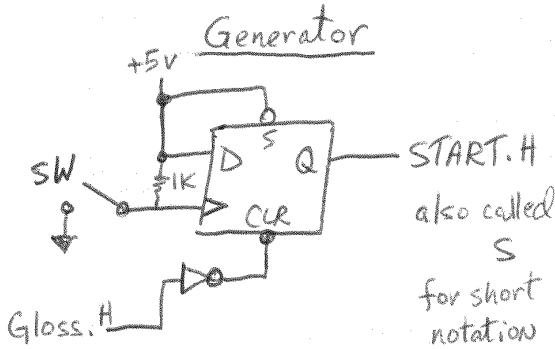


- SW is normally closed.
- put in your quarters and SW opens, sets START = H
- Gloss resets the START signal

## ASM Diagram

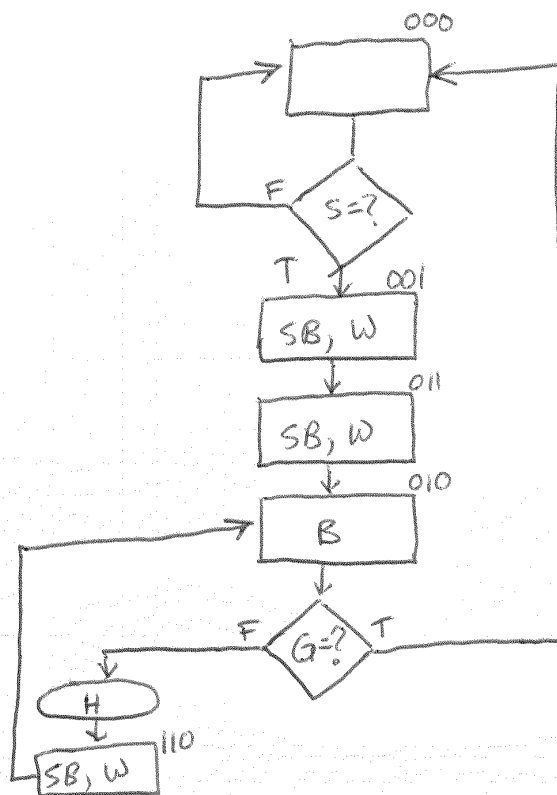

Procedure:

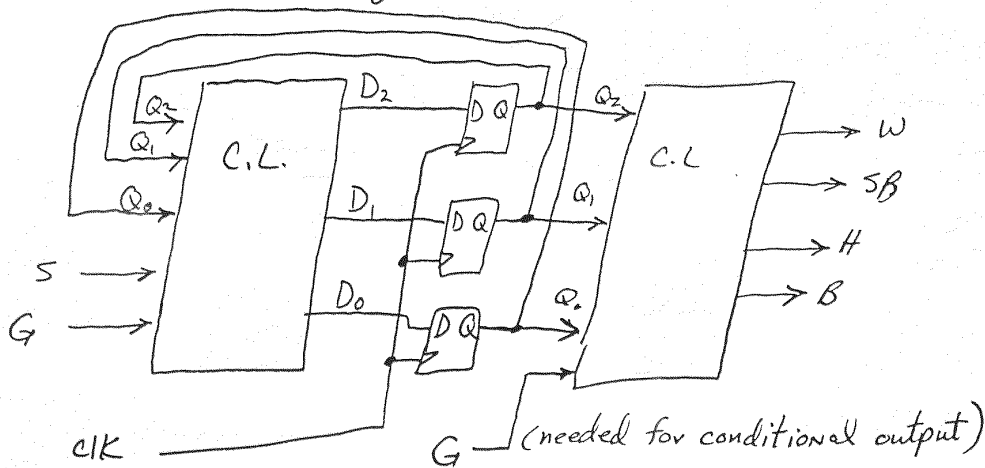- ① Determine ASM flow chart (given in this problem)
- ② Count states  $\Rightarrow 5$   
# compute # of F/Fs needed  $\Rightarrow 3$
- ③ Label states on ASM flow chart  
- try to label such that only one bit will change for each state transition... this will simplify the state variable equations
- ④ Functional Block Diagram & select F/F Type



⑤ Next State Table

(See next Page)

5)

inputs		Present State			Outputs				Next state			F/F inputs		
S	G	Q <sub>2</sub>	Q <sub>1</sub>	Q <sub>0</sub>	W	SB	H	B	Q <sub>2</sub> <sup>+</sup>	Q <sub>1</sub> <sup>+</sup>	Q <sub>0</sub> <sup>+</sup>	D <sub>2</sub>	D <sub>1</sub>	D <sub>0</sub>
0	X	X	X	X	0	0	0	0	0	0	0	0	0	0
1	0	0	0	0	0	0	0	0	0	0	1	0	0	1
1	0	0	0	1	1	1	0	0	0	1	1	0	1	1
1	0	0	1	0	0	0	1	1	1	1	0	1	1	0
1	0	0	1	1	1	1	0	0	0	1	0	0	1	0
1	0	1	0	0	X	X	X	X	X	X	X	X	X	X
1	0	1	0	1	X	X	X	X	X	X	X	X	X	X
1	0	1	1	0	1	1	0	0	0	1	0	0	1	0
1	0	1	1	1	X	X	X	X	X	X	X	X	X	X
1	1	0	0	0	0	0	0	0	0	0	1	0	0	1
1	1	0	0	1	1	1	0	0	0	0	1	0	0	1
1	1	0	1	0	0	0	0	1	0	0	0	0	0	0
1	1	0	1	1	1	1	0	0	0	1	0	0	1	0
1	1	1	0	0	X	X	X	X	X	X	X	X	X	X
1	1	1	0	1	X	X	X	X	X	X	X	X	X	X
1	1	1	1	0	1	1	0	0	0	1	0	0	1	0
1	1	1	1	1	X	X	X	X	X	X	X	X	X	X

### 6) Find State Variable Equations

- since  $S=T$  we count & when  $S=F$  we go to  $\phi$  & stay
- we can remove  $S$  from K-Maps and place in equations via inspection

$$\text{i.e. } D_2 = \left( \begin{array}{c} \text{equation} \\ \text{from K-Map} \end{array} \right) S$$

$$D_1 = \left( \text{from K-Map} \right) S$$

$$D_0 = \left( \text{from K-Map} \right) S$$

\* Also, if our F/Fs had a clear input signal (low true) we could connect  $S$  to this and remove from the equations.

"D<sub>2</sub>"

GQ <sub>2</sub>		00	01	11	10
Q <sub>1</sub> Q <sub>0</sub>	00	0	X	X	0
01	0	X	X	0	
11	0	X	X	0	
10	1	0	0	0	

$$D_2 = (\bar{G}\bar{Q}_2Q_1\bar{Q}_0)S$$

"D<sub>1</sub>"

GQ <sub>2</sub>		00	01	11	10
Q <sub>1</sub> Q <sub>0</sub>	00	0	X	X	0
01	1	X	X	0	
11	1	X	X	1	
10	1	1	1	0	

$$D_1 = (Q_2 + Q_1Q_0 + Q_0\bar{G} + Q_1\bar{G})S$$

check  
 $Q_2=0$   
 $Q_1=1$   
 $Q_0=0$   
 $G=1$  } should get 000 else get 110 when  $G=0$

"D<sub>0</sub>"

GQ <sub>2</sub>		00	01	11	10
Q <sub>1</sub> Q <sub>0</sub>	00	1	X	X	1
01	1	X	X	1	
11	0	X	X	0	
10	0	0	0	0	

$$D_0 = (\bar{Q}_1)S$$

7) Find Equations for output variables

- H is only true in state 010 when G=False (Conditional Output)

thus by inspection  $H = \bar{Q}_2 Q_1 \bar{Q}_0 \bar{G}$

W, SB & B are all unconditional outputs

and  $\therefore$  only dependent on  $Q_2, Q_1, \neq Q_0$

"W"

$Q_1, Q_0$		$Q_2$	
		0	1
00	0	X	
01	X	X	
11	1	X	
00	0	1	

$$W = Q_2 + Q_0$$

↑ check in ASM flow chart

"SB"

$Q_1, Q_0$		$Q_2$	
		0	1
00	0	X	
01	1	X	
11	1	X	
10	0	1	

$$SB = Q_2 + Q_0$$

B

$Q_1, Q_0$		$Q_2$	
		0	1
00	0	X	
01	0	X	
11	0	X	
10	1	0	

$$B = \bar{Q}_2 Q_1 \bar{Q}_0$$

↑ also you can get this by inspection

8A Physical Implementation w/ Gates

State Eq.  $D_2 = \bar{Q}_2 Q_1 \bar{Q}_0 \bar{G} S$ ,  $D_1 = S Q_2 + S Q_1 Q_0 + S Q_0 \bar{G} + S Q_1 \bar{G}$

$D_0 = \bar{Q}_1 S$






These ARE Logic Equations!

Outputs




$H = \bar{Q}_2 Q_1 \bar{Q}_0 \bar{G}$ ,  $W = Q_2 + Q_0$ ,  $SB = Q_2 + Q_0$ ,  $B = \bar{Q}_2 Q_1 \bar{Q}_0$

Circuitry

State Generator

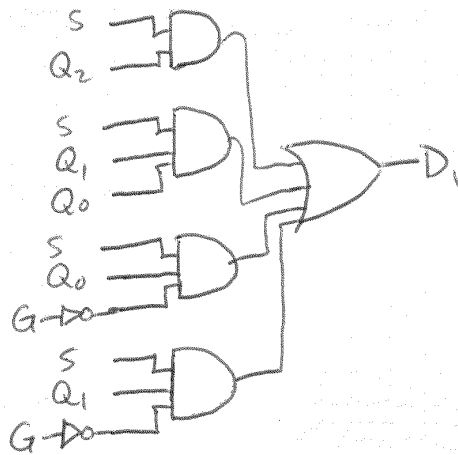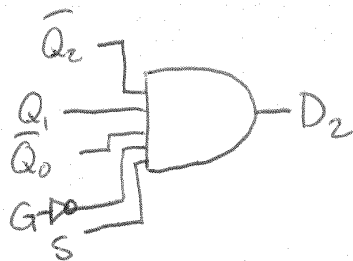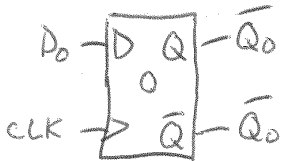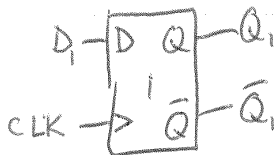
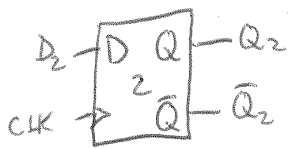


Output Generation

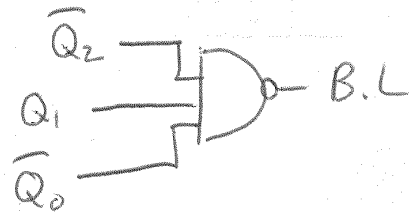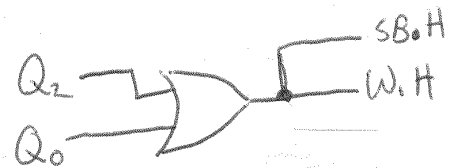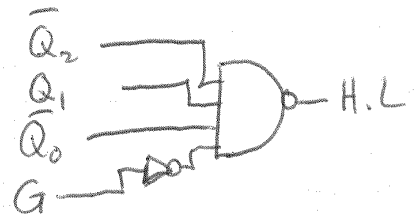
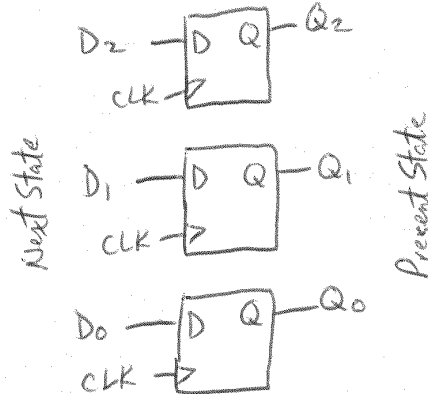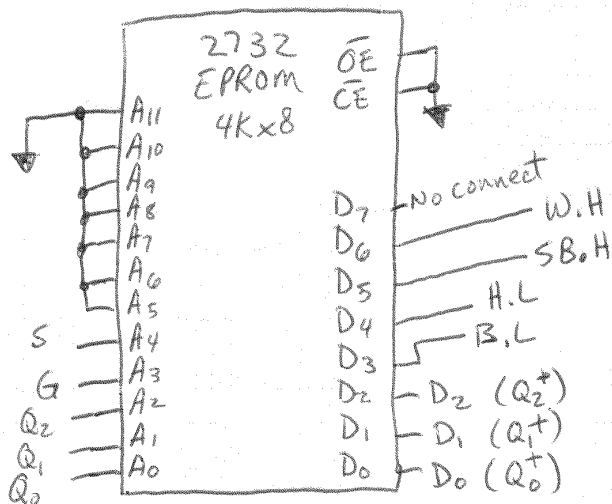
# 8B Physical Implementation w/ EPROM

Flip Flops synchronize the events to a clock (they are still needed!)



Note: we don't need  $\bar{Q}$  in F/F now

## Memory Contents

read straight out of Next State Table

Address		DATA								Actual Voltage to be Programmed						
Hex Value	BINARY	Logic								Hex Data Programmed						
	SG Q <sub>2</sub> Q <sub>1</sub> Q <sub>0</sub>	D <sub>6</sub> W	D <sub>5</sub> SB	D <sub>4</sub> H	D <sub>3</sub> B	D <sub>2</sub> D <sub>2</sub>	D <sub>1</sub> D <sub>1</sub>	D <sub>0</sub> D <sub>0</sub>	D <sub>6</sub> W	D <sub>5</sub> SB	D <sub>4</sub> H	D <sub>3</sub> B	D <sub>2</sub> D <sub>2</sub>	D <sub>1</sub> D <sub>1</sub>	D <sub>0</sub> D <sub>0</sub>	Hex Data Programmed
0	00000	0	0	0	0	0	0	0	L	L	H	H	L	L	L	18
1	00001	0	0	0	0	0	0	0	L	L	H	H	L	L	L	18
...	...	...	...	...	...	...	...	...	...	...	...	...	...	...	...	...
OF	01111	0	0	0	0	0	0	0	L	L	H	H	L	L	L	18
10	10000	0	0	0	0	0	0	1	L	L	H	H	L	L	H	19
11	10001	1	1	0	0	0	1	1	H	H	H	H	L	H	H	7B
12	10010	0	0	1	1	1	1	0	L	L	L	L	H	H	L	06
13	10011	1	1	0	0	0	1	0	H	H	H	H	L	H	L	7A
14	10100	X	X	X	X	X	X	X	L	L	L	L	L	L	L	00
15	10101	X	X	X	X	X	X	X	L	L	L	L	L	L	L	00
16	10110	1	1	0	0	0	1	0	H	H	H	H	L	H	L	7A
17	10111	X	X	X	X	X	X	X	L	L	L	L	L	L	L	00
18	11000	0	0	0	0	0	0	1	L	L	H	H	L	L	H	19
19	11001	1	1	0	0	0	0	1	H	H	H	H	L	L	H	79
1A	11010	0	0	0	1	0	0	0	L	L	H	L	L	L	L	10
1B	11011	1	1	0	0	0	1	0	H	H	H	H	L	H	L	7A
1C	11100	X	X	X	X	X	X	X	L	L	L	L	L	L	L	00
1D	11101	X	X	X	X	X	X	X	L	L	L	L	L	L	L	00
1E	11110	1	1	0	0	0	1	0	H	H	H	H	H	H	L	7E
1F	11111	X	X	X	X	X	X	X	L	L	L	L	L	L	L	00

Note: X will be programmed "L"

The end!