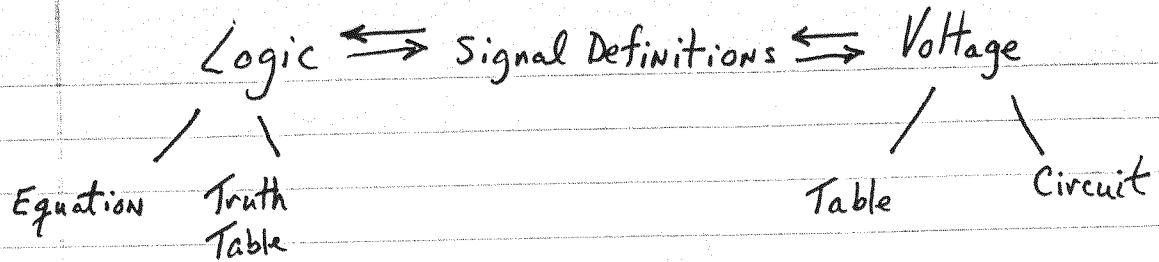


Note from **Dr. Schwartz**: Many things in this document are **NOT** the way that our class does mixed logic. Ask me if you are not sure.



Given: $y = \overline{AB} + C$

Logic Equation w/ A.L, B.H, C.H, Y.L
signal definition

① Write the Logic Truth Table?

A	B	C	y
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	0

② Write the Voltage Table?

A.L	B.H	C.H	Y.L
H	L	L	H
H	L	H	H
H	H	L	H
H	H	H	H
L	L	L	H
L	L	H	H
L	H	L	L
L	H	H	H

③ Implement the Circuit using NAND gates only?

3a) Positive Logic Method

I. Draw the Logic Equation using ANDs & OR Gates.

II. Add inverters for complements in the Logic Equation


III. Add inverters for low true input and output signals.

IV. Simplify using existing hardware.

I.
$$Y = \overline{AB} + C$$




II.

 

Note from Dr. Schwartz: All inputs and outputs should have labeled activation levels.


III. $A.L, B.H, C.H, Y.L$
* * *

 

Nands Only

IV. $\neg = \neg$


$\vee = \vee$

 

(36) Mixed Logic Method

I. Draw with selected gate in "AND" or "OR" configuration as needed.

i.e. selected gate = NAND

 

II. Look for mismatches in the circuit.
Mismatches should correspond to complements in the logic equation.


III. Add inverters to remove or add mismatches such that the existing mismatches all correspond to complements in the logic equations.

List of Mismatches


- (a) active low input signal connected to active high input wire
- (b) active high input signal connected to active low (bubble) wire
- (c) active high output wire connected to an active low output signal
- (d) active low output wire connected to an active high output signal

36) Mixed Logic Method (continued)

I. $y = \overline{\overline{AB} + C}$

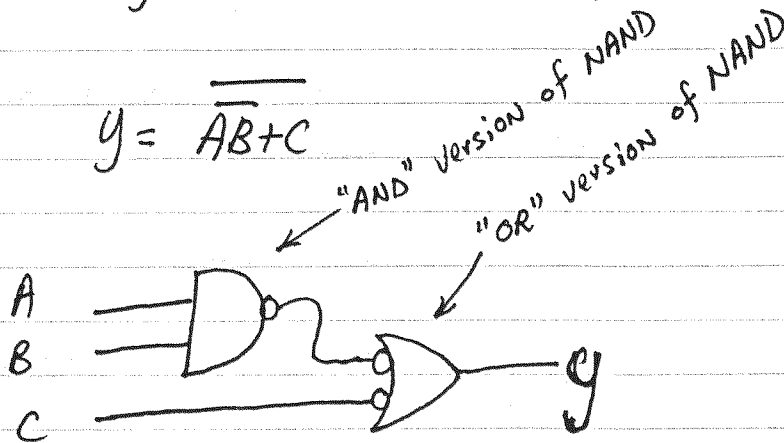

II. Look for mismatches

 


- we only want mismatches for $\overline{\overline{AB} + C}$

- mismatch #1 & #2 are not desired and should be removed with inverters

- mismatch #3 is $\overline{\overline{AB} + C}$ so this is okay
 also,
 - need to create mismatch

 III. Fixing Bad Mismatches & Creating one needed mismatch



- above circuit is complete but you should show:



$$\neg \triangleright = \neg \triangleright \neg = \neg \square$$

$$\triangleright \triangleright = \square$$


Extra Practice : Draw the circuit for L.E. $y = \overline{A} \overline{B} C + D$

using NORs w/y.L, A.H, B.H, C.H, D.L signal definiti:

Positive Logic Method

  


III. y.L, D.L

 

 IV. NOR $\overline{A} \overline{B} C = \overline{A \vee B} \vee C$, AND $\overline{A} \overline{B} C = \overline{A \vee B} \vee C$



Note from Dr. Schwartz: All inputs and outputs should have labeled activation levels.




Final Circuit

Mixed Logic "OR" style "AND" style

I. $\overline{A} \overline{B} C = \overline{A \vee B} \vee C$

II. *1-5 are mismatches!

 


*1 = bad, must remove *4 = Bad, rem
*2 = bad, must remove *5 = Bad, rem
*3 = okay, \overline{B}

— also, add mismatch

Note from Dr. Schwartz: All inputs and outputs should have labeled activation levels.

for $\overline{A} \overline{B} C$

Final Circuit III.

 

where, $\overline{A} \overline{B} C = \overline{A \vee B} \vee C$