

Exam 1

Last Name, First Name

[6%] 1. Do the following arithmetic problems. **Remember to show ALL work here and in EVERY problem on this exam.**

(2%) a) Determine the unsigned binary, octal, hexadecimal, and BCD representations of the number 99_{10} .

$$\begin{array}{r}
 2 \overline{) 99} \\
 \underline{2 \ 49} \quad 1 \\
 2 \overline{) 24} \quad 1 \\
 \underline{2 \ 12} \quad 0 \\
 2 \overline{) 6} \quad 0 \\
 \underline{2 \ 3} \quad 0 \\
 \underline{1} \quad 1 \\
 0 \quad 1
 \end{array}$$

Binary: 1100011
 Octal: 143
 Hex: 63
 BCD: 1001_A1001

(2%) b) Determine the **8-bit** signed magnitude, 1's complement, and 2's complement representations of the decimal number -19_{10} .

$$\begin{array}{r}
 2 \overline{) 19} \\
 \underline{2 \ 9} \quad 1 \\
 2 \overline{) 4} \quad 1 \\
 \underline{2 \ 2} \quad 0 \\
 \underline{2 \ 1} \quad 0 \\
 0 \quad 1
 \end{array}$$

Signed Mag: 1001_A0011
 1's Comp: 1110_A1100
 2's Comp: 1110_A1101

8 Bit binary
00010011

(2%) c) What is $99_{10} - 100_{10}$ in 8-bit 2's complement? Remember that you must **show all work**.

$$\begin{array}{r}
 99 \\
 -100 \\
 \hline
 -1
 \end{array}
 \qquad
 \begin{array}{r}
 0110,0011 (+99) \\
 1001,1100 (-100) \\
 \hline
 1111,1111
 \end{array}$$


$(99_{10} - 100_{10})_2$: 1111_A1111

binary $100_{10} = 0110,0100$
 - 1's comp(-100) = 1001,1011
 2's comp(-100) = 1001,1100₂

Exam 1

 Last Name, First Name

 [14%] 2. You are given the following new MSI device:





Inputs: E.L, A.H, B.H, C.H

Outputs: Y1.L, Y0.L

We would like to implement the following logic table:

E	A	B	C	Y1	Y0
0	X	X	X	0	0
1	0	0	0	1	1
1	0	0	1	1	0
1	0	1	0	1	1
1	0	1	1	1	0
1	1	0	0	0	1
1	1	0	1	0	0
1	1	1	0	0	1
1	1	1	1	0	0

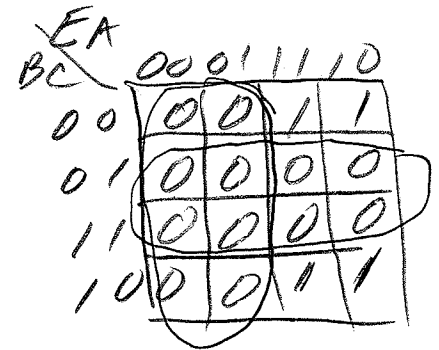 


(a) What are the logic equations for Y1 and Y0? Y1 should be in MSOP and Y0 MPOS.

Y1 (MSOP) = $E \cdot \bar{A}$ (4%)

Y0 (MPOS) = $E + \bar{C}$ (4%)

(b) Draw the mixed-logic circuit diagram required to implement the logic equations for Y0 (you don't have to implement Y1). Use minimum number of gates. (6%)

Use only NAND gates (and their alternative views).

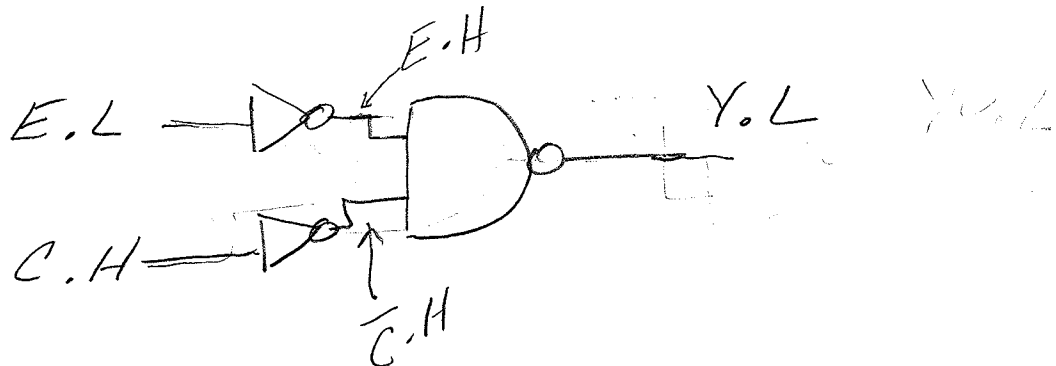

Exam 1

 Last Name, First Name

[12%] 3. Using any technique you desire, simplify the following equation. Give the result as a minimum product of sums (MPOS). **Show all work!**

$$Z = \overline{(A+B+C)} \cdot (A+C) + \bar{A} \cdot B \cdot (\bar{C} + C \cdot \bar{D})$$

$$= (\bar{A} \cdot \bar{B} \cdot \bar{C}) + (\bar{A} \cdot C) + \bar{A} \cdot B \cdot \bar{C} + \bar{A} \cdot B \cdot C \cdot \bar{D}$$

D is "don't care"
 1010
 1011

D is "don't care"
 0110
 0100
 0101

B D "don't care"
 0010
 0011
 0110
 0111

		A B					
		00	01	11	10		
C D	00	0	1	0	0		
	01	0	1	0	0		
11	1	1	0	1			
10	1	1	0	1			


$$Z_{MPOS} = (\bar{A} + \bar{B}) \cdot (B + C)$$

Exam 1

 Last Name, First Name

[12%] 4. Use the given 4-input multiplexers to solve each of the below problems. Choose a single activation level (either active high or active low) for each of the inputs and outputs for each problem. Use the minimum number of additional components. Show all work and draw any required mixed logic circuit diagrams (i.e., equations must not be used as replacements for circuit diagrams).


(4%) a) $Z_0 = A*B + A*C*/D$

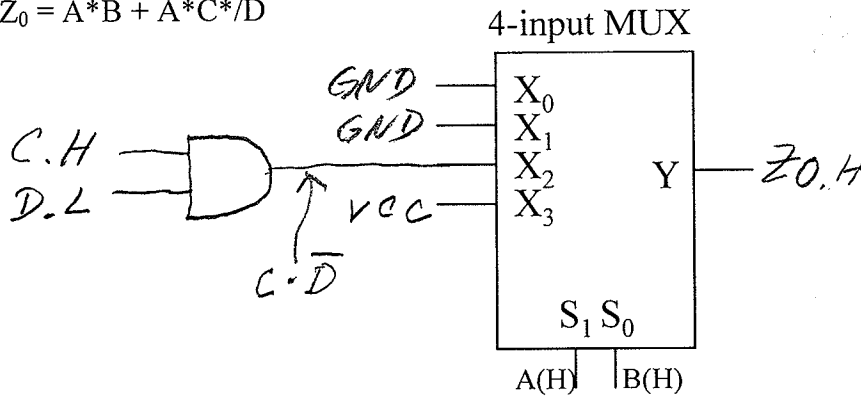

A	B	C	D	Z
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	0
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1

Handwritten annotations: $AB=00$ for first four rows, $AB=01$ for next four rows, $AB=10$ for next four rows, and $A=11$ for last four rows.

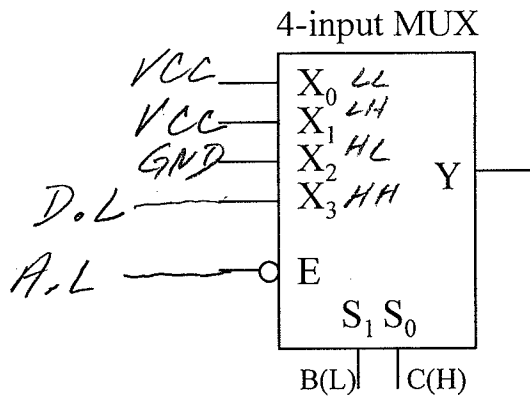
(4%) b) $Z_1 = A*B + A*C*/D$ (Notice the enable available on this MUX.)



Voltagetabelle for A.L=L

B	C	D	Z
H	L	H	L
H	L	L	L
H	H	H	H
H	H	L	L
L	L	H	H
L	L	L	H
L	H	H	H
L	H	L	H

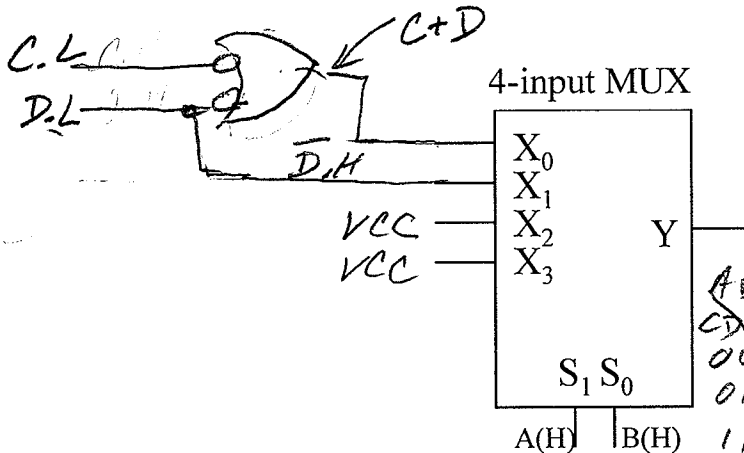(4%) c) Use the given 4-input multiplexer to implement Z_2 , which is defined by the voltage table.



AB	C	D	Z
00	0	1	1
00	1	1	1
01	1	0	1
01	0	1	1
11	0	0	1
11	0	1	1
10	1	1	1


A	B	C	D	Z ₂
L	L	L	L	L
L	L	L	H	H
L	L	H	L	H
L	L	H	H	H
L	H	L	L	H
L	H	L	H	L
L	H	H	L	H
L	H	H	H	L
H	L	L	L	H
H	L	L	H	H
H	L	H	L	H
H	L	H	H	H
H	H	L	L	H
H	H	L	H	H
H	H	H	L	H
H	H	H	H	H

Handwritten annotations: $AB=00$ for first four rows, $AB=01$ for next four rows, $AB=10$ for next four rows, and $AB=11$ for last four rows.

Exam 1

Last Name, First Name

 - [8%] 5. Determine the equation **directly** implemented with this mixed-logic circuit. Do **not** minimize the equation. It is **not** necessary to put the equation in lexical order. For partial credit, label the intermediate equations at the input to each gate.




$$F = \overline{(A \cdot B + C \cdot D \cdot E) \cdot (A \cdot C + B)} + \overline{A \cdot B}$$

Exam 1

 Last Name, First Name

 [8%] 6 Analyze the following circuit and produce a logic expression for **Z2**.



- For this problem, the expression for **Z2** should be in minimum SOP (MSOP) form.
- **Z2** should be a function of P, Q, and R.
- For credit, show all work.


$$\begin{aligned}
 \mathbf{Z2} &= E(\overline{A2} \cdot A1 \cdot \overline{A0} + A2 \cdot \overline{A1} \cdot \overline{A0} + A2 \cdot A1 \cdot \overline{A0}) \\
 &= R(\overline{P} \cdot Q \cdot Q + P \cdot \overline{Q} \cdot Q + P \cdot Q \cdot Q) \\
 &= R(\overline{P} \cdot Q + P \cdot Q) \\
 &= RQ(\overline{P} + P) = RQ
 \end{aligned}$$

Exam 1

Last Name, First Name

[12%] 7. MUX, logic vs. voltage.

 Show below is a block diagram of a “custom-built” 4-input MUX, with a mixture of active high and active low inputs and output.



(a) Give the logic equation for Y. (2 pts.)

$$Y = E \cdot (\overline{S1} \cdot \overline{S0} \cdot D0 + \overline{S1} \cdot S0 \cdot D1 + S1 \cdot \overline{S0} \cdot D2 + S1 \cdot S0 \cdot D3)$$

(b) Give the voltage table for the MUX. For maximum credit: (8 pts.)

- Order the voltage table in the “standard” order (E,S1,S0,D0,D1,D2,D3).
- Use “wild cards” or “don’t cares” to condense the table.

*CODE
EQUIVALENT
FOR
S1, S0*

	E	S1	S0	D0	D1	D2	D3	Y
01	L	X	X	X	X	X	X	H
01	H	L	L	X	L	X	X	L
00	H	L	L	X	H	X	X	H
00	H	L	L	X	H	X	X	H
11	H	L	H	L	X	X	X	H
11	H	L	H	L	X	X	X	L
10	H	H	L	X	X	L	X	H
10	H	H	L	X	X	H	X	L

(c) Visualize the logic equation of a 64-to-1 MUX. Give me the first 2 product terms of that equation and the last 2 product terms of that equation. (2 pts.)

First two product terms:

$$E \cdot \overline{S5} \cdot \overline{S4} \cdot \overline{S3} \cdot \overline{S2} \cdot \overline{S1} \cdot \overline{S0} \cdot D0 + E \cdot \overline{S5} \cdot \overline{S4} \cdot \overline{S3} \cdot \overline{S2} \cdot \overline{S1} \cdot S0 \cdot D1$$


Last two product terms:

$$E \cdot \overline{S5} \cdot \overline{S4} \cdot \overline{S3} \cdot \overline{S2} \cdot \overline{S1} \cdot S0 \cdot D2 + E \cdot \overline{S5} \cdot \overline{S4} \cdot \overline{S3} \cdot \overline{S2} \cdot S1 \cdot S0 \cdot D3$$


Exam 1

 Last Name, First Name

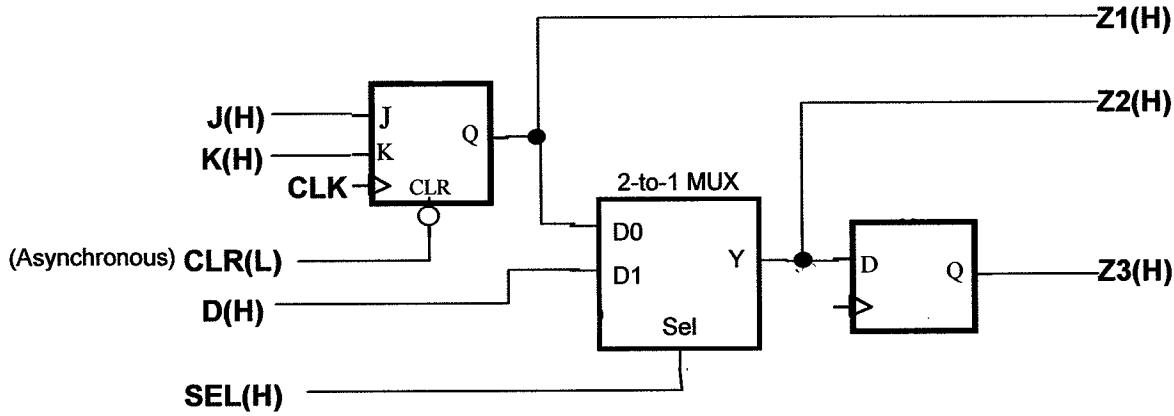[18%] 8. Circuit analysis and flip-flops.



 Given the above circuit, complete the following voltage timing diagrams.




(Note that CLR is an asynchronous clear input.)

Show propagation delays and go as far as you can.

Exam 1


 Last Name, First Name

 [10%] 9. Building switch and LED circuits.



Given the above circuit, implement the circuit on the “board” below using the given components. In other words, pretend that you are actually “wiring” your board in the lab and draw in the “wires”

 - Make all the necessary connections, including all VCC and GND connections.
- For ease of grading, use only the top 2 NAND gates.
- Be sure to draw each switch in the position (i.e., open or close) for which the switch produce a “True” value.



Laws and Theorems of Boolean Algebra

Exam 1

Last Name, First Name

Operations with 0 and 1:

1. $X + 0 = X$
2. $X + 1 = 1$

- 1D. $X \cdot 1 = X$
- 2D. $X \cdot 0 = 0$

Idempotent laws:

3. $X + X = X$

- 3D. $X \cdot X = X$

Involution laws:

4. $(X')' = X$

Laws of complementarity:

5. $X + X' = 1$

- 5D. $X \cdot X' = 0$

Commutative laws:

6. $X + Y = Y + X$

- 6D. $XY = YX$

Associative laws:

7. $(X + Y) + Z = X + (Y + Z) = X + Y + Z$

- 7D. $(XY)Z = X(YZ) = XYZ$

Distributive laws:

8. $X(Y + Z) = XY + XZ$

- 8D. $X + YZ = (X + Y)(X + Z)$

Simplification theorems:

9. $XY + XY' = X$
10. $X + XY = X$
11. $(X + Y')Y = XY$

- 9D. $(X + Y)(X + Y') = X$
- 10D. $X(X + Y) = X$
- 11D. $XY' + Y = X + Y$

DeMorgan's laws:

12. $(X + Y + Z + \dots)' = X'Y'Z'$

- 12D. $(XYZ\dots)' = X' + Y' + Z'$

13. $[f(A, B, \dots, Z, 0, 1, +, \bullet)]' = f(A', B', \dots, Z', 1, 0, \bullet, +)$

Duality:

14. $(X + Y + Z + \dots)^D = XYZ\dots$

- 14D. $(XYZ\dots)^D = X + Y + Z + \dots$

15. $[f(A, B, \dots, Z, 0, 1, +, \bullet)]^D = f(A, B, \dots, Z, 1, 0, \bullet, +)$

Theorems for multiplying out and factoring:

16. $(X + Y)(X' + Z) = XZ + X'Y$

- 16D. $XY + X'Z = (X + Z)(X' + Y)$

Consensus theorems:

17. $XY + YZ + X'Z = XY + X'Z$

- 17D. $(X + Y)(Y + Z)(X' + Z) = (X + Y)(X' + Z)$