



# Exam 1

\_\_\_\_\_

Last Name, First Name

[6%] 1. Do the following arithmetic problems. **Remember to show ALL work here and in EVERY problem on this exam.**

(2%) a) Determine the unsigned binary, octal, hexadecimal, and BCD representations of the number  $99_{10}$ .

Binary: \_\_\_\_\_

Octal: \_\_\_\_\_

Hex: \_\_\_\_\_

BCD: \_\_\_\_\_

(2%) b) Determine the **8-bit** signed magnitude, 1's complement, and 2's complement representations of the decimal number  $-19_{10}$ .

Signed Mag: \_\_\_\_\_

1's Comp: \_\_\_\_\_

2's Comp: \_\_\_\_\_


(2%) c) What is  $99_{10} - 100_{10}$  in 8-bit 2's complement? Remember that you must **show all work.**

$(99_{10} - 100_{10})_2$ : \_\_\_\_\_
 
# Exam 1

\_\_\_\_\_  
 Last Name, First Name

[14%] 2. You are given the following new MSI device:



**Inputs:** E.L, A.H, B.H, C.H

**Outputs:** Y1.L, Y0.L

We would like to implement the following logic table:

E	A	B	C	Y1	Y0
0	X	X	X	0	0
1	0	0	0	1	1
1	0	0	1	1	0
1	0	1	0	1	1
1	0	1	1	1	0
1	1	0	0	0	1
1	1	0	1	0	0
1	1	1	0	0	1
1	1	1	1	0	0

(a) What are the logic equations for Y1 and Y0? Y1 should be in MSOP and Y0 MPOS.

Y1 (MSOP) = \_\_\_\_\_ (4%)

Y0 (MPOS) = \_\_\_\_\_ (4%)

(b) Draw the mixed-logic circuit diagram required to implement the logic equations for **Y0** (you don't have to implement Y1). Use minimum number of gates. (6%)

**Use only NAND gates (and their alternative views).**

## Exam 1

\_\_\_\_\_  
Last Name, First Name

- [12%] 3. Using any technique you desire, simplify the following equation. Give the result as a minimum product of sums (MPOS). **Show all work!**

$$Z = \overline{(\overline{A+B+C}) \cdot (A+\overline{C})} + \overline{A} \cdot B \cdot (\overline{C} + C \cdot \overline{D})$$


$Z_{\text{MPOS}} =$  \_\_\_\_\_

# Exam 1


\_\_\_\_\_  
 Last Name, First Name

[12%] 4. Use the given 4-input multiplexers to solve each of the below problems. Choose a single activation level (either active high or active low) for each of the inputs and outputs for each problem. Use the minimum number of additional components. Show all work and draw any required mixed logic circuit diagrams (i.e., equations must not be used as replacements for circuit diagrams).


(4%) a)  $Z_0 = A*B + A*C*/D$

 

 (4%) b)  $Z_1 = A*B + A*C*/D$  (Notice the enable available on this MUX.)



 (4%) c) Use the given 4-input multiplexer to implement  $Z_2$ , which is defined by the voltage table.




A	B	C	D	$Z_2$
L	L	L	L	L
L	L	L	H	H
L	L	H	L	H
L	L	H	H	H
L	H	L	L	H
L	H	L	H	L
L	H	H	L	H
L	H	H	H	L
H	L	L	L	H
H	L	L	H	H
H	L	H	L	H
H	L	H	H	H
H	H	L	L	H
H	H	L	H	H
H	H	H	L	H
H	H	H	H	H
 
# Exam 1

\_\_\_\_\_  
Last Name, First Name

- [8%] 5. Determine the equation **directly** implemented with this mixed-logic circuit. Do **not** minimize the equation. It is **not** necessary to put the equation in lexical order. For partial credit, label the intermediate equations at the input to each gate.




F = \_\_\_\_\_
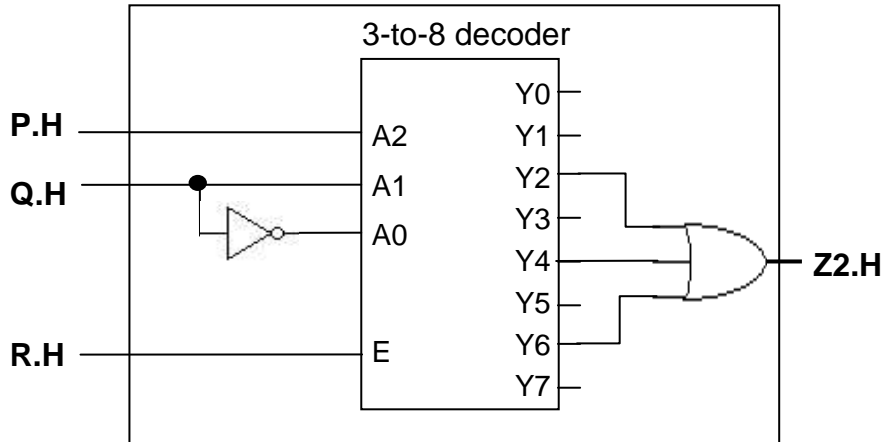
# Exam 1

\_\_\_\_\_  
Last Name, First Name

[8%] 6 Analyze the following circuit and produce a logic expression for **Z2**.



- For this problem, the expression for **Z2** should be in minimum SOP (MSOP) form.
- Z2 should be a function of P, Q, and R.
- For credit, show all work.


**Z2 =**

# Exam 1

\_\_\_\_\_  
Last Name, First Name

[12%] 7. MUX, logic vs. voltage.

 Show below is a block diagram of a “custom-built” 4-input MUX, with a mixture of active high and active low inputs and output.



(a) Give the logic equation for Y. (2 pts.)

(b) Give the voltage table for the MUX. For maximum credit: (8 pts.)

- Order the voltage table in the “standard” order (E,S1,S0,D0,D1,D2,D3).
- Use “wild cards” or “don’t cares” to condense the table.

(c) Visualize the logic equation of a 64-to-1 MUX. Give me the first 2 product terms of that equation and the last 2 product terms of that equation. (2 pts.)

First two product terms:


Last two product terms:



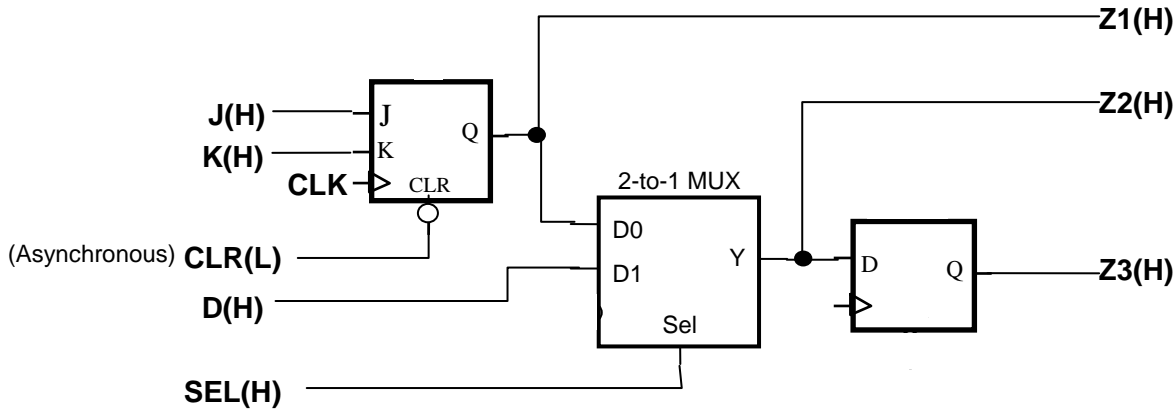
# Exam 1

\_\_\_\_\_  
 Last Name, First Name

[18%] 8. Circuit analysis and flip-flops.



 Given the above circuit, complete the following voltage timing diagrams.




(Note that CLR is an asynchronous clear input.)

Show propagation delays and go as far as you can.
 
# Exam 1


\_\_\_\_\_  
 Last Name, First Name

[10%] 9. Building switch and LED circuits.



Given the above circuit, implement the circuit on the “board” below using the given components. In other words, pretend that you are actually “wiring” your board in the lab and draw in the “wires”

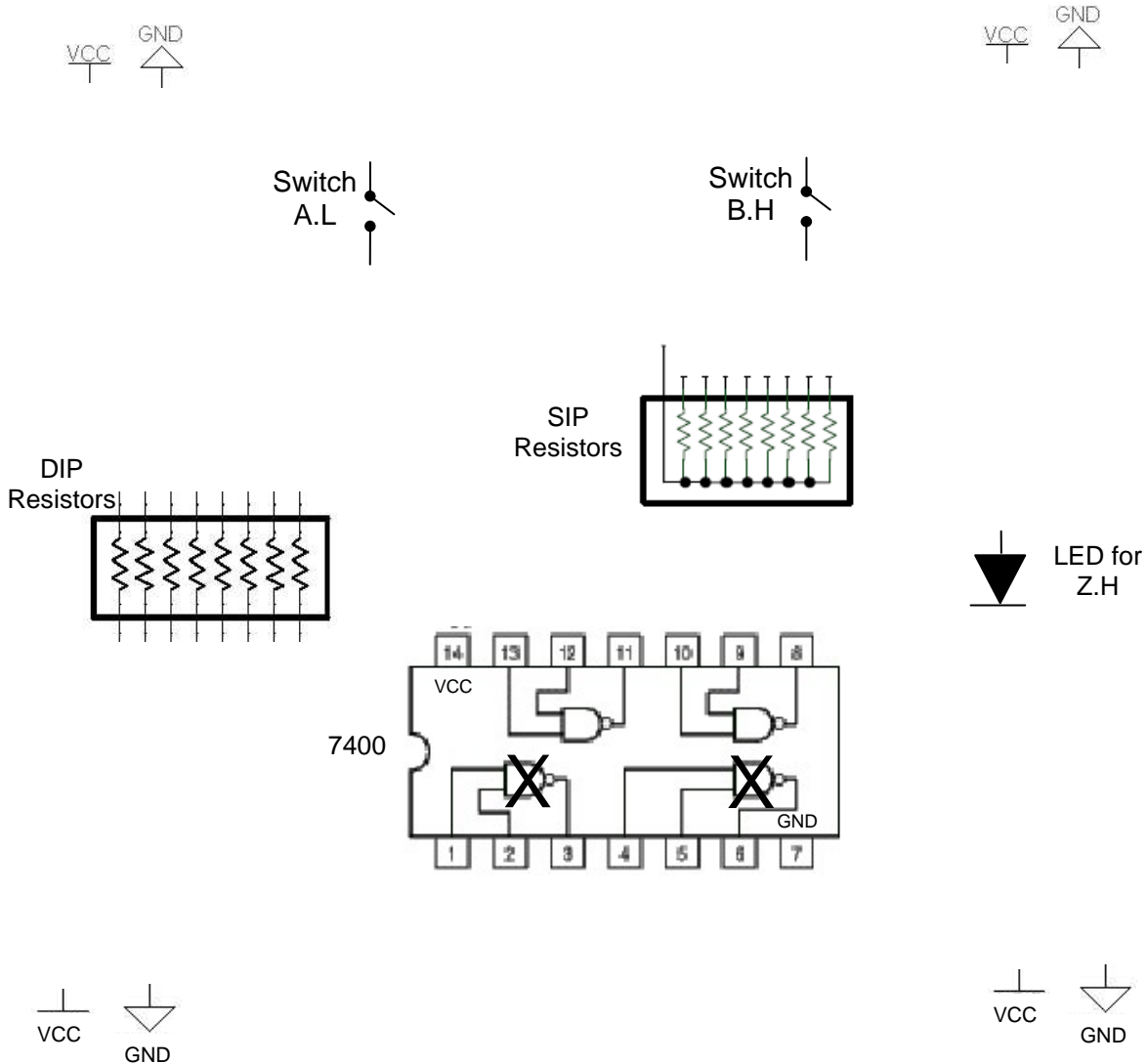- Make all the necessary connections, including all VCC and GND connections.
- For ease of grading, use only the top 2 NAND gates.
- Be sure to draw each switch in the position (i.e., open or close) for which the switch produce a “True” value.



## Exam 1

\_\_\_\_\_  
Last Name, First Name

### Laws and Theorems of Boolean Algebra

Operations with 0 and 1:

1.  $X + 0 = X$

2.  $X + 1 = 1$

1D.  $X \cdot 1 = X$

2D.  $X \cdot 0 = 0$

Idempotent laws:

3.  $X + X = X$

3D.  $X \cdot X = X$

Involution laws:

4.  $(X')' = X$

Laws of complementarity:

5.  $X + X' = 1$

5D.  $X \cdot X' = 0$

Commutative laws:

6.  $X + Y = Y + X$

6D.  $XY = YX$

Associative laws:

7.  $(X + Y) + Z = X + (Y + Z) = X + Y + Z$

7D.  $(XY)Z = X(YZ) = XYZ$

Distributive laws:

8.  $X(Y + Z) = XY + XZ$

8D.  $X + YZ = (X + Y)(X + Z)$

Simplification theorems:

9.  $XY + XY' = X$

9D.  $(X + Y)(X + Y') = X$

10.  $X + XY = X$

10D.  $X(X + Y) = X$

11.  $(X + Y')Y = XY$

11D.  $XY' + Y = X + Y$

DeMorgan's laws:

12.  $(X + Y + Z + \dots)' = X'Y'Z'$

12D.  $(XYZ\dots)' = X' + Y' + Z'$

13.  $[f(A, B, \dots, Z, 0, 1, +, \bullet)]' = f(A', B', \dots, Z', 1, 0, \bullet, +)$

Duality:

14.  $(X + Y + Z + \dots)^D = XYZ\dots$

14D.  $(XYZ\dots)^D = X + Y + Z + \dots$

15.  $[f(A, B, \dots, Z, 0, 1, +, \bullet)]^D = f(A, B, \dots, Z, 1, 0, \bullet, +)$

Theorems for multiplying out and factoring:

16.  $(X + Y)(X' + Z) = XZ + X'Y$

16D.  $XY + X'Z = (X + Z)(X' + Y)$

Consensus theorems:

17.  $XY + YZ + X'Z = XY + X'Z$

17D.  $(X + Y)(Y + Z)(X' + Z) = (X + Y)(X' + Z)$