


Remember to show **ALL** work here and in **EVERY** problem on this exam.



(10 pts.)

 1. Draw a mixed-logic circuit diagram (with the minimum number of gates) to **directly implement** the below equation. All inputs and the output can be of any activation-level desired. Be sure to **specify the desired activation levels**. Do **not** simplify this equation. You may **only use** gates available on 74HC10 chips (shown). Use as many 74HC10 chips as you need, but use the minimum number required to solve this problem.

$$\overline{\overline{A}} \overline{\overline{E}} (\overline{\overline{B}} + \overline{\overline{C}}) D = Y$$



2. Answer the following for the given next-state **truth (logic) table**. Y and Z are outputs and X is the only input.

(14 pts.)

X	Q ₂	Q ₁	Q ₀	Y	Z	Q ₂ ⁺	Q ₁ ⁺	Q ₀ ⁺
0	0	0	0	0	0	1	1	1
0	0	0	1	0	0	0	0	0
0	0	1	0	0	0	0	0	1
0	0	1	1	1	1	0	1	0
0	1	0	0	X	X	X	X	X
0	1	0	1	X	X	X	X	X
0	1	1	0	1	0	0	1	1
0	1	1	1	1	1	1	1	0
1	0	0	0	0	0	1	1	1
1	0	0	1	0	0	1	1	1
1	0	1	0	0	0	1	1	1
1	0	1	1	1	0	1	1	1
1	1	0	0	X	X	1	1	1
1	1	0	1	X	X	1	1	1
1	1	1	0	1	0	1	1	1
1	1	1	1	1	0	1	1	1

- a) What **kind** of output is Y; and what **type** is Z? Be specific.

Y: (1 pt.)


Z: (1 pt.)

2. (continue)

Design a circuit to implement the **truth table** from the previous page.

- Use only a ROM and D-FF's. Use **no** other SSI, MSI or LSI elements.
- The signals **X and Y are active-high** and **Z is active-low**.
- Use as little of the EEPROM as possible. List the ROM contents in order stating at address 0

 (b) Complete the following circuit by drawing in the appropriate number of D-FF's and show connections to **all** EEPROM signals. (4 pts.)



(c) List the ROM contents in order stating at address 0, with both address and data specified **in HEX**. Program Zeros for "Don't Cares" (8 pts.)

3. Hand Assembly & Program Analysis (Use the G-CPU information in the appendix)



Assume that you are given an 8Kx8 EPROM that has been erased completely. i.e. all memory contents are now \$FF.

(14 pts.)

Hand Assemble the following G-CPU program and show the contents of EPROM memory (Address & Data) that has been modified after the EPROM is programmed:

```

    ORG      $0080
T1   dc.b   $45
T2   dc.b   $88
T3   dc.b   %10101101
    ORG      $0
    LDAA     $81
    LDAB     T1
    OR_BA
    LDX     #$0180
TOP  STAA   $12,X
    BN      TOP
    
```

(a) EPROM Memory Programmed due to the above Data & G-CPU Code:

<u>Addr (Hex)</u>	<u>Data (Hex)</u>	<u>Addr (Hex)</u>	<u>Data (Hex)</u>	<u>Addr (Hex)</u>	<u>Data (Hex)</u>
_____	_____	_____	_____	_____	_____
_____	_____	_____	_____	_____	_____
_____	_____	_____	_____	_____	_____
_____	_____	_____	_____	_____	_____
_____	_____	_____	_____	_____	_____
_____	_____	_____	_____	_____	_____
_____	_____	_____	_____	_____	_____
_____	_____	_____	_____	_____	_____


(b) In the above program what is the effective address associated with the “STX T1” instruction?
 _____ Hex

(c) What is the effective address associated with the “LDX #\$0180” instruction?
 _____ Hex

(d) What is the effective address associated with the “STX \$12,X” instruction?
 _____ Hex

(e) What is the value of the A register the first time “STX \$12,X” is executed? Will the branch occur?
 A Register Contents = _____ Hex Branch will occur (circle one)? T or F

 4. Program Execution (Use the G-CPU information in the appendix)



Given the following program in EPROM memory, fill out the cycle table that follows:

(18 pts.)

<u>Addr</u>	<u>Data</u>
0	02
1	35
2	06
3	0A
4	00

Using the the G-CPU Controller ASM & Block Diagram (Appendix A handouts), complete the cycle table below:


<u>Cycle#</u>	<u>R/- W</u>	<u>PC (Hex)</u>	<u>MAR</u>	<u>A15:0 (Hex)</u>	<u>Data (Hex)</u>	<u>IR (Hex)</u>	<u>A (Hex)</u>	<u>AddrSel1:0</u>
1	1	0000	XXXX	0000	02	XX	XX	00
2								
3								
4								
5								
6								
7								
8								
9								
10								

5. Memory Maps, Memory Devices & Decoding



You are given as many of the following EPROM and SRAM devices that you need for the problem below:

(15 pts.)

 

If the processor is a GCPU with a 16 bit address bus (A15:0) and 8 bit data bus (D7:0), show the required **devices & decode circuitry** below to place an 8Kx8 EPROM starting **at 2000 Hex** and an 8Kx8 SRAM immediately following the EPROM in the system memory map.


Implement the 8Kx8 EPROM.
Show devices & connections
(below) =>

Implement the 8Kx8 SRAM.
Show devices & connections
(below) =>

Show EPROM Memory Decode
Circuit (below) =>

Show SRAM Decode Circuit
(below) =>

 6. GCPU Assembly Programming (Use the G-CPU instruction set in Appendix A)



(12 pts.)

Given the following constants in EPROM and SRAM Memory, write a program **to fill the first 128 memory locations in SRAM with zeros.**

Assumptions:

1. EPROM exists in the memory map from 0-FFF Hex.
2. SRAM exists in the memory map from 1000-1FFF Hex.
3. Your program should begin at address 0 in EPROM.
4. Write a program to zero out (clear) the first 128 locations in SRAM.



(17 pts.)

7. **Controller (ASM) design for the G-CPU. (Use the G-CPU block diagram and ASM charts in the appendix.)**

Using the signal names shown in controller G-GPU block diagram in the appendix, complete the ASM chart (on the next page) to implement the following 3 instructions (**SUM_BA**, **LDAB #data**, and **STAA \$addr**), including the completion of State A and State B.

Notes:

- (1) In each state and conditional output, specify **only the signals that should be true**.
- (2) However, you should use the notation: **MSA=01**, **MSB=10**, **MSC=000**.
- (3) When not specified, the default actions for each state is to “hold” **REGA and REGB** and **OUT = REGA**.

Important Hint: You should use the ASM charts provided in the appendix. Then, all you have to do is to determine what signals are supposed to be TRUE in each state.

<u>MSA1/MSB1</u>	<u>MSA0/MSB0</u>	
0	0	INPUT Bus
0	1	REGA Output Bus
1	0	REGB Output Bus
1	1	OUTPUT Bus

<u>MSC2:0 (Most Significant Bit is on the left)</u>
000 => REGA Bus to OUTPUT Bus
001 => REGB Bus to OUTPUT Bus
010 => bit wise AND REGA/REGB Bus to OUTPUT Bus
011 => bit wise OR REGA/REGB Bus to OUTPUT Bus
100 => complement of REGA Bus to OUTPUT Bus
101 => REGA Bus Plus REGB Bus Plus Cin to OUTPUT Bus & Cout (There is an external Cin and an external Cout for the ALU)
110 => shift REGA Bus left one bit to OUTPUT Bus (0 is shifted into OUTPUT Bus[0].)
111 => shift REGA Bus right one bit to OUTPUT Bus (0 is shifted into OUTPUT Bus[3].)

Put the solution on the next page.

8 (continued): Put solution here:

