


Remember to show **ALL** work here and in **EVERY** problem on this exam.

[10%] **1. Circuit Analysis**

What is the logic equation for X in the given circuit? Do **not** simplify or transform it into an SOP or POS form. Leave the logic expression as it is after analysis. Also, draw the **intermediate** expression at the **input** to **each** gate.

- Notation reminder: $A(H)$ is the same as $A.H$
- Boolean expression answers must be in **lexical order**, i.e., $/A$ before A , A before B , etc.


EQUATION: $X =$ _____

 


[10%] **2. Circuit Synthesis**

Draw a mixed-logic circuit diagram (with the minimum number of gates) to **directly implement** the below equation. All inputs and the output can be of any activation-level desired. Be sure to **specify the desired activation levels**. Do **not** simplify this equation. You may **only use** gates available on 74HC27 chips (shown). Use as many 74HC27 chips as you need, but use the minimum number required to solve this problem.
 
$$F = A * B * C + C * /D * /E + A * /B * D$$



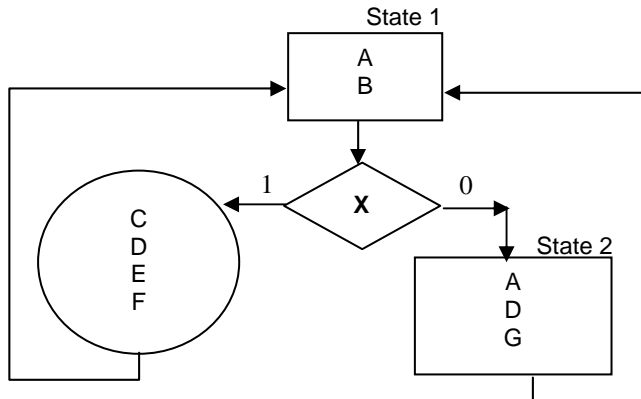[12%] **3. Implementation of an ASM chart using J-K flip-flops**




J-K characteristic table:


J	K	Q	Q+
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

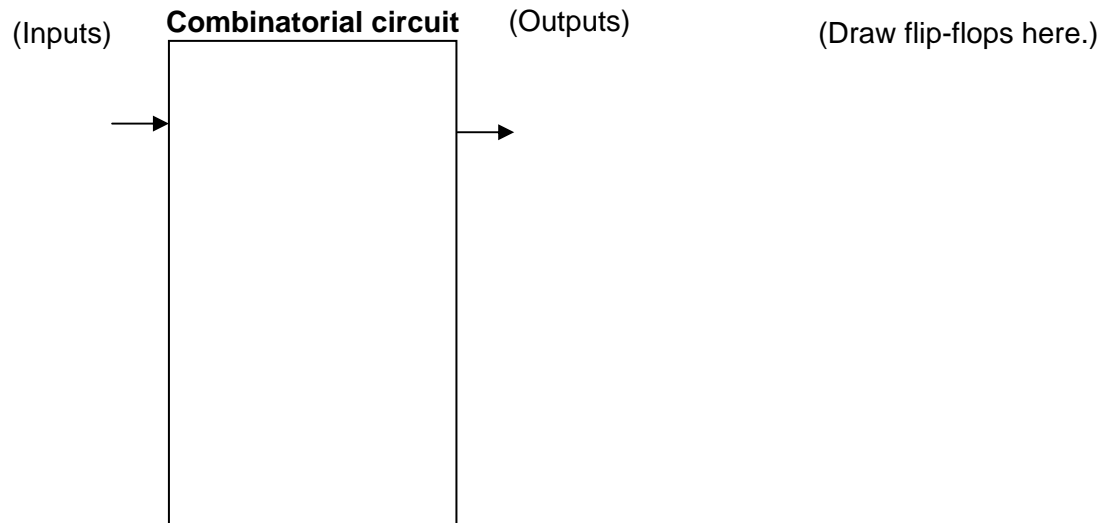(a) Given the above ASM chart, complete the following block diagram of its implementation using the minimum number of J-K flip-flops: (2%)

- Determine how many J-K flip-flops that are needed.
- Draw in all the inputs and outputs of the combinatorial circuit.
- Make all necessary connections to complete the block diagram (between the combinatorial circuit and the flip-flops).



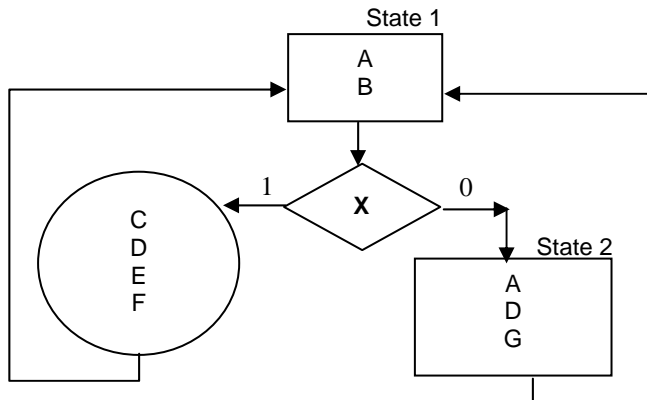3. (continued) (ASM chart is repeated here for your convenience/)



J-K characteristic table:

J	K	Q	Q+
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

(b) Finish the implementation of the ASM by determining the minimum sum-of-products (MSOP) logic expressions for the following signals: (10%)

J =

K =

A =

B =

C =

D =

E =

F =

G =

(If necessary, use the bottom/back of the previous page to do your work.)

[12%] 4. Given the following program segment, EQU statements, and contents of memory locations:

```

ORG      0
1  LDX   #$000C      Data0 EQU $0026
2  LDAA  #150;       Data1 EQU $0032
3  LDAB  #60;        Data2 EQU $0037
4  SUM_BA
5  "next instruction (a,b,c,d,e, or f)"
Data3 EQU $0038
Data4 EQU $0050
Data5 EQU $00EF
Data6 EQU $5000
Data7 EQU $73AB
Data8 EQU $73AC
    
```

Memory Locations	
Address	Content
\$0026	\$66
\$0032	\$BB
\$0037	\$74
\$0038	\$EC
\$0050	\$C3
\$00EF	\$AB
\$5000	\$3E
\$73AB	\$AA
\$73AC	\$E2

a) Assume the 4 instructions in the above program segment have already been executed and the "next instruction" (i.e., 5th. instruction) is **LDAA 50**. Hand-assemble the LDAA instruction and fill in the blanks (including EA and register A) using **HEX**.

Note: EA is the "effective address", the actual address in memory where the data is loaded from in a "load" instruction (like LDAA, LDX, etc), or where the data is stored in a "store" instruction (like STAA). If no memory is accessed, write "none" for EA.


<u>ADDRESS</u>	<u>INSTRUCTION</u>	<u>HEX ADDRESS</u>	<u>HEX VALUE</u>
\$0008	LDAA 50	_____	_____
EA = _____		_____	_____
A = _____		_____	_____
		_____	_____

Repeat the same problem **if** the "next instruction" is the instruction in "b", "c", "d", "e", or "f", again assuming instructions 1 through 4 have been executed.

b) \$0008	LDX Data7	_____	_____
EA = _____		_____	_____
X = _____		_____	_____
		_____	_____
c) \$0008	STAA 38,X	_____	_____
EA = _____		_____	_____
Value stored = _____		_____	_____
		_____	_____
d) \$0008	LDY #Data7	_____	_____
EA = _____		_____	_____
Y = _____		_____	_____
		_____	_____
e) \$0008	BN \$EF	_____	_____
EA = _____		_____	_____
PC after this instruction = _____		_____	_____
		_____	_____
f) \$0008	BEQ \$EF	_____	_____
EA = _____		_____	_____
PC after this instruction = _____		_____	_____
		_____	_____

[10%] **5. EEPROM and SRAM**

 You are given as many of the following EEPROM and SRAM devices that you need for the problem below:



You are to implement a 16Kx8 memory module, containing 8Kx8 SRAM, starting in location 0, followed immediately by 8Kx8 EEPROM.

The 16K X 8 memory module should have an “R/-W” input and a “-CE” input.

For ease of grading, draw the 8Kx8 SRAM circuit here (i.e., show the devices & connections):



Draw the 8Kx8 EEPROM circuit here (i.e., show the devices & connections):



[15%] **6. Program Execution** (Use the G-CPU information in the back of the test.)

Given the following program in EPROM memory, fill out the following cycle table that illustrates its execution:

<u>Addr</u>	<u>Data</u>
0	01
1	07
2	01
3	07

Using the the **G-CPU Controller ASM & Block Diagram (at the end of this test)**, complete the cycle table below. Use as many rows as you need.

<u>Cycle#</u>	<u>R/- W</u>	<u>Addr Sel1:0</u>	<u>PC (Hex)</u>	<u>MAR</u>	<u>A15:0 (Hex)</u>	<u>Data (Hex)</u>	<u>IR (Hex)</u>	<u>A (Hex)</u>	<u>B (Hex)</u>
1	1	00	0000	0400			06	32	16
2									
3									
4									
5									
6									
7									
8									
9									
10									

[15%] **7. GCPU Assembly Programming** (Use the G-CPU instruction set in back of this test.)

Write an assembly language program using **only** the G-CPU instructions

- There are \$25 bytes already stored in memory starting in Location \$1000
- Your program should go through the \$25 bytes and count the number of “non-zero” bytes (i.e., bytes that are not equal to \$00).
- At the end of the program, Memory Location \$0FFF should contain the count of non-zero bytes.
- To increase your chances of partial credit, comment your program.

Important restriction: You **have to use REGA** as the “loop counter”.

[16%] **8. Controller (ASM) design for the G-CPU.** (Use the G-CPU block diagram and ASM charts in the back of the test.)

Using the signal names shown in controller G-GPU block diagram in the back of the test, complete the ASM chart (on the next page) to implement the following 3 instructions (**AND_BA**, **LDA \$addr**, and **BEQ \$addrL**), including the completion of State A and State B.

Notes:

- (1) In each state and conditional output, specify **only the signals that should be true**.
- (2) However, you should use the notation: **MSA=01**, **MSB=10**, **MSC=000**.
- (3) The default actions for each state should be specified to “**hold**” **REGA** and **REGB** and **OUT = REGA**.
- (4) For your convenience, the required values for MSA, MSB, and MSC are given below:

Table 1: Input source MUXs for Registers A and B.

MSA1/ MSB1	MSA0/ MSB0	Bus Selected as Input to REGA/REGB
0	0	INPUT Bus
0	1	REGA Bus
1	0	REGB Bus
1	1	OUTPUT Bus

Table 2: ALU function selection MUX. (MUX C)

MSC2:0	Action
000	REGA Bus to OUTPUT Bus
001	REGB Bus to OUTPUT Bus
010	complement of REGA Bus to OUTPUT Bus
011	bit wise AND REGA/REGB Bus to OUTPUT Bus
100	bit wise OR REGA/REGB Bus to OUTPUT Bus
101	sum of REGA Bus & REGB Bus to OUTPUT Bus
110	shift REGA Bus left one bit to OUTPUT Bus
111	shift REGA Bus right one bit to OUTPUT Bus without sign extension

Put the solution on the next page.

8 (continued): Put solution here:

