

**COVER SHEET:**

Prob.	Points:	
1		(10)
2		(10)
3		(10)
4		(14)
5		(14)
6		(15)
7		(15)
8		(12)

**Total:**  (100)

**Re-Grade Information:**

---

---

---

---

---

---

---

---

---

---

---

---

---

---

---

---

---

---

---

---

---

---

---

---


Remember to show **ALL** work here and in **EVERY** problem on this exam.

[10%] **1. Circuit Analysis**

What is the logic equation for X in the given circuit? Do **not** simplify or transform it into an SOP or POS form. Leave the logic expression as it is after analysis. Also, draw the **intermediate** expression at the **input** to **each** gate.

- Notation reminder:  $A(H)$  is the same as  $A.H$
- Boolean expression answers must be in **lexical order**, i.e., /A before A, A before B, etc.


**EQUATION:  $X =$**  \_\_\_\_\_

 


[10%] **2. Circuit Synthesis**

Draw a mixed-logic circuit diagram (with the minimum number of gates) to **directly implement** the below equation. All inputs and the output can be of any activation-level desired. Be sure to **specify the desired activation levels**. Do **not** simplify this equation. You may **only use** gates available on 74HC10 chips (shown). Use as many 74HC10 chips as you need, but use the minimum number required to solve this problem.
 
$$F = A * B * D + B * /C * /E + /A * C * /D$$



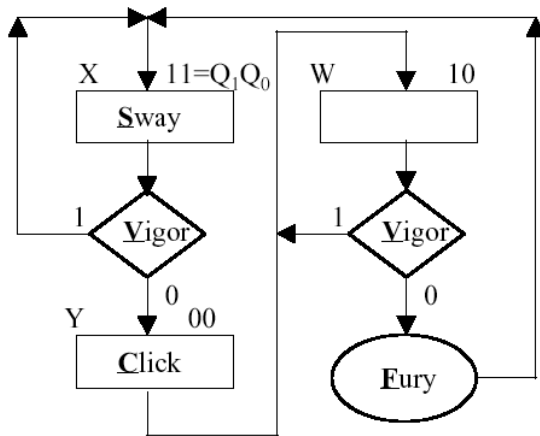[10%] **3. Implementation of an ASM chart using clocked S-R FFs**




**S-R characteristic table:**


S	R	Q	Q+
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	?
1	1	1	?

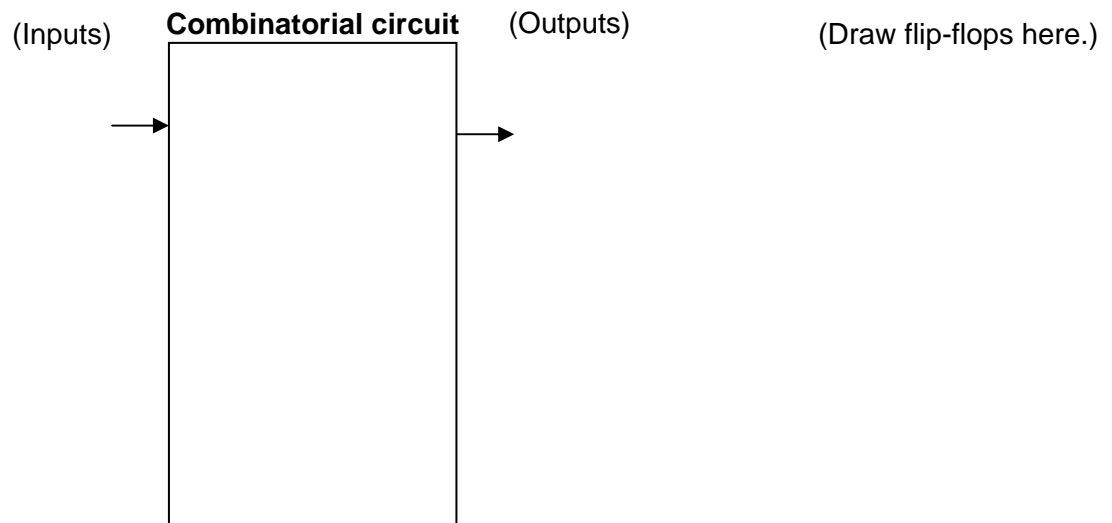(a) Given the above ASM chart, complete the following block diagram of its implementation using the minimum number of **clocked** S-R flip-flops: (2%)

- Determine how many clocked S-R flip-flops that are needed.
- Draw in all the inputs and outputs of the combinatorial circuit.
- Make all necessary connections to complete the block diagram (between the combinatorial circuit and the clocked S-R flip-flops).



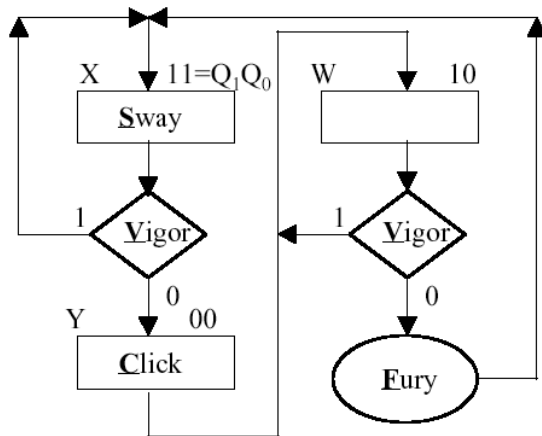3. (continued) (ASM chart is repeated here for your convenience)



S-R characteristic table:

S	R	Q	Q+
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	?
1	1	1	?

(b) Finish the implementation of the ASM by determining the **minimum sum-of-products (MSOP)** logic expressions for all the output signals: (8%)

(If necessary, use the bottom/back of the previous page to do your work.)

[14%] 4. Assume the below has already been run, and the code that follows in a, b, c, d, e, f, g will follow. Hand assemble the following instructions and fill in the blanks. EA is the 16-bit effective address. If there is no effective address, write none. (Use the G-CPU instruction set attached to this test).

```

Data0    ORG    $0032    Data6    ORG    $0048
         DC.B   $66      Data6    DC.B   $3E
         ORG    $0028    Data6    ORG    $0058
Data1    DC.B   $A3      Data7    DC.B   $9E
         ORG    $002A    Data7    ORG    $2A42
Data2    DC.B   $74      Data8    DC.B   $99, $AC
         ORG    $0038
Data3    DC.B   $EC
         ORG    $003A
Data4    DC.B   $EC
         ORG    $0040
Data5    DC.B   $AB
         SUM_AB
    
```

<u>ADDRESS</u>	<u>INSTRUCTION</u>	<u>HEX ADDRESS</u>	<u>HEX VALUE</u>
a) \$0008	STAB 48,X	<u>0008</u>	<u>          </u>
EA = _____		<u>0009</u>	<u>          </u>
Value stored = _____		<u>000A</u>	<u>          </u>
		<u>000B</u>	<u>          </u>
b) \$0008	LDAA 40	<u>0008</u>	<u>          </u>
EA = _____		<u>0009</u>	<u>          </u>
A = _____		<u>000A</u>	<u>          </u>
		<u>000B</u>	<u>          </u>
c) \$0008	LDX #Data8	<u>0008</u>	<u>          </u>
EA = _____		<u>0009</u>	<u>          </u>
X = _____		<u>000A</u>	<u>          </u>
		<u>000B</u>	<u>          </u>
d) \$0008	TBA	<u>0008</u>	<u>          </u>
EA = _____		<u>0009</u>	<u>          </u>
A = _____		<u>000A</u>	<u>          </u>
		<u>000B</u>	<u>          </u>
e) \$0008	LDAB Data8	<u>0008</u>	<u>          </u>
EA = _____		<u>0009</u>	<u>          </u>
B = _____		<u>000A</u>	<u>          </u>
		<u>000B</u>	<u>          </u>
f) \$0008	BN \$EF	<u>0008</u>	<u>          </u>
EA = _____		<u>0009</u>	<u>          </u>
PC after this instruction = _____		<u>000A</u>	<u>          </u>
		<u>000B</u>	<u>          </u>
g) \$0008	BNE \$EF	<u>0008</u>	<u>          </u>
EA = _____		<u>0009</u>	<u>          </u>
PC after this instruction = _____		<u>000A</u>	<u>          </u>
		<u>000B</u>	<u>          </u>

**[14%] 5. EEPROM and SRAM**

Given as many **256x8 EEPROM chips** and **256x8 static RAM chips** as needed, design a **1024x8** memory module (**with a CS**) that has **512x8** of **RAM** at the lowest addresses and **512x8** of **EEPROM** at the highest addresses. The **512x8** of **RAM** must start at address 0 and the first address of the **512x8** of **EEPROM** must immediately follow the last RAM address. Add the minimum number of additional components required. Make sure the EEPROM **is NEVER** enabled during a write cycle and the RAM is enabled for **both** read and write cycles. The EEPROM and SRAM devices have active low **CS** and the SRAM devices have a R/W control signal.

- (2%) a) What is the address range for **each of the** memory components (in **binary** and in **hex**)?

SRAM

EEPROM

- (12%) b) Design the required memory device below. Make sure you show the memory module's inputs and outputs and all the individual memory component devices. **Use labels instead of wires in the design.**







[12%] **8. GCPU Instruction Design** (See the G-CPU Next State Table attached to this test)


We want to implement a new instruction for the GCPU. The new instruction will be denoted as **SBAM addr**. It added the content of register B to register A (like SUM\_BA). But, it also stores the result into memory at location “addr”. The **new opcode** for this instruction will be designated as **\$32** and the **next state available** in the Controller’s ASM is **\$34**. Show the additional states required to implement this new instruction in the Controller’s ASM below and show all controller output signals that must be true in each new state for this new instruction:

**Assume:** R/-W is True for **Read** and **False** for **Write**.

**Control Signals:** PC\_INC, PC\_LD\_Upper, PC\_LD\_Lower, MAR\_INC, MAR\_LD\_Upper, MAR\_LD\_Lower, X\_INC, X\_LD\_Upper, X\_LD\_Lower, Y\_INC, Y\_LD\_Upper, Y\_LD\_Lower, IR\_LD, R/-W, ADDR\_SEL1:0, XD\_LD, YD\_LD

**Note1:** The controller output signals are also shown in the G CPU Block Diagram for reference.

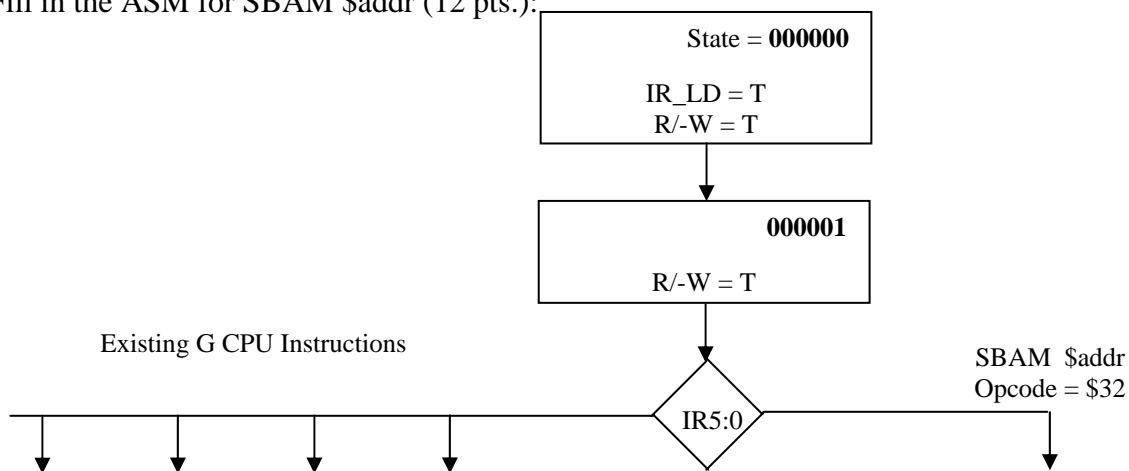Fill in the ASM for SBAM \$addr (12 pts.):



**GCPU Instructions****Data Movement Instructions:**

Opcode	Instruction	Operand	Description	# of States
0	TAB	none	Transfer A to B (inherent addressing)	2
1	TBA	none	Transfer B to A (inherent addressing)	2
2	LDAA #data	8 bit data	Load A with immediate data (immediate addr.)	3
3	LDAB #data	8 bit data	Load B with immediate data (immediate addr.)	3
4	LDAA addr	16 bit address	Load A with data from memory location addr (extended addressing)	5
5	LDAB addr	16 bit address	Load B with data from memory location addr (extended addressing)	5
6	STAA addr	16 bit address	Store data in A to memory location addr (extended addressing)	5
7	STAB addr	16 bit address	Store data in B to memory location addr (extended addressing)	5
8	LDX #data	16 bit data	Load X with immediate data (immediate addr.)	4
9	LDY #data	16 bit data	Load Y with immediate data (immediate addr.)	4
A	LDX addr	16 bit addr	Load X with data from memory location addr. (extended addressing)	6
B	LDY addr	16 bit addr	Load Y with data from memory location addr. (extended addressing)	6
C	LDAA dd,X	8 bit displacement	Load A with data from memory location pointed to by X + dd (indexed addressing)	4
D	LDAA dd,Y	8 bit displacement	Load A with data from memory location pointed to by Y + dd (indexed addressing)	4
E	LDAB dd,X	8 bit displacement	Load B with data from memory location pointed to by X + dd (indexed addressing)	4
F	LDAB dd,Y	8 bit displacement	Load B with data from memory location pointed to by Y + dd (indexed addressing)	4
10	STAA dd,X	8 bit displacement	Store data in A to memory location pointed to by X + dd (indexed addressing)	4
11	STAA dd,Y	8 bit displacement	Store data in A to memory location pointed to by Y + dd (indexed addressing)	4
12	STAB dd,X	8 bit displacement	Store data in B to memory location pointed to by X + dd (indexed addressing)	4
13	STAB dd,Y	8 bit displacement	Store data in B to memory location pointed to by Y + dd (indexed addressing)	4


14	SUM_BA	none	Sum A, B and place in A (inherent addressing)	2
15	SUM_AB	none	Sum A, B and place in B (inherent addressing)	2
16	AND_BA	none	AND A, B and place in A (inherent addressing)	2
17	AND_AB	none	AND A, B and place in B (inherent addressing)	2
18	OR_BA	none	OR A, B and place in A (inherent addressing)	2
19	OR_AB	none	OR A, B and place in B (inherent addressing)	2
1A	COMA	none	Complement contents in A (inherent addressing)	2
1B	COMB	none	Complement contents in B (inherent addressing)	2
1C	SHFA_L	none	Shift A left by one bit (inherent addressing)	2
1D	SHFA_R	none	Shift A right by one bit (inherent addressing)	2
1E	SHFB_L	none	Shift B left by one bit (inherent addressing)	2
1F	SHFB_R	none	Shift B right by one bit (inherent addressing)	2
30	INX	none	Increment X (inherent addressing)	2
31	INY	none	Increment Y (inherent addressing)	2

20	BEQ	addrL	Branch if A = 0, i.e., Z Flag = 1 (absolute addressing)	3
21	BNE	addrL	Branch if A ≠ 0, i.e., Z Flag = 0 (absolute addressing)	3
22	BN	addrL	Branch if A is negative, i.e., N Flag = 1 (absolute addressing)	3
23	BP	addrL	Branch if A is positive (or zero), i.e., N Flag = 0 (absolute addressing)	3

Special Notes

- Z flag and N flag are only set and cleared by the contents in register A.
- A branch is accomplished by moving the operand address "addr" to the lower byte of the PC. The upper byte of the PC remains unchanged after a branch.
- The Branch Instructions use absolute addressing where only the low byte of the address is used as an operand. If the branch condition is met, the high byte of the PC is unchanged and the low byte takes the value of the operand (addrL).

### GCPU Block Diagram

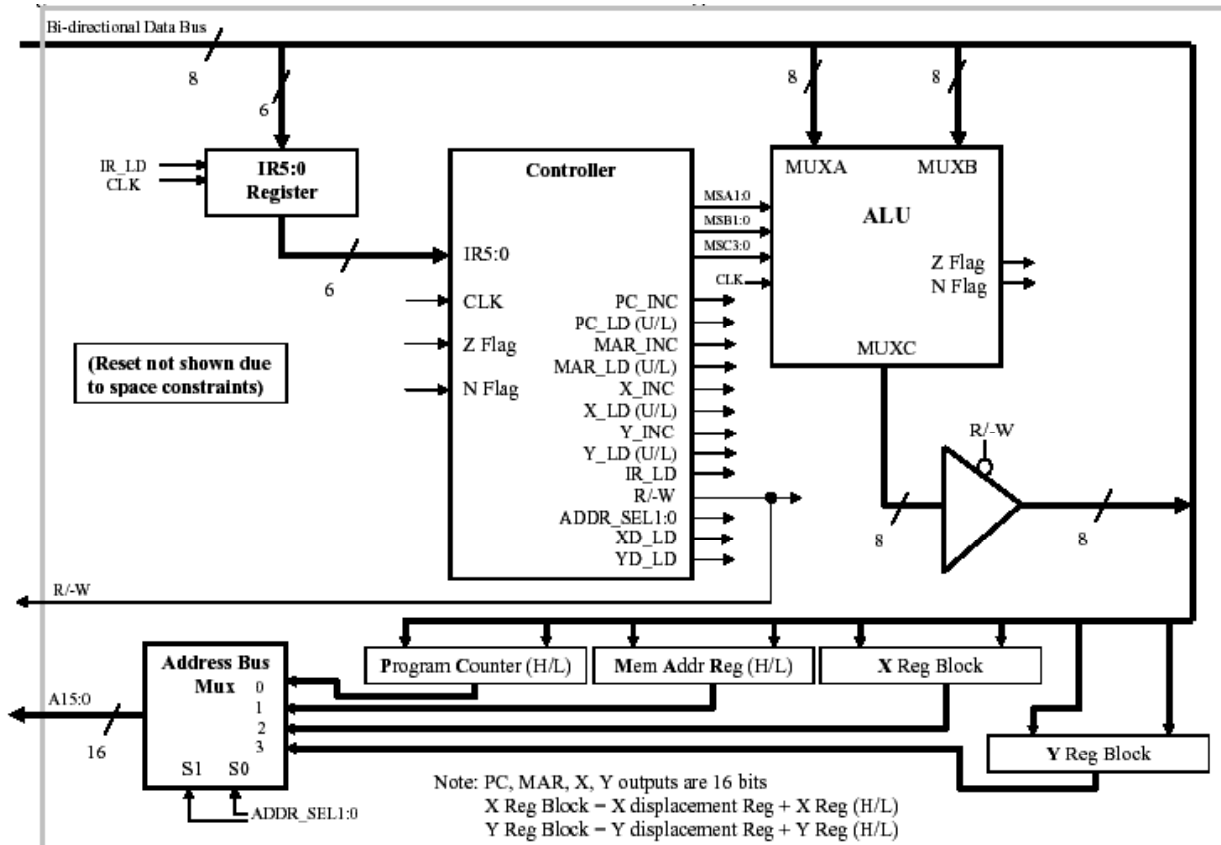

MSA1/ MSB1	MSA0/ MSB0	Bus Selected as Input to REGA/REGB
0	0	INPUT Bus
0	1	REGA Output Bus
1	0	REGB Output Bus
1	1	OUTPUT Bus

MSC2:0	Action
000	REGA Bus to OUTPUT Bus
001	REGB Bus to OUTPUT Bus
010	complement of REGA Bus to OUTPUT Bus
011	bit wise AND REGA/REGB Bus to OUTPUT Bus
100	bit wise OR REGA/REGB Bus to OUTPUT Bus
101	sum of REGA Bus & REGB Bus to OUTPUT Bus
110	shift REGA Bus left one bit to OUTPUT Bus
111	shift REGA Bus right one bit to OUTPUT Bus (without sign extension)

**Partial GCPU Next State Table**

Pres State	Opcode	Flags	Next State	Mux Select			Control		REG INC	ADDR SEL	PC	MAR	X,Y Loading		Disp Regs	Present State Function
				MSA [1..0]	MSB [1..0]	MSC [3..0]	IR LD	R /W	PC MAR X Y	ADDR SEL [1..0]	PC LD L/U	MAR LD L/U	X LD L/U	Y LD L/U	XD_LD YD_LD	
000000	XXXXXXX	XX	000001	01	10	0000	1	1	0000	00	00	00	00	00	00	generic instruction fetch
000001	000000	XX	000000	01	01	0000	0	1	1000	00	00	00	00	00	00	Transfer A to B (TAB)
000001	000001	XX	000000	10	10	0000	0	1	1000	00	00	00	00	00	00	Transfer B to A (TBA)
000001	000010	XX	000010	01	10	0000	0	1	1000	00	00	00	00	00	00	LDAA #data, state 1
000010	XXXXXXX	XX	000000	00	10	0000	0	1	1000	00	00	00	00	00	00	LDAA #data, state 2
000001	000011	XX	000011	01	10	0000	0	1	1000	00	00	00	00	00	00	LDAB #data, state 1
000011	XXXXXXX	XX	000000	01	00	0001	0	1	1000	00	00	00	00	00	00	LDAB #data, state 3
000001	000100	XX	000100	01	10	0000	0	1	1000	00	00	00	00	00	00	LDAA addr, state 1
000100	XXXXXXX	XX	000101	01	10	0000	0	1	1000	00	00	10	00	00	00	LDAA addr, state 4
000101	XXXXXXX	XX	000110	01	10	0000	0	1	1000	00	00	01	00	00	00	LDAA addr, state 5
000110	XXXXXXX	XX	000000	00	10	0000	0	1	0000	01	00	00	00	00	00	LDAA addr, state 6
000001	000101	XX	000111	01	10	0000	0	1	1000	00	00	00	00	00	00	LDAB addr, state 1
000111	XXXXXXX	XX	001000	01	10	0000	0	1	1000	00	00	10	00	00	00	LDAB addr, state 7
001000	XXXXXXX	XX	001001	01	10	0000	0	1	1000	00	00	01	00	00	00	LDAB addr, state 8
001001	XXXXXXX	XX	000000	01	00	0000	0	1	0000	01	00	00	00	00	00	LDAB addr, state 9
000001	000110	XX	001010	01	10	0000	0	1	1000	00	00	00	00	00	00	STAA addr, state 1
001010	XXXXXXX	XX	001011	01	10	0000	0	1	1000	00	00	10	00	00	00	STAA addr, state A
001011	XXXXXXX	XX	001100	01	10	0000	0	1	1000	00	00	01	00	00	00	STAA addr, state B
001100	XXXXXXX	XX	000000	01	10	0000	0	0	0000	01	00	00	00	00	00	STAA addr, state C
000001	000111	XX	001101	01	10	0000	0	1	1000	00	00	00	00	00	00	STAB addr, state 1
001101	XXXXXXX	XX	001110	01	10	0000	0	1	1000	00	00	10	00	00	00	STAB addr, state D
001110	XXXXXXX	XX	001111	01	10	0000	0	1	1000	00	00	01	00	00	00	STAB addr, state E
001111	XXXXXXX	XX	000000	01	10	0001	0	0	0000	01	00	00	00	00	00	STAB addr, state F
000001	010100	XX	000000	11	10	0010	0	1	1000	00	00	00	00	00	00	SUM_BA state 1
000001	010101	XX	000000	01	11	0010	0	1	1000	00	00	00	00	00	00	SUM_AB state 1
000001	010110	XX	000000	11	10	0011	0	1	1000	00	00	00	00	00	00	AND_BA state 1
000001	010111	XX	000000	01	11	0011	0	1	1000	00	00	00	00	00	00	AND_AB state 1
000001	100011	X0	110010	01	10	0000	0	1	1000	00	00	00	00	00	00	BP addr state 1
000001	100011	X1	110011	01	10	0000	0	1	1000	00	00	00	00	00	00	BP addr state 1
110010	XXXXXXX	XX	000000	01	10	0000	0	1	0000	00	10	00	00	00	00	BP addr state 32
110011	XXXXXXX	XX	000000	01	10	0000	0	1	1000	00	00	00	00	00	00	BP addr state 33
000001	110000	XX	000000	01	10	0000	0	1	1010	00	00	00	00	00	00	Increment X (INX)
000001	110001	XX	000000	01	10	0000	0	1	1001	00	00	00	00	00	00	Increment Y (INY)