

Open book and open notes, **90-minute** examination. **No electronic devices are permitted.**

Page 1) 13 points _____ Page 2) 25 points _____

Page 3) 19 points _____ Page 4) 15 points _____

Page 5) 16 points _____ Page 6) 12 points _____

TOTAL _____ of 100

Re-grade requests must be handed in the day exams are returned in class. Write the problem number you wish reviewed. **A maximum of three review problems is allowed.** Do not write anywhere else on the exam other than below or you will receive a zero on the exam.

1. Problem No. _____

2. Problem No. _____

3. Problem No. _____

1. Perform the following binary additions and subtractions by hand. For full credit, **show all your work below.** Assume the numbers are all **unsigned binary**. (3,2,3 pt.)

$$\begin{array}{r} 111111 \\ 101010 \\ + \underline{111111} \end{array}$$

$$\begin{array}{r} 10101010 \\ - \underline{01111011} \end{array}$$

$$\begin{array}{r} 1101.001 \\ \times \underline{100.110} \end{array}$$


2. Write **-27** as a **16 bit Signed Hex** number. (2 pt.)

3. When multiplying (2) **8 bit Signed** numbers ($A * B$), how many bits are required in the final answer such that no overflow will ever occur? Hint: Solve for a smaller word length. (3 pt.)


4. Directly synthesize a circuit for the following Logic Equation using only **2 Input NOR gates**. (9 pt.)

$$Y = \overline{\overline{\overline{A}} + ((\overline{\overline{B+C}}) * D)} \quad ; A.L, B.L, C.H, D.L, Y.H \quad \text{Do Not Simplify the Equation!}$$

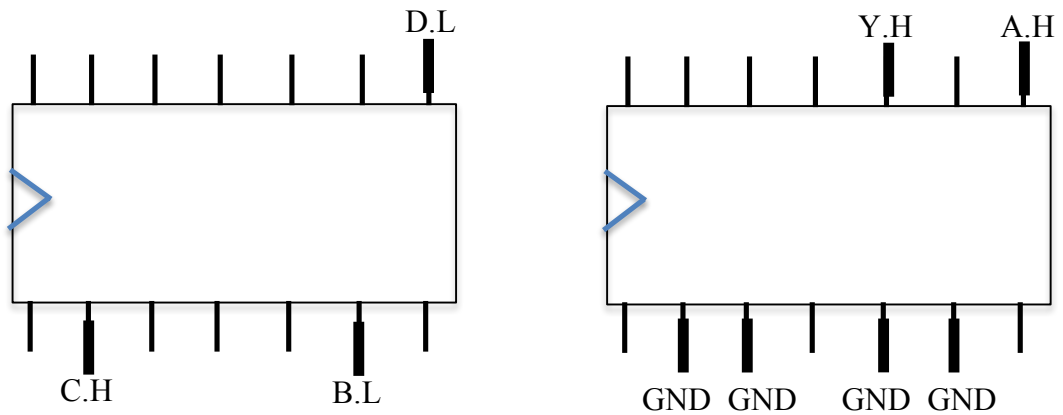5. Show the **ALL the CONNECTIONS** below to implement the above circuit in the two 74HC02 NOR ICs below. (7 pts.)



 9. Derive the logic equations for the following signals listed after the circuit below. **Show all intermediate signals as HIGH true for partial credit purposes. DO NOT SIMPLIFY YOUR ANSWER!**




Y.H = _____ (9 pt.)

10. Find the **minimum sum of products** and **minimum product of sums** for the logic equation below using a K-Map.



$$(B+C+D)(\bar{A}+B+\bar{C}+D)(A+\bar{C}+\bar{D})(\bar{B}+\bar{D})(A+B+\bar{C}+D)(\bar{A}+\bar{B}+\bar{D})$$

Y (MSOP) = _____ (5)

Y (MPOS) = _____ (5)

 

  11. Given the circuit below complete the **voltage timing diagram** for signals X and Y. Assume all devices have a **10 nsec** propagation delay. (9 pt.) Assume **A = B = Y = L, C = W = H** initially.



=> | t_p 10 ns | <=

12. Simplify the equation below with **De Morgan's Rule** and **Boolean Identities** to find the **MSOP**. (10 pt.)


$$P = (\overline{\overline{W}} * X)(\overline{\overline{W}} * \overline{\overline{Y}} * \overline{\overline{Z}})(\overline{\overline{V}} * \overline{\overline{W}} * \overline{\overline{Y}} * \overline{\overline{Z}})(\overline{\overline{V}} * X)(\overline{\overline{V}} * \overline{\overline{W}})(\overline{\overline{W}} * \overline{\overline{Y}} * \overline{\overline{Z}})$$

Y = _____ MSOP

13. Lucky #%\$@##! 13! Perform the following **Unsigned Binary division** below by hand. **Show at least 6 fractional binary bits in your answer.** (5 pt.)

$$11.01 \overline{) 10111.101}$$

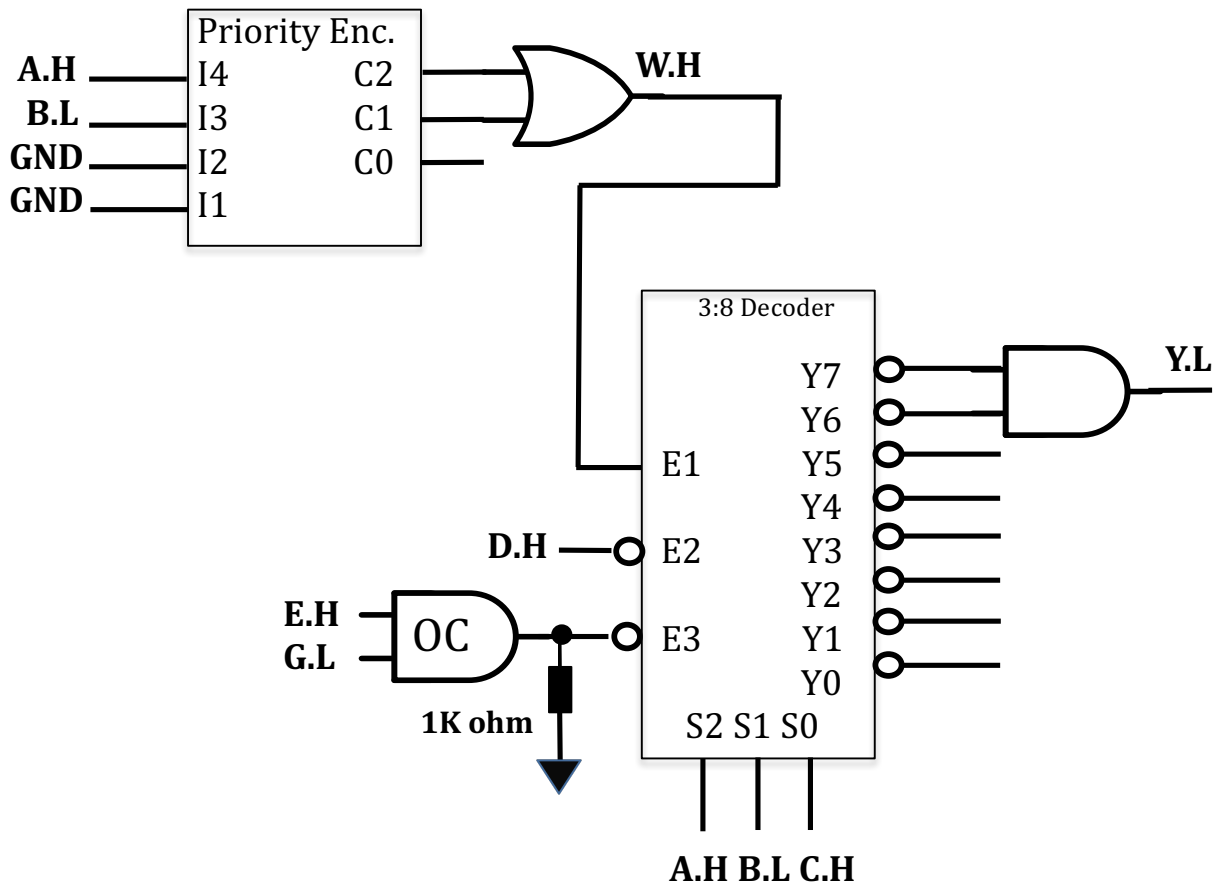14. For the circuit below find the **MSOP** for **W.H** and **Y.L**. (10 pt.)



W.H = _____ **MSOP** (3 pt.)

Y.L = _____ **MSOP** (7 pt.)

15. Implement the logic equation $Z = A*/B*/C$ (Z.L, A.L, B.H, C.L) in hardware using **Open Collector Inverters** and **1K ohm** resistors. (6 pt.)

16A. Design a **Signed Multiplier** that **multiplies a 3 bit signed (2's complement) number by -7**. The input is therefore a 3 bit signed number and output should be the input value multiplied by a constant (-7) Assume all inputs & outputs are high true. Create a Logic Truth Table below for the device below. (8 pt.)

16B. Determine the MSOP logic equation for the output Most Significant Bit (MSB). (4 pt.)