

Open book and open notes, 90-minute examination. No electronic devices are permitted.

Page 1) 9 points _____ Page 2) 23 points _____

Page 3) 18 points _____ Page 4) 17 points _____

Page 5) 18 points _____ Page 6) 15 points _____

TOTAL _____ of 100


Re-grade requests must be handed in the day exams are returned in class. Write the problem number you wish reviewed. A maximum of three review problems is allowed. Do not write anywhere else on the exam other than below or you will receive a zero on the exam.

1. Directly synthesize a circuit for the following equation using only 2 Input NOR gates only. (9 pt.)

$$Y = \overline{\overline{A} * (\overline{B * C}) + E + \overline{D}} \quad ; A.L, B.H, C.L, D.H, E.L, Y.H \quad \text{Do Not Simplify the Equation!}$$

 2. Find the **minimum sum of products** and **minimum product of sums** for the logic equation below using a K-Map. (14 pt.)


$$Y = (A+B+C+D)(/A+/B+C+D)(/A+C+D)(B+/C+D)(A+/B+/D)$$



Y (MSOP) = _____ (8)

Y (MPOS) = _____ (6)

 3. Derive the logic equations for the following signals listed after the circuit below. **Show all intermediate signals as HIGH true for partial credit purposes. DO NOT SIMPLIFY YOUR ANSWER!**



W.H = _____ (5 pt.)

Y.L = _____ (4 pt.)

4. Simplify the equation below with **De Morgan's Rule** and **Boolean Identities** to find the **MSOP**. (10 pt.)

$$Y = (X+Y+Z)(\overline{X+\overline{Y+W}})(\overline{X+\overline{Z+W}})(\overline{X+\overline{Z}})(\overline{X+\overline{Z+W}})(\overline{X+Y+Z})$$

Y = _____ **MSOP**

5. A student would like to design a **multiplier** that computes the product of a **2 bit unsigned number** times a **3 bit unsigned number**. i.e. $P = M_{1:0} \times N_{2:0}$;where all numbers are unsigned binary

How many bits are required for P? _____ (2 pt.)

Write the **Canonical Sum of Products (CSOP)** for the **most significant bit of P** based on inputs **M1:0** and **N2:0** below. (8 pt.)


6 – 8. Perform the following addition, subtraction and multiplication. (9 pt.)

$$\begin{array}{r} 111001 \\ 101101 \\ + \underline{111111} \\ \hline \end{array}$$

$$\begin{array}{r} 10010001 \\ - \underline{01111110} \\ \hline \end{array}$$


$$\begin{array}{r} 10101.01 \\ \times \underline{101.01} \\ \hline \end{array}$$

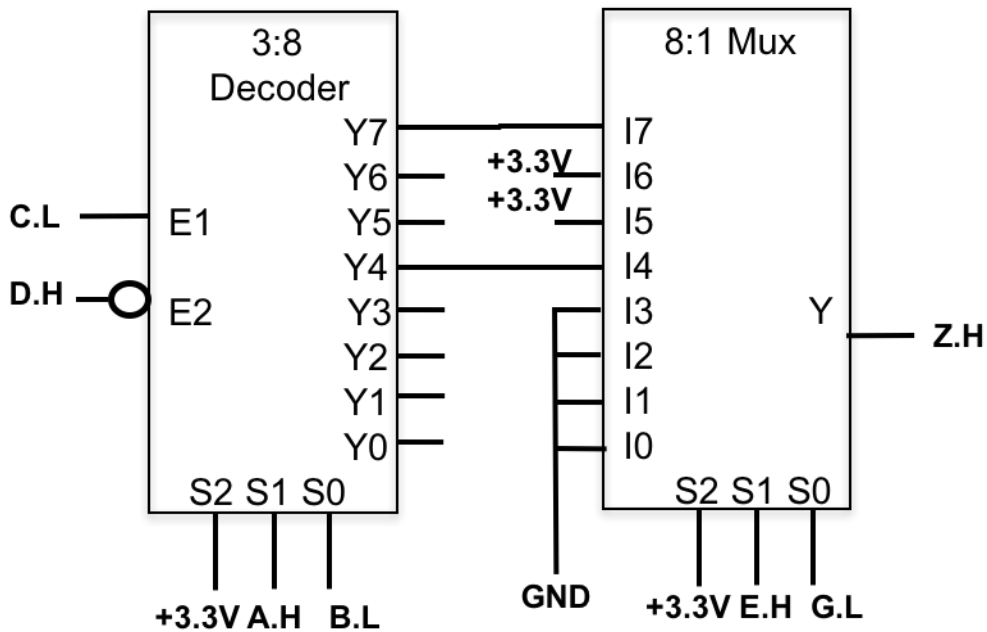9. For the circuit below, derive the logic equation for Z.H. **Do not Simplify!** (8 pt.)




Z.H = _____

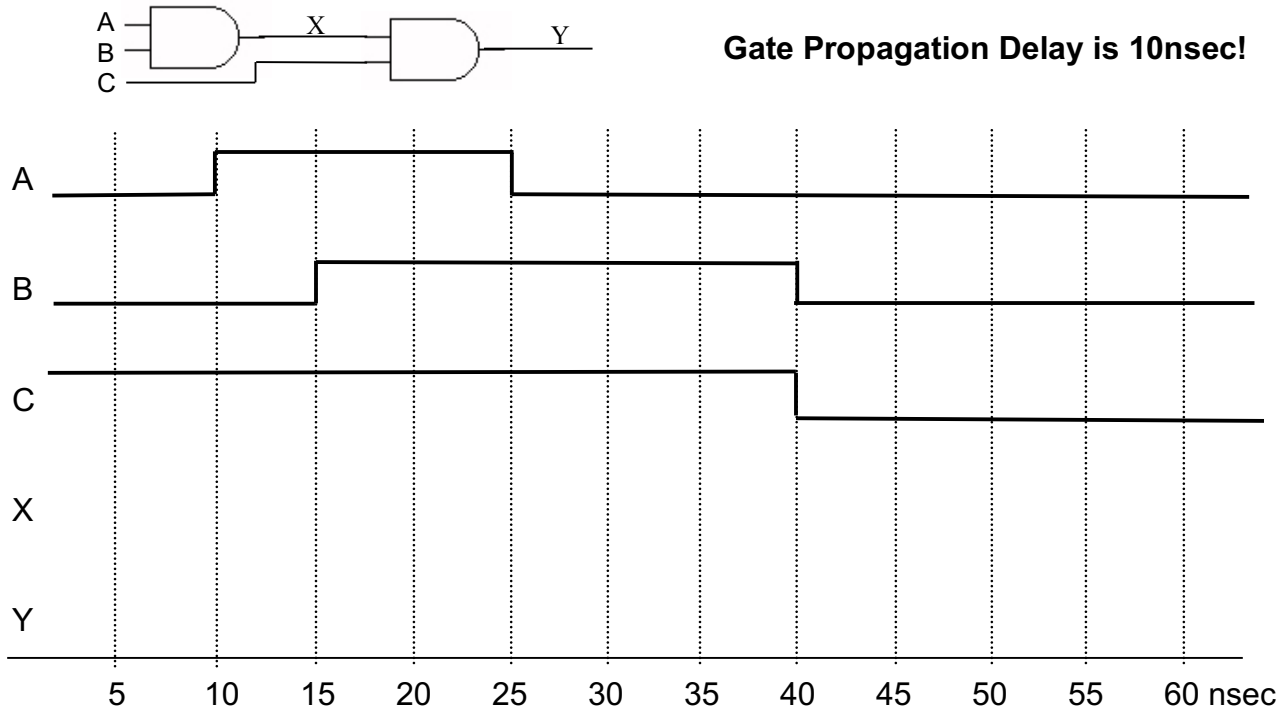10. Given the circuit below complete the voltage timing diagram for signals X and Y. Assume all devices have a **10nsec** propagation delay. (8 pt.) **Assume A=L, B=L, C=H initially.**



 11. For the circuit below derive the **logic equation for Y** and **add the required missing Pull-up or Pull-down resistor** to make Y a function of A,B,C,D, E, G and N. (10 pt.)



Y.L = _____

12. Create a device that decrements a **4 bit Signed Number** by 1. **N3:0** is the **signed input** and **M3:0** is the **signed output** equivalent to **N3:0 - 1**. For example, if a "3" is input to the device, the output should be "2". One additional output, V, should also be generated that indicates when an overflow occurs. For example, if decrementing an input by 1 creates an overflow condition, output V = 1, otherwise V = 0.

Draw the truth table for the device below:

N3 N2 N1 N0 M3 M2 M1 M0 V (10 pt.)

Derive the MSOP Logic Equation for **M0** and **V** (5 pt.):