 


Open book/open notes, **90-minute** exam to be done in **non-red** pen. **No electronic devices permitted.**

Point System: Page 1 => 10 points _____ Page 2 => 14 points _____
 Page 3 => 14 points _____ Page 4 => 12 points _____
 TOTAL => _____ (50 pt.)

Grade Review Information: (NOTE: deadline of request for grade review is the day the exam is returned.)

1. For the circuit below, derive Z.L. **Do not simplify.** Write all intermediate terms as high true. (5 pt.)




Z.L = _____

2. Implement the logic equation below using 2 Input NOR Gates only. (5 pt.)

$$Y = (\overline{A} * B) + C + (\overline{D} * \overline{E}) \quad ; A.H, B.L, C.H, D.L, E.H, Y.H$$

 5. Refer to the CPU, Controller and ROM Contents in Appendix A to complete the Voltage Timing Diagram Below. Use 'X' to indicate an unknown condition and show all answers in **HEX**. (8 pt.)



Note: RA3:0 = Register A, RB3:0 = Register B

6. Using only 2:1 decoders, flip-flops, 2:1 muxes, single bit full adders and any other elementary digital components, design the X Register Block in the G CPU. Label all signals in your design. Note: Several of these signals should match those shown in the G CPU Block Diagram. Best design = Most points. (6 pts.)

7. For the next set of questions, see the G CPU shown in Appendix B. Fill in the cycle table below for the **second pass** of the line of code shown below. (7 pt.)


	STAB		2,Y							Dev driving	Dev Driving
Cycle	Addr Bus	Data Bus	IR	PC	R/-W	B Reg	Y Reg			Addr Bus	Data Bus
1											
2											
3											
4											

8. Show the modified contents of RAM, after the code has executed in Appendix B. Note: show only the locations modified in RAM at execute (run) time. Show both the modified addresses and data. (2 pt.)


9. Assuming that only one ROM is used in the system for the code in Appendix B, what is the maximum size possible for this ROM? (1 pt.)

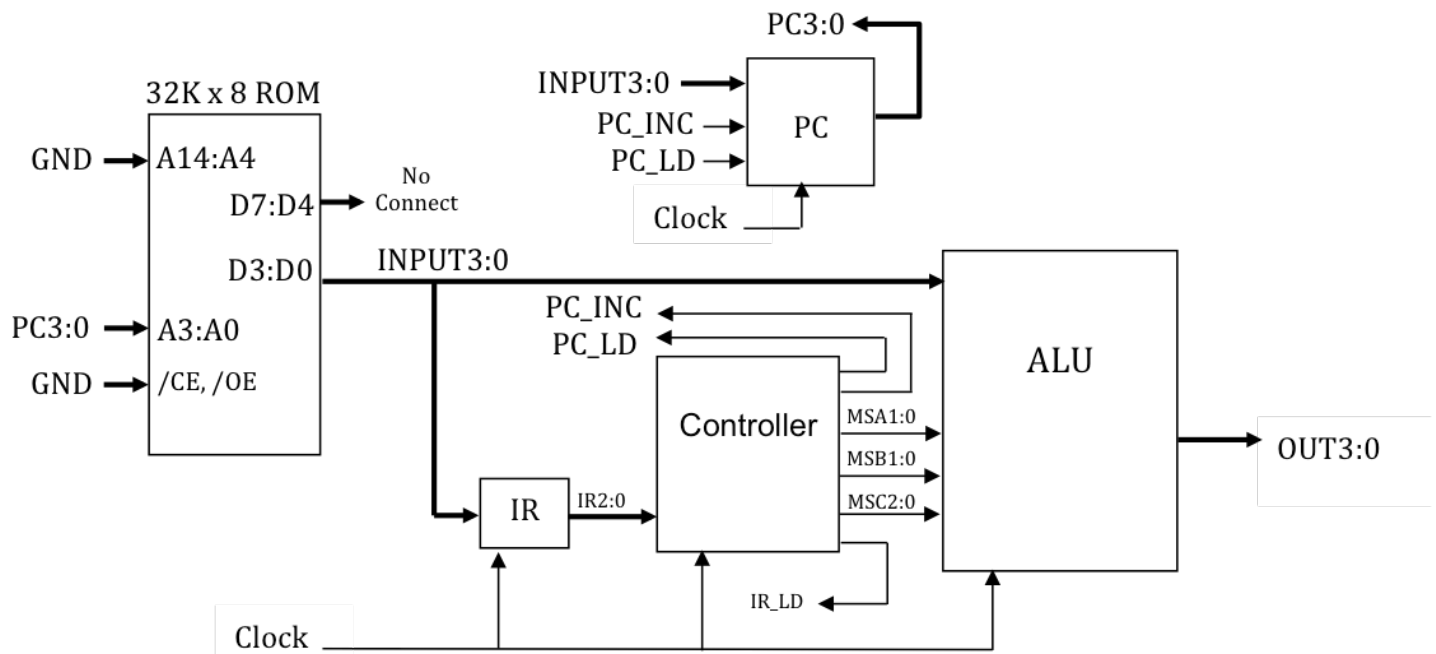10. How many bits of storage are required if a ROM is used to implement the G CPU Controller? (2 pt.)

Appendix A. Elementary CPU (Lab #9), Controller ASM and ROM Contents



Controller ASM:

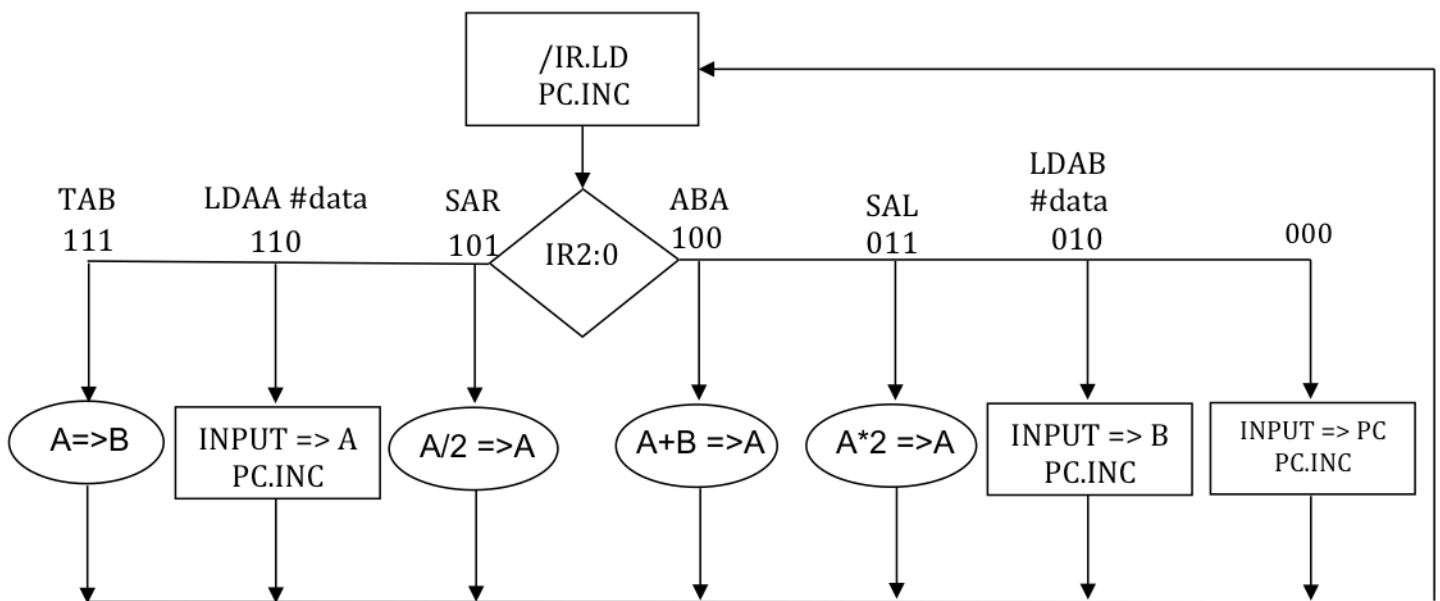

32K x 8 ROM Contents:

Address	=>	0	1	2	3	4	5	6
Data (Hex)	=>	F6	FA	F5	F2	FC	F4	F7

Appendix B. G-CPU Code for Problem #7 (space on left for hand assembly):

```

                ORG      $0
                LDX      #$0
                LDY      #$4000
                LDAA     #8
                STAA     0,Y

T1              LDAA     2,X
                TAB
                SUM_AB
                STAB     2,Y      ;show 2nd pass of executing this code
                INX
                INY

                LDAA     $4000
                LDAB     #$FE
                SUM_BA
                STAA     $4000
                BNE      T1

END            BRA      END
```