 


Open book/open notes, **90-minute** exam to be done in **non-red** pen. **No electronic devices permitted.**

Point System: Page 1 => 10 points _____ Page 2 => 14 points _____
 Page 3 => 14 points _____ Page 4 => 12 points _____
 TOTAL => _____ (50 pt.)

Grade Review Information: (NOTE: deadline of request for grade review is the day the exam is returned.)



1. For the circuit below, derive Z.L. Do not simplify. Write all intermediate terms as high true. (5 pt.)



Z.L = $(\overline{AB})(\overline{C+D}) \cdot (E+F)$

  2. Implement the logic equation below using 2 Input NOR Gates only. (5 pt.)

$Y = (\overline{A} * B) + C + (\overline{D} * E)$; A.H, B.L, C.H, D.L, E.H, Y.H



KEY

3. A student has interfaced a 8K x 8 ROM with the G-CPU starting at address zero. The student also has interfaced an 16K x 8 RAM that begins immediately after the ROM in the G-CPU memory map. What is the memory range and logic equation for the RAM device? (4 pt.)


RAM Memory Range (Hex) 2000 to 5FFF

RAM Decode Equation = $CIK \cdot \overline{A15} (\overline{A14} \cdot A13 + A14 \cdot \overline{A13}) = CIK \cdot \overline{A15} (A13 \oplus A14)$

2000 - 3FFF 001x/xxxx/xxxx/xxxx 010x/xxxx/xxxx/xxxx

 4. A vector starting at address 0x800 in ROM contains an unknown amount of signed numbers that are 3 bytes in length. The last three byte signed number in the array is known to be -512 decimal. Write the code to count the number of negative numbers in the array and store the final result in Y. (10 pt.)

```
LDX #0x800 ; X ptr to data
LDY #0 ; init counter
```



```
TOP Ldaa 0, X ; get lower byte
BNE INC, Y ; = 0?
```

```
INC_Y : Ldaa 2, X
BP SKIP
IN Y
SKIP/IN X
IN X
TOP IN X
Ldaa #0
BEQ TOP
```


```
Ldaa 1, X
Ldab #2
Sum-ba
BNE INC_Y
```

```
Ldaa 2, X
Ldab #1
Sum-ba
BNE INC_Y
```

DONE BEQ DONE

OK to count or not count -512

13
2

 

64K RAM 2000 - 3FFF 8K 4000 - 5FFF 8K
Rom 0 - 1FFF

0 - 8FFF 4K 0010 0000 0000
 8 - 7FFF 8K 1101 1111 1111

0X FFFE 20

3. A student has interfaced a 8K x 8 ROM with the G-CPU starting at address zero. The student also has interfaced an 16K x 8 RAM that begins immediately after the ROM in the G-CPU memory map. What is the memory range and logic equation for the RAM device? (4 pt.)

RAM Memory Range (Hex) 2000 to 5FFF

RAM Decode Equation = $\overline{A_{15}} A_{14} \overline{A_{13}} + \overline{A_{15}} A_{14} A_{13}$

2000 - 3FFF 8K

4. A vector starting at address 0x800 in ROM contains an unknown amount of signed numbers that are 3 bytes in length. The last three byte signed number in the array is known to be -512 decimal. Write the code to count the number of negative numbers in the array and store the final result in Y. (10 pt.)

```
LDX # $0800 -- just init things
LDY # $0000
LDAB # $FE
```

LOOP: (0x0005)

```
LDAA $00, X
```

(0x0009) BP \$000D (check)

```
INY -- if neg, inc Y
```

(0x000D) -- Check if we are done

```
Check: LDAB 0XFF01 -- check for
```

```
SUM - BA
```

0xFF

```
BNE $0005 (loop)
```

0013

```
Ld AB 0x20 -- check for FE
```

```
LDAA $01, X
```

```
SUM - BA
```

```
BNE $0005 (loop)
```

```
LDAA $00, X -- check for 0
```

001F

```
INX -- inc X 3 times
```

```
INX
```

```
INX
```

```
BNE $0005 (loop)
```

END



```
BEQ END
```

5. Refer to the CPU, Controller and ROM Contents in Appendix A to complete the Voltage Timing Diagram Below. Use 'X' to indicate an unknown condition and show all answers in HEX. (8 pt.)


CLK								
PC3:0	0	1	2	3	4	5	6	7
INP3:0	6	A	5	2	C	4	7	
RA3:0	X	X	A	5	5	5	1	
RB3:0	X	X	X	X	X	C	C	
		LDAA #6	SAR		LDAB #C		ABA	TAB

Note: RA3:0 = Register A, RB3:0 = Register B

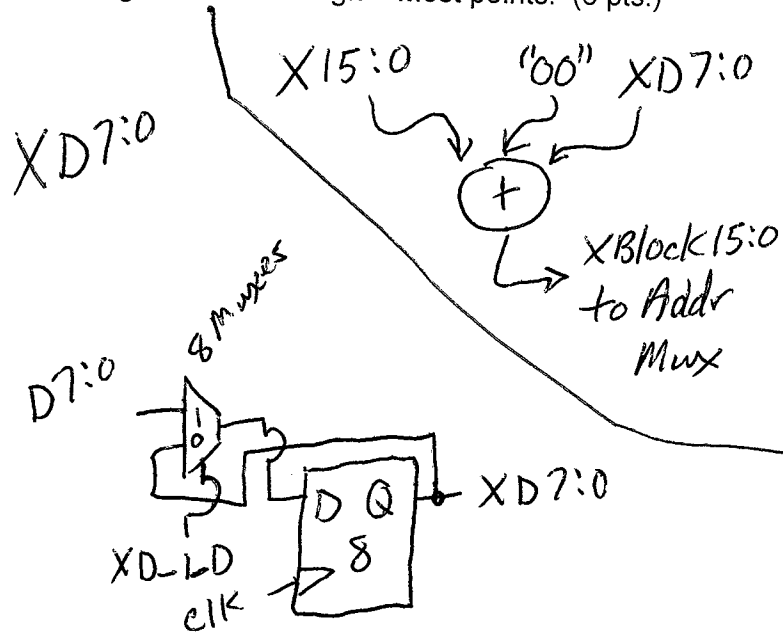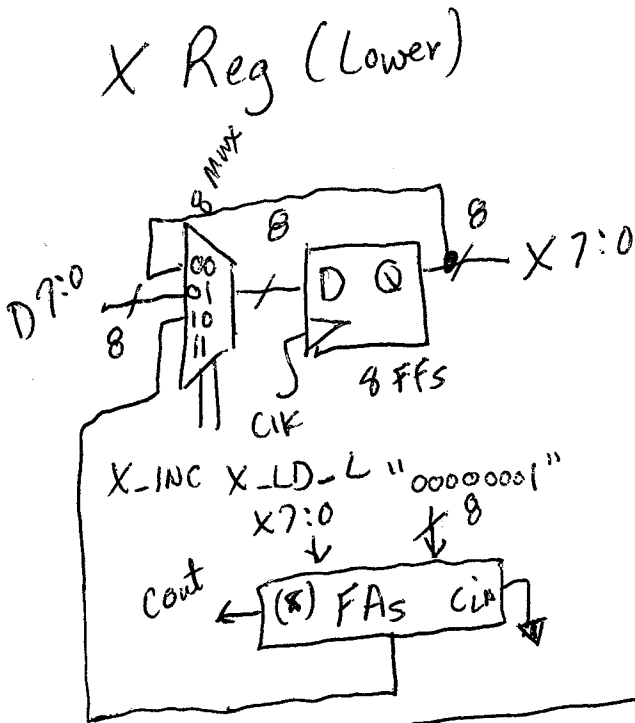6. Using only 2:1 decoders, flip-flops, 2:1 muxes, single bit full adders and any other elementary digital components, design the X Register Block in the G CPU. Label all signals in your design. Note: Several of these signals should match those shown in the G CPU Block Diagram. Best design = Most points. (6 pts.)



Same as above
 8 new Mux, 8 new F/Fs
 8 FAs; replace
 X-LD-L with
 X-LD-H

 

Page 3
 Cout → Cin and add "00"
 X7:0 → X15:8

Yes

7. For the next set of questions, see the G CPU shown in Appendix B. Fill in the cycle table below for the **second pass** of the line of code shown below. (7 pt.)

STAB 2,Y

Cycle	Addr Bus	Data Bus	IR	PC	R/-W	B Reg	Y Reg	Dev driving Addr Bus	Dev Driving Data Bus
1	000E	13	15	000E	1	12	4001	PC	ROM
2	000E	13	13	000E	1	12	4001	PC	ROM
3	000F	02	13	000F	1	12	4001	PC	ROM
4	4003	12	13	0010		12	4001	Y Block	CPU

8. Show the modified contents of RAM, after the code has executed in Appendix ^B. Note: show only the locations modified in RAM at execute (run) time. Show both the modified addresses and data. (2 pt.)

4000 [00] 4002 [00] 4003 [12]

4004 [00] 4005 [80]

9. Assuming that only one ROM is used in the system for the code in Appendix B, what is the maximum size possible for this ROM? (1 pt.)

0 - 3FFF


$2^{14} \Rightarrow 16K \times 8$

10. How many bits of storage are required if a ROM is used to implement the G CPU Controller? (2 pt.)


$2^8 \times 18$ or 256×18 } +2

256×26 } +2.5 extra 0.5!

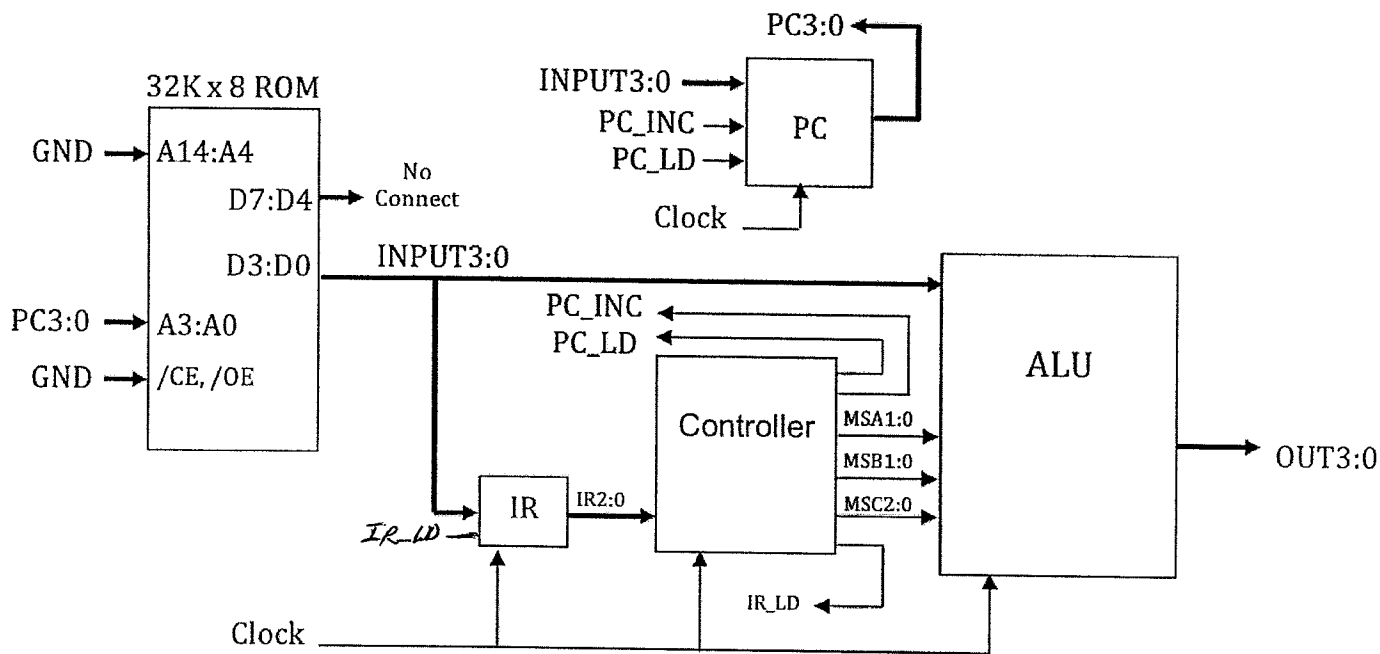Appendix A. Elementary CPU (Lab #9), Controller ASM and ROM Contents



Controller ASM:

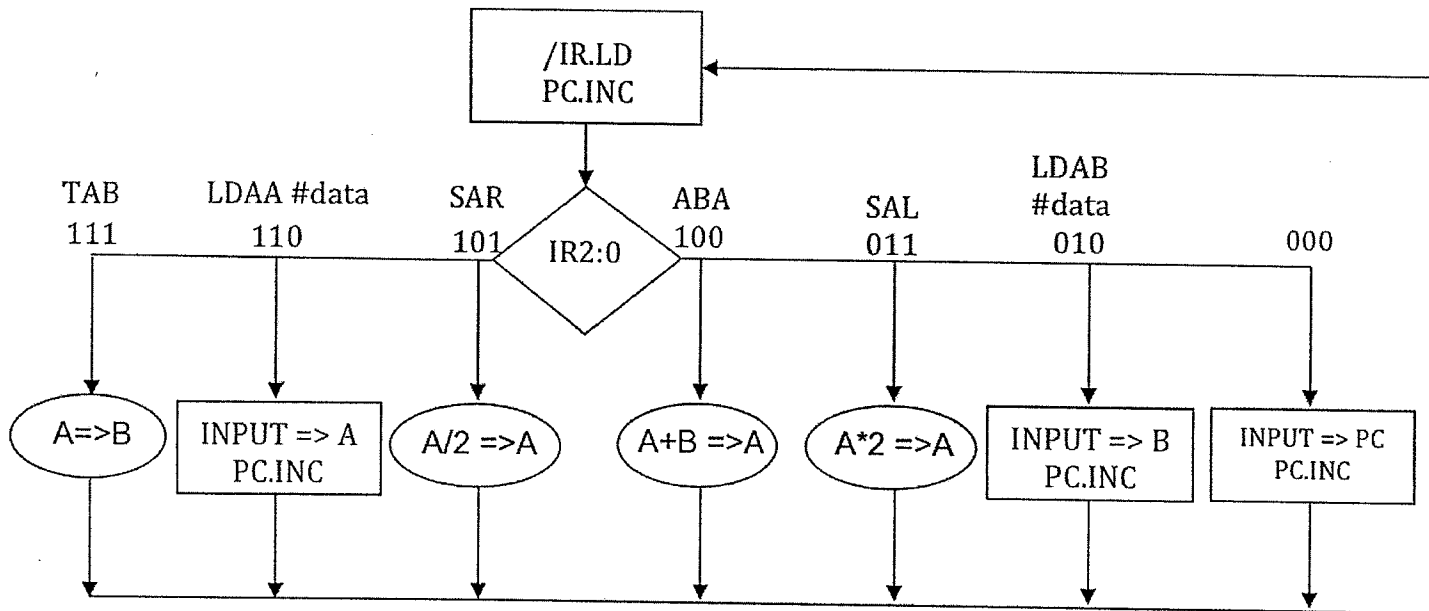

32K x 8 ROM Contents:

Address =>	0	1	2	3	4	5	6
Data (Hex) =>	F6	FA	F5	F2	FC	F4	F7

Handwritten annotations: LDAA #6; 2cy. (points to address 0), SAR; 1cy. (points to address 2), LDAB #C; 2cy. (points to address 3), ABA; 1cy. (points to address 4), TAB; 1cy. (points to address 6).

Appendix B. G-CPU Code for Problem #7 (space on left for hand assembly): Key

```

    ORG     $0
    LDX     #$0
    LDY     #$4000
    LDAA    #8
    STAA    0,Y

T1     LDAA    2,X
       TAB
       SUM_AB
       STAB   2,Y
       INX
       INY

       LDAA    $4000
       LDAB    #FEE = -2
       SUM_BA
       STAA    $4000
       BNE    T1

END     BRA     END
    
```

0006 →
0810 →

1st Pass	2nd Pass
X = 0	X = 1
Y = 4000	Y = 4001
A = B = 00	A = B = 9
Sum = 0	Sum = 12
4002 [00]	4003 [12]

; show 2nd pass of executing this code

3rd Pass	4th Pass
X = 2	X = 3
Sum = 00	Sum = 80

Addr	Data	
0	08	LDX #0
1	00	
2	00	
3	09	LDY #\$4000
4	00	
5	40	
6	02	LDAA #8
7	08	
8	11	STAA 0,Y
9	00	
A	0C	LDAA 2,X
B	02	

Addr	Data	
C	00	TAB
D	15	SUM_AB
E	13	STAB 2,Y
F	02	

4000 [00] 4002 [00] 4003 [12]
4004 [00] 4005 [80]