

*May the Schwartz  
be with you!*

**Exam 1P**

\_\_\_\_\_  
Last Name, First Name


**Go Gators!**

 **Instructions:**

- Turn off all **cell phones** and other **noise making devices** and put away **all electronics**.
- Show **all** work on the **front** of the test papers. **Box** each answer. If you need more room, make a clearly indicated note on the front of the page, "**MORE ON BACK**", and use the back. The back of the page will **not** be graded without an indication on the front.
- You may **not** use any notes, HW, labs, other books, scratch paper, or calculators.
- This exam counts for **27%** of your total course grade.
- Read each question **carefully** and **follow the instructions**.
- The point values for problems may be changed at prof's discretion.
- You must pledge and sign this page in order for a grade to be assigned.
- **CLEARLY** write your name at the top of **this** test page (and, if you remove the staple, all others). Be sure your exam consists of **10** distinct pages. Sign your name and add the date below. (If we struggle to read your name, **you will lose points**.)
- For circuit diagrams, use **labels** to identify physical connections instead of drawing lines (wires). Failure to do so will cost you one point per problem.
- For anything undefined, if necessary, state a reasonable assumption.
- Failure to follow the below rules will result in **NO** partial credit.
  - The **base** (radix) of all number must be indicated with a **subscript** or **prefix**.
  - Truth tables, voltage tables, and timing simulations must be in **counting** order.
  - Label the inputs and outputs of each circuit with activation-levels.
  - For each mixed-logic circuit diagram, label inputs of **each** gate with the appropriate logic equations.
  - For K-maps, label **each** grouping with the appropriate equation.
  - Labels inside of parts must be provided whenever it can be confusing, e.g., they **MUST** be specified for **MU**, but not for **NANDs** and **ORs**.
  - For each circuit design, equations must **not** be used as replacements for circuit elements.
  - Boolean expression answers must be in **lexical order**, (i.e., /A before A, A before B, & D<sub>3</sub> before D<sub>2</sub>).



UF CIMAR/MIL AV (Robot) Indy (Race Car) Challenge



**Good luck!**

**Please read  
carefully.**



**PLEDGE:** On my honor as a University of Florida student, I certify that I have neither given nor received any aid on this examination, nor I have seen anyone else do so.

\_\_\_\_\_  
SIGN YOUR NAME

\_\_\_\_\_  
DATE (9 Oct 2019)

Regrade comments below: Give page # and problem # and reason for the petition.	Problems	Available	Points
.	1	13	
.	2	10	
.	3-4	11	
.	5	12	
.	6	13	
.	7	14	
.	8	16	
.	9	11	
.	<b>TOTAL</b>	<b>100</b>	

# Exam 1P

\_\_\_\_\_   
Last Name, First Name

[13%] 1. Solve the following arithmetic problems. **Remember to show ALL work here and in EVERY problem on this exam.**

(4%) a) Determine the unsigned hexadecimal, octal, binary, and BCD representations of the number  $311_{10}$ .  
(I **strongly** recommend that you **check your work before** moving on to the next problem.)

5 min

Binary: \_\_\_\_\_

Octal: \_\_\_\_\_

Hex: \_\_\_\_\_

BCD: \_\_\_\_\_

(3%) b) Determine the **10-bit** signed magnitude, 1's complement, and 2's complement representations of the decimal number  $-311_{10}$ . (I **strongly** recommend that you **check your work before** moving on to the next problem.)

3 min

Signed Mag: \_\_\_\_\_

1's Comp: \_\_\_\_\_

2's Comp: \_\_\_\_\_

(3%) c) What is  $256_{10} - 311_{10}$  in **10-bit** 2's complement? You must use binary numbers to **derive** and determine the solution (not decimal). Hint:  $256 = 2^8$ . You must **show all work**.

3 min

$(256_{10} - 311_{10})_{2 \text{ 10-bit 2's comp}}$ : \_\_\_\_\_

# Exam 1P

\_\_\_\_\_   
 Last Name, First Name

(3%)  
3 min

1. d) What is  $-256_{10} - 311_{10}$  in **10-bit** 2's complement? You must use binary numbers to **derive** and determine the solution (not decimal). Hint:  $256 = 2^8$ . You must **show all work**

$(-256_{10} - 311_{10})_{2 \text{ 10-bit 2's comp}}$ : \_\_\_\_\_

[10%]  
7 min

2. Directly implement the below equation with a mixed-logic circuit diagram, i.e., do **NOT** simplify the equation. Use only **NOR** gates (or their mixed-logic equivalent). Minimize the **total number of gates**. You are free to choose the activation levels ; but the chosen activation-levels should optimize your solution. **Check twice** that you correctly read the equation!

$$UF = \overline{\overline{[(N + \bar{U}) + M] * (O * \bar{N} + E)}}$$

N( )\_\_

U( )\_\_

M( )\_\_

O( )\_\_

\_\_\_\_\_UF( )

E( )\_\_

# Exam 1P

\_\_\_\_\_  
Last Name, First Name



[5%]  
5 min

3. **Simplify** the following logic equation using only Boolean identities, laws, or theorems. Show all work. Give the solution in MSOP or MPOS form in **lexical** order. **Check twice** that you correctly read the equation!

$$UF = \overline{(\overline{I + S})} * \overline{\overline{[(\overline{B + \overline{E}}) + \overline{S} + T]}}$$

[6%]  
3 min

 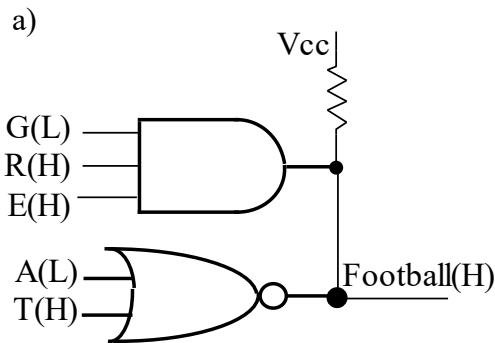4. Analyze the below circuits **carefully**. What are the equations for the outputs of the two similar circuits of parts a and b? Give the solution in **MSOP** or **MPOS** form in **lexical** order.




# Exam 1P

\_\_\_\_\_  
 Last Name, First Name

[12%] 5. Use the given multiplexers to **design mixed-logic circuit diagrams** that solve each of the below problems. **Be careful to read the equation correctly.** Choose activation levels for each signal (that has not already been assigned) to **minimize** the number of additional parts required. Use only SSI gates and add the **minimum** number necessary. Show all work. (The three below problems are **independent** of each other, but the equations are identical [other than the subscripts on  $X$ ].)


( %)   
 6 min

 a)  $X_0 = \overline{W} C + Y * (\overline{B * \overline{A}}) C$  (Note the **NON** tri-state enable.)




( %)   
 3 min

 b)  $X_1 = \overline{W} C + Y * (\overline{B * \overline{A}}) C$  (Note the **tri-state** enable.)



( %)   
 2 min

 c)  $X_2 = \overline{W} C + Y * (\overline{B * \overline{A}}) C$  (Note the **NON** tri-state enable.)



# Exam 1P


\_\_\_\_\_  
 Last Name, First Name

[13%] 6. Use the below equation for this problem.

$$Y = (\bar{A} + B + \bar{C} + D)(A + \bar{C} + \bar{D}) * (\bar{A} + C + D) * (A + \bar{C} + D) * (\bar{B} + C + D) * (A + C + D)$$

(8%)  
 8 min

 
a) Use a K-Map to simplify the above equation. Give the result in **MPOS** form and lexical order. Label **ALL** circles.



$Y_{MPOS} =$

(4%)  
 3 min

 b) If the terms ABCD=0001 and ABCD=1011, i.e., the textbook's d(1) and d(11), are **DON'T CAREs (X)**, determine the new **MSOP** equation, in lexical order. Label **ALL** circles.



$Y_{MSOP} =$

(1%)  
 1 min

c) Are the above equations (in parts a and b) **equivalent**? Why or why not?

\_\_\_\_\_

\_\_\_\_\_

\_\_\_\_\_

# Exam 1P

\_\_\_\_\_  
Last Name, First Name


[14%] 7. In this problem, you will design a mixed-logic circuit diagram and some input and output circuits.

(6%)

5 min

- a) Draw the **mixed-logic circuit** diagram to directly implement these two equations using parts from the 74'UF chip shown. These should be **circuit diagrams**, not layout diagrams. Choose the optimal (best) activation-levels for A and B. **Label the pin numbers** on your circuit diagram. X must be **active-high**, i.e., X(H).


$$X = \overline{A + B}$$
$$Y = A * B$$

 

(8%)

3 min

 - b) Draw the required switch **circuits** and LED **circuits** to complete the circuit design for this problem. (These should be **circuit diagrams**, **not** layout diagrams.) Draw the switches in their **true** positions. Both a switch and an LED circuit symbol are shown here. (The switch shown is in its open position.) Do **not** draw unnecessary components.







## Exam 1P

\_\_\_\_\_  
Last Name, First Name

- (3%)  
5 min
8. c) Find the required **simplified** (MSOP or MPOS) equations for **ONLY** the following signals: the **T-FF input** and the **Y output**. If necessary (i.e., not done already done in the functional block diagram), also determine the equations necessary to **asynchronously** go to state **10** when **Restart (active-low)** goes true.

- (4%)  
5 min
- d) Design the complete circuit, using the T-FF, D-FF(s), and JK-FF(s), as described previously. All **inputs** and **outputs** of the circuit should be **clearly indicated coming into or out of** the below dashed box. Your design must include the circuitry necessary to **asynchronously** go to state **10** when **Restart (active-low)** goes true. Equations not calculated should be shown as an empty box with the necessary inputs and outputs.

Inputs

Outputs

## Exam 1P

\_\_\_\_\_  
Last Name, First Name

[11%] 9. In this problem you will design a 6-input MUX with no enable.

(1%)

3 min

- a) Draw a functional block diagram for a 6-input MUX with no enable. Use select lines labeled  $S_I$  and inputs labeled  $X_J$  (with the normally used subscripts). All  $S_I$  and  $X_J$  are active-high, as is the output  $Y$ .

(5%)

4 min

- b) Use a single 4-input MUX and a single 2-input MUX, both with single tri-state enables, to design a 6-input MUX with no enable. For each of these MUXes, use select lines labeled  $S_I$  and inputs labeled  $X_J$  (with the normally used subscripts). All  $S_I$  and  $X_J$  are active-high, as are these MUX outputs. Use the **minimum number** of additional SSI component. Choose the activation levels of the enables to **minimize** your additional SSI components.

(5%)

5 min

- c) Use a single 4-input MUX and as many 2-input MUXes as needed (but the minimum number), all with single **non**-tri-state enables, to design a 6-input MUX with no enable. For each of these MUXes, use select lines labeled  $S_I$  and inputs labeled  $X_J$  (with the normally used subscripts). All  $S_I$  and  $X_J$  are active-high, as are these MUX outputs. Use the **minimum number** of additional SSI component. Choose the activation levels of the enables to **minimize** your additional SSI components.