 


Exam 1P

10-Jun-19 -- 5:41 PM

*May the Schwartz
be with you!*


Last Name, First Name



PropaGator 1: World Champion,
2013 RoboBoat Competition

Instructions:

- Turn off all **cell phones** and other **noise making devices** and put away **all electronics**.
- Show **all** work on the **front** of the test papers. **Box** each answer. If you need more room, make a clearly indicated note on the front of the page, "**MORE ON BACK**", and use the back. The back of the page will **not** be graded without an indication on the front.
- You may **not** use any notes, HW, labs, other books, scratch paper, or calculators.
- This exam counts for **28%** of your total course grade.
- Read each question **carefully** and **follow the instructions**.
- The point values for problems may be changed at prof's discretion.
- You must pledge and sign this page in order for a grade to be assigned.
- **CLEARLY** write your name at the top of **this** test page (and, if you remove the staple, all others). Be sure your exam consists of **11** distinct pages. Sign your name and add the date below. (If we struggle to read your name, **you will lose points**.)
- For anything undefined, if necessary, state a reasonable assumption.
- Failure to follow the below rules will result in **NO** partial credit
 - The **base** (radix) of all number should be indicated with a **subscript** or **prefix**.
 - Truth tables, voltage tables, and timing simulations must be in **counting** order.
 - Label the inputs and outputs of each circuit with activation-levels.
 - For each mixed-logic circuit diagram, label inputs of **each** gate with the appropriate logic equations.
 - For K-maps, label **each** grouping with the appropriate equation.
 - Labels inside of parts must be provided whenever it can be confusing, e.g., they **MUST** be specified for MUXes and Decoders, but not for NANDs and ORs.
 - For each circuit design, equations must **not** be used as replacements for circuit elements.
 - Boolean expression answers must be in **lexical order**, (i.e., /A before A, A before B, & D₃ before D₂).

 

Good luck!

Please read carefully.

Go Gators!



PLEDGE: On my honor as a University of Florida student, I certify that I have neither given nor received any aid on this examination, nor I have seen anyone else do so.

SIGN YOUR NAME

DATE (27 Feb 2019)

Regrade comments below: Give page # and problem # and reason for the petition.	Pages	Available	Points
	2-3	19	
	4	10	
	5	11	
	6	11	
	7	10	
	8-9	17	
	10	15	
	11	8	
	TOTAL	100	

Exam 1P

Last Name, First Name

[13%] 1. Solve the following arithmetic problems. **Remember to show ALL work here and in EVERY problem on this exam.**

(4%) a) Determine the unsigned hexadecimal, octal, binary, and BCD representations of the number 415_{10} .
(I **strongly** recommend that you **check your work before** moving on to the next problem.)

4 min

Binary: _____

Octal: _____

Hex: _____

BCD: _____

(3%) b) Determine the **10-bit** signed magnitude, 1's complement, and 2's complement representations of the decimal number -415_{10} . (I **strongly** recommend that you **check your work before** moving on to the next problem.)

3 min

Signed Mag: _____

1's Comp: _____

2's Comp: _____

(3%) c) What is $-415_{10} - 128_{10}$ in **10-bit** 2's complement? You must use binary numbers to **derive** and determine the solution (not decimal). Hint: $128 = 2^7$. You must **show all work**.

3 min

$(-415_{10} - 128_{10})_{2 \text{ 10-bit 2's comp}}$: _____

Exam 1P

Last Name, First Name


- (3%) 1. d) What is $-415_{10} - 64_{10}$ in **10-bit** 2's complement? You must use binary numbers to **derive** and determine the solution (not decimal). Hint: $64 = 2^6$. You must **show all work**

3 min

$(-415_{10} - 64_{10})_2$ 10-bit 2's comp: _____

- [6%] 2. Directly implement the below equation with a mixed-logic circuit diagram, i.e., do **NOT** simplify the equation. Use only gates of the type shown here (or its mixed-logic equivalent). Minimize the **total number of gates**. You are free to choose the activation levels that are not already specified and that will optimize your solution. **Check twice** that you are correctly reading the equation!

6 min

 

$$UF = \overline{\overline{[(B + \bar{A}) * S * \bar{E}] + B * \bar{A}}} * \bar{L}$$

B()___

A(H)___

S()___

E()___

L()___

_____UF()

Exam 1P

 Last Name, First Name

- [4%] 3. **Simplify** the following logic equation using only Boolean identities, laws or theorems. (Note that this equation is **NOT** the same as in the previous problem. Show all steps. Give the solution in MSOP or MPOS form in **lexical** order.


[6 min]

$$UF = \overline{\left\{ \left[\overline{(B + \bar{A}) * S * \bar{E}} \right] + \overline{(B * \bar{A})} \right\} * \bar{L}}$$


- [6%] 4. Analyze the below circuits **carefully**. What are the equations for the outputs of the two similar circuits of parts a and b? Give the solution in MSOP or MPOS form in **lexical** order.

(%) [3 min]

a)

 

(%) [3 min] b)

 

Exam 1P


 Last Name, First Name

[11%] 5. Use the given multiplexers to **design mixed-logic circuit diagrams** that solve each of the below problems. **Be careful to read the equation correctly.** Choose activation levels for each signal (that has not already been assigned) to **minimize** the number of additional parts required. Use only SSI gates and add the **minimum** number necessary. Show all work. (The four below problems are **independent**, but the equations are identical.)

(4%)

6 min

 a) $UF_0 = (G + \bar{Y}) * \bar{M} + Y * (N * A) * \bar{M}$




(3%)

3 min

b) $UF_1 = (G + \bar{Y}) * \bar{M} + Y * (N * A) * \bar{M}$

(Note the **NON** tri-state enable.)

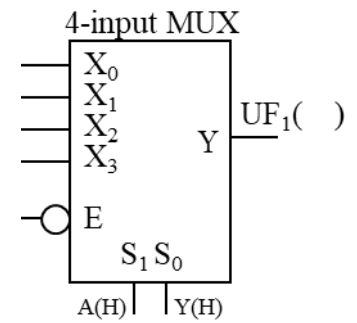


(2%)

2 min

c) $UF_2 = (G + \bar{Y}) * \bar{M} + Y * (N * A) * \bar{M}$

(Note **TRI**-state enable.)

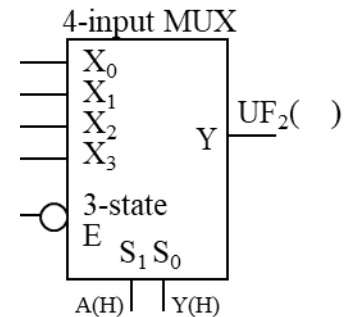


(2%)

4 min

d) $UF_3 = (G + \bar{Y}) * \bar{M} + Y * (N * A) * \bar{M}$

(Note the **NON** tristate enable.)

 

Exam 1P

Last Name, First Name

[11%] 6. Use the below equation for this problem.

$$Y = (\bar{A} + B + \bar{C} + \bar{D}) * (A + \bar{B} + C + \bar{D}) * (A + B + \bar{D}) * (B + \bar{C} + D) * (B + C + D)$$

(7%) a) Simply the above equation and put the result in **MPOS** form, in lexical order. Label **ALL** circles.

6 min

AB
CD _____

$Y_{MPOS} =$

(3%) b) If the terms ABCD=0111 and ABCD=1000, i.e., the textbook's d(7) and d(8), are **DON'T CAREs (X)**, determine the new **MSOP** equations, in lexical order. Label **ALL** circles.

3 min

AB
CD _____

$Y_{MSOP} =$

(1%) c) Are the above equations (in parts a and b) **equivalent**? Why or why not?

1 min

Exam 1P

Last Name, First Name

[10%] 7. Use the below circuit for this problem.

- (5%)
5 min
- a) Draw the **mixed-logic circuit** diagram to directly implement (i.e., do **NOT** simplify) the below equation using parts from any **one single chip**, with **A active-high**. Use the **minimum number of gates** from this **single** chip. (This should be a **circuit diagram**, not a layout diagram.)

$$X = \overline{\overline{A} + B * \overline{C}}$$

- (3%)
3 min
- b) Draw the required switch circuits and LED circuits to complete the circuit design for this problem. (These should be **circuit diagrams**, not layout diagrams.) Draw the switches in their **true** positions.

- (2%)
2 min
- c) Draw a **voltage timing** simulation diagram of the output of the **A** switch circuit when **the switch is moved** from **open to close**. Be sure to label both axes with appropriate scales including units.

Exam 1P

Last Name, First Name

- (4%) 8. c) Find the required **simplified** (MSOP or MPOS) equations for **T**, **K**, and **Y**. For the other equations, you do **not** need MSOP or MPOS equations, but you **must provide** correct SOP or POS for each.

5 min

- (4%) d) Design the complete circuit, using the T-FF, D-FF(s), and JK-FF(s), as described previously. All **inputs** and **outputs** of the circuit should be **clearly indicated coming into or out of** the below dashed box. Your design must include the circuitry necessary to **asynchronous** go to state “2” when **Restart (active-high)** goes true.

5 min

Inputs

Outputs


Exam 1P

 Last Name, First Name


[6%] 9. Design a 4-to-16 decoder with a single enable using only, if possible, the two below parts. If this is not possible, add a minimum number of only SSI gates in your design.

5 min

3-to-8 Decoder

 

3-to-8 Decoder

 


[9%] 10. Determine each of the below equations **in lexical order**. For parts a through d, assume that the dashed line is **not there**.

(1%)

2 min

a) $V = f_0(R, O)$

$V =$

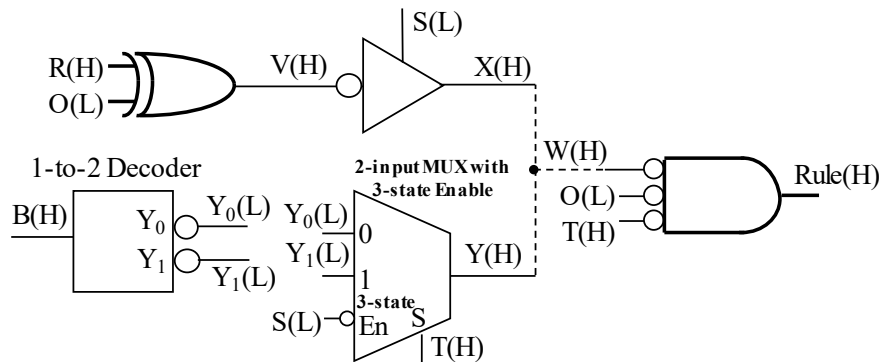

(2%)

3 min

b) $X = f_2(V, S)$

$X =$

(1%)

2 min

c) $Y_0 = f_3(B)$ and $Y_1 = f_4(B)$

$Y_0 =$

$Y_1 =$

(2%)

3 min

d) $Y = f_5(Y_0, Y_1, S, T)$

$Y =$

(3%)

3 min

e) If $X(H)$ and $Y(H)$ are connected (as shown with the dashed lines) and the combined signal is called $W(H)$, what is the equation for $W = f_6(V, Y_0, Y_1, S, T)$.

$W =$

Exam 1P

Last Name, First Name

[8%] 11. In this problem you will design two different 6-input multiplexers.

(1%)
2 min a) Draw a functional block diagram of a **6-input multiplexer with a single active-high enable**. All other inputs and outputs are also active-high. The inputs are X and S (with the normally used subscripts), the output is Y.

(3%)
4 min b) Design a **6-input multiplexer with a non-tri-state enable**. Use **two 2-input MUXes and one 4-input MUX**. Assume that each of these MUXes have **all** the **non-tri-state enables** (with any activation level) that you need, but do **not** use more than you need. Use no additional parts. If you can **not** solve it this way, use additional necessary parts for a **significant point reduction**.

(4%)
4 min c) Design a **6-input multiplexer with a tri-state enable**. Use the **minimum number** of **2-input MUXes and 4-input MUXes**. Assume that each of these MUXes have **all** the **tri-state enables** (with any activation level) that you need, but do **not** use more than you need. Use no additional parts. If you can **not** solve it this way, use additional necessary parts for a **significant point reduction**.