



*May the Schwartz
be with you!*

Exam 1P

Last Name, First Name

Instructions:

- Turn off all **cell phones** and other **noise making devices** and put away **all electronics**.
- Show **all** work on the **front** of the test papers. **Box** each answer. If you need more room, make a clearly indicated note on the front of the page, "**MORE ON BACK**", and use the back. The back of the page will **not** be graded without an indication on the front.
- You may **not** use any notes, HW, labs, other books, scratch paper, or calculators.
- This exam counts for **28%** of your total course grade.
- Read each question **carefully** and **follow the instructions**.
- The point values for problems may be changed at prof's discretion.
- You must pledge and sign this page in order for a grade to be assigned.
- **CLEARLY** write your name at the top of **this** test page (and, if you remove the staple, all others). Be sure your exam consists of **11** distinct pages. Sign your name and add the date below. (If we struggle to read your name, **you will lose points**.)
- For anything undefined, if necessary, state a reasonable assumption.
- Failure to follow the below rules will result in **NO** partial credit
 - The **base** (radix) of all number must be indicated with a **subscript** or **prefix**.
 - Truth tables, voltage tables, and timing simulations must be in **counting** order.
 - Label the inputs and outputs of each circuit with activation-levels.
 - For each mixed-logic circuit diagram, label inputs of **each** gate with the appropriate logic equations.
 - For K-maps, label **each** grouping with the appropriate equation.
 - Labels inside of parts must be provided whenever it can be confusing, e.g., they **MUST** be specified for MUXes and Decoders, but not for NANDs and ORs.
 - For each circuit design, equations must **not** be used as replacements for circuit elements.
 - Boolean expression answers must be in **lexical order**, (i.e., /A before A, A before B, & D₃ before D₂).

  

SubjuGator 8: Early CAD for 2019 RoboSub Competition

Good luck!

**Please read
carefully.**



PLEDGE: On my honor as a University of Florida student, I certify that I have neither given nor received any aid on this examination, nor I have seen anyone else do so.

SIGN YOUR NAME

DATE (2 July 2019)

Regrade comments below: Give page # and problem # and reason for the petition.

| Pages | Available | Points |
|-------|-----------|--------|
| 2-3 | 19 | |
| 4 | 10 | |
| 5 | 11 | |
| 6 | 11 | |
| 7 | 8 | |
| 8-9 | 17 | |
| 10 | 11 | |
| 11 | 13 | |
| TOTAL | 100 | |

Exam 1P

Last Name, First Name

[13%] 1. Solve the following arithmetic problems. **Remember to show ALL work here and in EVERY problem on this exam.**

(4%) a) Determine the unsigned hexadecimal, octal, binary, and BCD representations of the number 347_{10} .
[5 min] (I **strongly** recommend that you **check your work before** moving on to the next problem.)

Binary: _____

Octal: _____

Hex: _____

BCD: _____

(3%) b) Determine the **10-bit** signed magnitude, 1's complement, and 2's complement representations of
[3 min] the decimal number -347_{10} . (I **strongly** recommend that you **check your work before** moving on to the next problem.)

Signed Mag: _____

1's Comp: _____

2's Comp: _____

(3%) c) What is $-347_{10} + 384_{10}$ in **10-bit** 2's complement? You must use binary numbers to **derive** and
[3 min] determine the solution (not decimal). Hint: $384 = 256 + 128 = 2^8 + 2^7$. You must **show all work**.

$(-347_{10} + 384_{10})_{2 \text{ 10-bit 2's comp}}$: _____

Exam 1P

Last Name, First Name

(3%)
3 min

1. d) What is $-347_{10} - 128_{10}$ in **10-bit** 2's complement? You must use binary numbers to **derive** and determine the solution (not decimal). Hint: $128 = 2^7$. You must **show all work**

$(-347_{10} - 128_{10})_{2 \text{ 10-bit 2's comp:}}$ _____

[6%]
6 min

2. Directly implement the below equation with a mixed-logic circuit diagram, i.e., do **NOT** simplify the equation. Use only gates of the type shown here (**or** its mixed-logic equivalent). Minimize the **total number of gates**. You are free to choose the activation levels that are not already specified and that will optimize your solution. **Check twice** that you correctly read the equation!



$$USA = [W * (\overline{S + \overline{O} + C})] * [\overline{(\overline{C} + E) * R}]$$

W(H)____

S(L)____

O()____

C()____

____USA(L)

E(H)____

R(L)____

Exam 1P

Last Name, First Name

[4%]

5 min

3. **Simplify** the following logic equation using **only Boolean identities, laws or theorems**. (Note that this equation is **NOT** the same as in the previous problem. Show all steps. Give the solution in MSOP or MPOS form in **lexical** order. **Check twice** that you correctly read the equation!


$$USA = \overline{[W * (S + \bar{O} + C)] * [(\bar{C} + E) * R]}$$

[6%]

4. Analyze the below circuits **carefully**. What are the equations for the outputs of the two similar circuits of parts a and b? Give the solution in MSOP or MPOS form in **lexical** order.


(%)

3 min

 

(%)

3 min

 


Exam 1P

Last Name, First Name

- [11%] 5. Use the given multiplexers to **design mixed-logic circuit diagrams** that solve each of the below problems. **Be careful to read the equation correctly.** Choose activation levels for each signal (that has not already been assigned) to **minimize** the number of additional parts required. Use only SSI gates and add the **minimum** number necessary. Show all work. (The four below problems are **independent** of each other, but the equations are identical.)


(4%)
6 min

 a) $F_0 = (\bar{U} + T) * B * \overline{(A * \bar{L})}$




(2%)
3 min

 b) $F_1 = (\bar{U} + T) * B * \overline{(A * \bar{L})}$ (Note the **NON** tri-state enable.)




(2%)
2 min

 c) $F_2 = (\bar{U} + T) * B * \overline{(A * \bar{L})}$ (Note the **NON** tri-state enable.)



(3%)
4 min

d) $F_3 = (\bar{U} + T) * B * \overline{(A * \bar{L})}$ (Note the **NON** tristate enable.)

 

Exam 1P

Last Name, First Name

[11%] 6. Use the below equation for this problem.

$$Y = \bar{A} * \bar{B} * C * D + A * \bar{B} * D + A * B * \bar{C} + A * B * C * D + A * \bar{C} * D + B * C * \bar{D}$$

(7%) a) Simplify the above equation and put the result in **MSOP** form and lexical order. Label **ALL** circles.

7 min

AB
CD _____

$Y_{\text{MSOP}} =$

(3%) b) If the terms ABCD=0110 and ABCD=1010, i.e., the textbook's d(6) and d(10), are **DON'T CAREs (X)**, determine the new **MPOS** equations, in lexical order. Label **ALL** circles.

3 min

AB
CD _____

$Y_{\text{MPOS}} =$


(1%) c) Are the above equations (in parts a and b) **equivalent**? Why or why not?

1 min

Exam 1P

Last Name, First Name

- [8%] 7. In this problem, you will design a mixed-logic circuit diagram and some input and output circuits.
- (5%)
[5 min] a) Draw the **mixed-logic circuit** diagram to directly implement these two equations with the **minimum number of real gates**. (Real SSI gates were defined in class as all inputs having the same activation levels.) These should be **circuit diagrams**, not layout diagrams. The B input and X output must be active-high, and Y must be active-low, i.e., B(H), X(H), and Y(L). Choose the optimal (best) activation-level for A.
- $$X = A + \bar{B}$$
$$Y = \bar{A} * B$$
- (3%)
[3 min] b) Draw the required switch **circuits** and LED **circuits** to complete the circuit design for this problem. (These should be **circuit diagrams**, **not** layout diagrams.) Draw the switches in their **true** positions. Both a switch and an LED circuit symbol are shown here. (The switch shown is in its open position.) Do **not** draw unnecessary components.

 

[illegible]

Exam 1P

Last Name, First Name

- (4%) 8. c) Find the required **simplified** (MSOP or MPOS) equations for this circuit.

5 min

- (4%) d) Design the complete circuit, using the T-FF, D-FF(s), and JK-FF(s), as described previously. All **inputs** and **outputs** of the circuit should be **clearly indicated coming into or out of** the below dashed box. Your design must include the circuitry necessary to **asynchronously** go to state “0” when **Restart (active-low)** goes true.

Inputs

Outputs

A large dashed rectangular box intended for the student to draw their circuit design. The box is empty and occupies the central portion of the page below the question text.

Exam 1P

Last Name, First Name

- [11%] 9. Determine the appropriate equations in **lexical order** for each of the below circuits. Both of these circuits have MUXes with **tri-state** enables. All equations must be in lexical order.

- (2%)
3 min a) For Figure 1, if S(L) is **true**, determine the equation for $X = f_a(A, T, R)$, i.e., as a function of A, T, and R.

 


Fig 1: Circuit for parts a) – e).

- (0.5%)
1 min b) For Figure 1, if S(L) is **true**, determine the equation for $G = f_b(X, O)$, if S(L) is **true**.

- (0.5%)
2 min c) For Figure 1, if S(L) is **true**, determine the equation for $G = f_c(A, T, O, R)$.

- (2%)
2 min d) For Figure 1, if S(L) is **false**, determine the equation for $X = f_d(A, T, R)$, i.e., as a function of A, T, and R.

- (1%)
2 min e) For Figure 1, determine the equation for $G = f_e(A, T, O, R)$, i.e., as a function of A, T, O, and R, if S(L) is **false**.

- (4%)
3 min f) Determine the equation for $X = f_f(A, T, R, B, E, S, \bar{S})$, for the circuit to the right. Hint: First find equations for the top and bottom X's.

 


Fig 2: Circuit for parts f) – g).

- (1%)
2 min g) Determine the equation for $G = f_g(X, O)$.

Exam 1P

Last Name, First Name

[7%]

5 min

10. Design a 4-input MUX with an **active-low** **NON**-tristate enable, $E(L)$. Use the **minimum number** of 2-input MUXes and **no** other parts in your design. You may assume that the 2-input MUXes have one or more enables, of any activation-levels that you need. Label the MUX inputs as $X_i(H)$ and the MUX select lines as $S_j(H)$, and the output as $Y(H)$.

[6%]

5 min

11. Design a 2-to-4 decoder with an **active-low** enable, $E(L)$. Use the **minimum number** of 1-to-2 decoders and **no** other parts in your design. You may assume that the 1-to-2 decoders have one or more enables, of any activation-levels that you need. Label the decoder inputs as $X_i(H)$ and the decoder outputs as $Y_j(L)$.