

Exam 1

 Last Name, First Name

Instructions:

- Turn off all **cell phones, beepers** and other noise making devices.
- Show **all** work on the **front** of the test papers. **Box** each answer. If you need more room, make a clearly indicated note on the front of the page, "MORE ON BACK", and use the back. The back of the page will **not** be graded without an indication on the front.
- You may **not** use any notes, HW, labs, books, or calculators.
- This exam counts for 20% of your total grade.
- Read each question **carefully** and **follow the instructions**.
- You must pledge and sign this page in order for a grade to be assigned.
- The point values for problems may be changed at prof's discretion.
- Truth tables and voltage tables must be in **counting** order.
- Label the inputs and outputs of each circuit with activation-levels.
- For each mixed-logic circuit design, equations must **not** be used as replacements for circuit elements. Label inputs of **each gate** with the appropriate logic equations.
- Boolean expression answers must be in **lexical order**, (i.e., /A before A, A before B, & D₃ before D₂).
- For K-maps, label **each** grouping with the appropriate equation.
- Put your name at the top of **this** test page (and, if you remove the staple, all others). Be sure your exam consists of **11** distinct pages. Sign your name and add the date below.

*Good Evening!
Welcome!*

*Good luck &
Go Gators!!!*

PLEDGE: On my honor as a University of Florida student, I certify that I have neither given nor received any aid on this examination, nor I have seen anyone else do so.

 SIGN YOUR NAME

 DATE (4 October 2010)

Regrade comments below: Give page # and problem # and reason for the petition.

Page	Available	Points
2	10	
3	8	
4	8	
5-6	18	
7	13	
8	14	
9	11	
10	8	
11	10	
TOTAL	100	

Exam 1

Last Name, First Name

[10%] 1. Do the following arithmetic problems. **Remember to show ALL work here and in EVERY problem on this exam.**

(4%) a) Determine the unsigned hexadecimal, octal, binary, and BCD representations of the number 111_{10} .

3 min

Binary: _____

Octal: _____

Hex: _____

BCD: _____

(3%) b) Determine the **8-bit** signed magnitude, 1's complement, and 2's complement representations of the decimal number -111_{10} .

3 min

Signed Mag: _____

1's Comp: _____

2's Comp: _____

(3%) c) What is $74_{10} - 111_{10}$ in 8-bit 2's complement? You must use binary numbers to derive the solution (not decimal). Remember that you must **show all work.**

3 min

$(74_{10} - 111_{10})_{2\text{-bit } 2\text{'s comp}}$: _____

Exam 1

Last Name, First Name

- (3%) 1. d) What is $74_{10} + 111_{10}$ in 8-bit 2's complement? You must use binary numbers to derive and determine the solution (not decimal). Remember that you must **show all work**.

3 min

$(74_{10} + 111_{10})_2$ 8-bit 2's comp: _____

- [2%] 2. Divide the following **unsigned binary** numbers. Only three digits to the right of the binary point are required. The answer should be of the same type (i.e., unsigned binary).

4 min

$$1000\ 1001 \div 1101$$

- [3%] 3. Add the following **8-bit 2's complement** numbers. (Show all **carries** and work below.) What is the result in **8-bit 2's complement and in hexadecimal**? What is the result in **decimal**?

2 min


$$\begin{array}{r} 0100\ 1001 \\ +1111\ 1100 \\ \hline \end{array}$$

Exam 1


 Last Name, First Name

- [8%] 4. Determine the SOP or POS equations for the output Y in each of the below circuits. Please **look carefully** at each of the circuits.


8 min

 


$Y_1 =$ _____

 


$Y_2 =$ _____

 

$Y_3 =$ _____

 

$Y_4 =$ _____

 

$Y_5 =$ _____

Exam 1

Last Name, First Name

[18%] 5. Design a 1-to-2 decoder with an active-low (**non**-tri-state) enable. **All** other signals should be **active-high**.

(%) a) Draw a functional block diagram (showing all inputs and outputs) of the required decoder. I suggest you use subscripted variables where appropriate.

1 min

(%) b) Draw the truth table for this decoder.

2 min

(%) c) Determine the MSOP **or** MPOS equation(s) of this decoder.

2 min

(%) d) Draw the mixed-logic circuit diagram to implement this circuit.

2 min

(%) e) Draw a functional block diagram of a **2-to-4** decoder **WITHOUT** enable. Then design this decoder using **ONLY** 1-to-2 decoders (with **active-low** enables), if possible. If not possible, use a minimum of **SSI** gates in addition to 1-2 decoders.

4 min

1-to-2 decoder Functional Block Diagram

Exam 1

Last Name, First Name

- (%) 5. f) Draw a functional block diagram of a **2-to-4** decoder **WITH** active-low **enable**. Then design this decoder using 1-to-2 decoders (with **active-low** enables) and a **minimum** number of SSI gates. (Assume that each SSI gate costs 5¢ and each 1-to-2 decoder cost ~~10¢~~ ~~20¢~~).

4 min

- (%) g) Design a 3-to-8 decoder **WITH** active-low enable, using only **2-to-4** decoders **with enables** and a minimum number of SSI gates. (Assume that each SSI gate costs 5¢ and each 2-to-4 decoder cost ~~20¢~~ ~~50¢~~.)

4 min

Exam 1

 Last Name, First Name

[4%] 6. Find the MSOP **or** MPOS equivalent of the below Boolean expression. Show **ALL** work.

4 min

$$Y = \overline{\overline{A + B \times \overline{C}} \times (\overline{C} + D) \times E + \overline{F + \overline{G}} \times \overline{F}}$$

$$Y = \{ \{ \{ (A + (B * C)) * (C + D) \} * [E + (F + G)] * F \}$$

Y = _____

[9%] 7. Determine the MSOP **and** MPOS equivalent of the below Boolean expression.

6 min

$$W = (A + B + D) * (A + B + C + D) * (A + B + C) * (A + B + C + D) * (A + C + D)$$

W_{MSOP} = _____

W_{MPOS} = _____

Exam 1


 Last Name, First Name

[15%] 8. Use the given multiplexers to **design mixed-logic circuit diagrams** that solve each of the below problems. **Be careful to read the equation correctly.** Choose activation levels for each signal (that has not already been assigned) to **minimize** the number of additional parts required. Use the **minimum** number of additional SSI gates. Show all work. (The four below problems are independent.)

2 min

(%) a) $Y_0 = /A * B * /C + /A B C /D$


3 min

 

(%) b) $Y_1 = /A * B * /C + /A B C /D$

3 min


(Note the **tri-state** enable.)

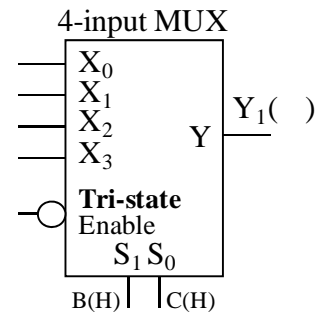

(%) c) $Y_2 = /A * B * /C + /A B C /D$

3 min


(Note the **NON** tri-state enable.)

 

(%) d) $Y_3 = /A * B * /C + /A B C /D$

3 min

(Note the **NON** tri-state enable.)

 

Exam 1

Last Name, First Name

- [8%] 9. Directly implement the below equation with a mixed-logic circuit diagram. (Do **NOT** simply the equation!) Use only one type gate, i.e., use as many of the **SAME** chips as needed (but with a minimum number of gates). Use the appropriate mixed-logic symbols. Pick whatever activation levels you want for the inputs and output, except **I** must be **active-high** and **O** must be **active-low**.

5 min

$$Go = \overline{\left[(I * \bar{E}) + E + (E * \bar{B}) \right]} \overline{(O + T)}$$

$Go = \{ \neg [(I * E) + E] + E * B \} * \neg (O + T)$

I(H)___

E()___

___Go()

B()___

O(L)___

T()___

- [3%] 10. Create next-state truth tables for the D-, T- and J-K Flip-Flops. These will help you in the next problem.



4 min

Exam 1

Last Name, First Name

- [8%] 11. Complete the timing diagram for the given circuit, i.e., fill in the values of Q1, Q0, and Y. Note that the T-FF and D-FF **both have bubbles** at the CLK input. Assume all propagation delays are 10ns (one grid). **All SET and CLR inputs are asynchronous.**

9 min

 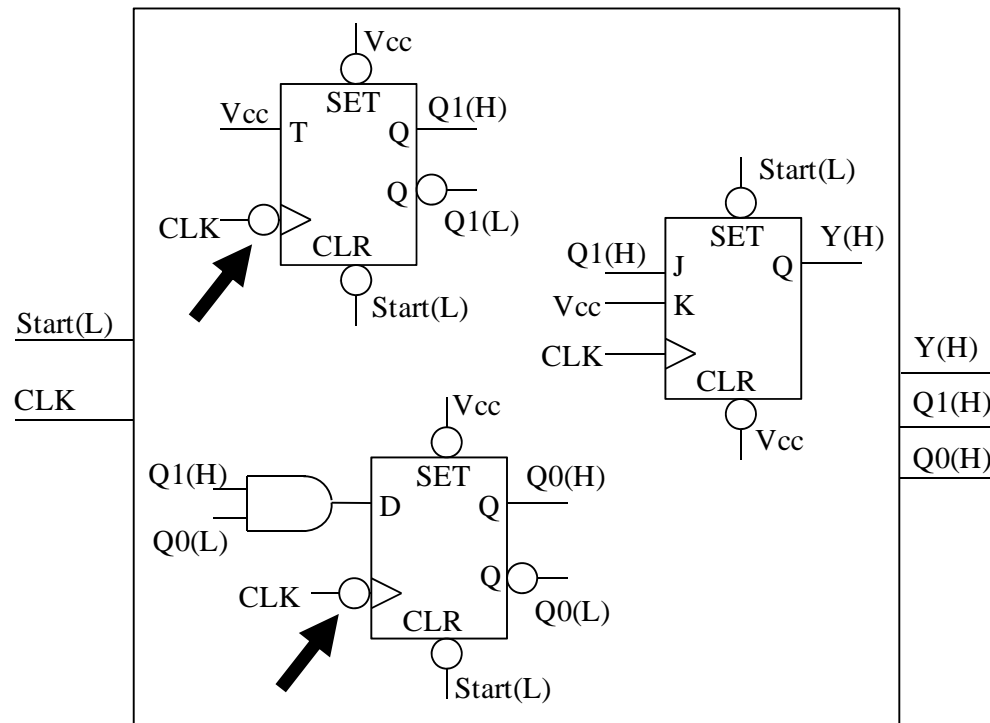

Exam 1

Last Name, First Name

[10%] 12. Use the given drawing of the **8-pin 74'Gator** chip to solve the below problems.


(5%)

4 min

- a) Draw the **mixed-logic circuit** diagram to implement the below two equations using parts from the 74'Gator chip shown. Also draw the required switch circuits and LED circuits. (These should be **circuit diagrams**, not layout diagrams.) Draw the switches in their **true** positions. A must be **active-high**, i.e., A(H).

$$X = /A + /B$$


$$Y = A * B$$

 



(5%)

5 min

 - b) Now draw a **layout** of the entire above circuit **including** each of the **switch and LED circuits**. A layout shows each of the parts as they appear on the breadboard. Include the needed switches, resistors (SIP and/or DIP), and LEDs. Label the wires for each of the inputs and outputs (A, B, X and Y) with their activation levels. I suggest that you **use labels** to replace long wires. The dark part of the switches in the figure are the parts that you move to change the switch's closure state. Draw the switches in their **true** positions.



LEDs

  

8-pin Chip

