

# Exam 1

\_\_\_\_\_  
 Last Name, First Name

**Instructions:**

- Turn off all **cell phones** and other noise making devices and put away **all electronics**.
- Show **all work** on the **front** of the test papers. **Box** each answer. If you need more room, make a clearly indicated note on the front of the page, "MORE ON BACK", and use the back. The back of the page will **not** be graded without an indication on the front.
- This exam counts for 20% of your total grade.
- Read each question **carefully** and **follow the instructions**.
- You may **not** use any notes, HW, labs, other books, or calculators.
- The point values for problems may be changed at prof's discretion.
- You must pledge and sign this page in order for a grade to be assigned.
- Put your name at the top of **this** test page (and, if you remove the staple, all others). Be sure your exam consists of **11** distinct pages. Sign your name and add the date below.
- For each circuit design, equations must **not** be used as replacements for circuit elements.
- For each mixed-logic circuit diagram, label inputs of each gate with the appropriate logic equations
- Truth tables and voltage tables must be in **counting** order.
- Label the inputs and outputs of each circuit with activation-levels.
- Boolean expression answers must be in **lexical order**,( i.e., /A before A, A before B, & D<sub>3</sub> before D<sub>2</sub>).
- For K-maps, label **each** grouping with the appropriate equation.



**CongreGators:** UF MIL's Swarm Robots.

**Please read  
carefully.**

**Good luck &  
Go Gators!!!**

**PLEDGE:** On my honor as a University of Florida student, I certify that I have neither given nor received any aid on this examination, nor I have seen anyone else do so.

\_\_\_\_\_  
 SIGN YOUR NAME

\_\_\_\_\_  
 DATE (8 Oct 2013)

Regrade comments below: Give page # and problem # and reason for the petition.

Pages	Available	Points
2-3	19	
4	13	
5	7	
6	11	
7	10	
8	11	
9	11	
10	12	
11	6	
<b>TOTAL</b>	<b>100</b>	

# Exam 1

\_\_\_\_\_  
Last Name, First Name

[15%] 1. Solve the following arithmetic problems. **Remember to show ALL work here and in EVERY problem on this exam.**

(4%) a) Determine the unsigned hexadecimal, octal, binary, and BCD representations of the number  $287_{10}$ .

4 min

Binary: \_\_\_\_\_

Octal: \_\_\_\_\_

Hex: \_\_\_\_\_

BCD: \_\_\_\_\_

(3%) b) Determine the **10-bit** signed magnitude, 1's complement, and 2's complement representations of the decimal number  $-287_{10}$ .

3 min

Signed Mag: \_\_\_\_\_

1's Comp: \_\_\_\_\_

2's Comp: \_\_\_\_\_

(2%) c) What is  $-256_{10} - 287_{10}$  in **10-bit** 2's complement? You must use binary numbers to **derive** and determine the solution (not decimal). You must **show all work**.

3 min

$(-256_{10} - 283_{10})_{2 \text{ 10-bit 2's comp}}$ : \_\_\_\_\_

# Exam 1

\_\_\_\_\_

Last Name, First Name

- (2%) 1. d) What is  $384_{10} - 287_{10}$  in **10-bit** 2's complement? You must use binary numbers to **derive** and determine the solution (not decimal). Remember that you must **show all work**.

4 min

$(384_{10} - 283_{10})_{2 \text{ 10-bit 2's comp}}$ : \_\_\_\_\_

- (4%) 1. e) Perform the requested operations in binary. If necessary,

4 min

$$\begin{array}{r} 10\ 0101 \\ \times \quad 101 \\ \hline \end{array}$$

$10\ 0101 \div 101$   
(Show 3 digits after the binary point)

- [4%] 2. Find the MSOP **or** MPOS equivalent of the below Boolean expression. Show **ALL** work.

5 min

$$Beat = \overline{\overline{L * \bar{S} * U}} + \overline{\overline{(\bar{L} + S) * U}}$$

Beat = \_\_\_\_\_

# Exam 1

\_\_\_\_\_  
 Last Name, First Name

[13%] 3. Answer the following questions.

(3%)

2 min

a) Sketch the bdf file so that it looks like what you would create in Quartus for the equation  $Y = (\neg A * B)$  with A(H), B(L), Y(L) using the **minimum number** of gates.

(3%)

3 min

b) Draw a **complete** timing diagram, exactly as Quartus would; include 10ns propagation delays, as Quartus would. Label the inputs and output and the time axis.



(4%)


2 min

c) Draw the required switch circuits and LED circuit to complete the circuit design for this problem. (These should be **circuit diagrams**, not layout diagrams.) Draw the switches in their **true** positions.


(3%)

5 min

 
d) Draw a **layout** of the entire above circuit **including** each of the **switch and LED circuits** for **part d** and the logic from **part b**. A layout shows each of the parts as they appear on the breadboard. Include the needed switches, resistors (SIP and/or DIP), and LEDs. I don't know what chip you used, so assume whatever pin numbers you want (for the 14-pin chip), along with the **normal** power and ground pins. Label the pin numbers **in part b**. Label the wires for each of the inputs and outputs (A, B, and Y) with their activation levels. I suggest that you **use labels** to replace long wires. The dark part of the switches in the figure are the parts that you move to change the switch's closure state. Draw the switches in their **true** positions.




14-pin Chip

 

Switches

 

LEDs

 


# Exam 1

Last Name, First Name

[7%]

5 min

 4. Directly implement the below equation with a mixed-logic circuit diagram. (Do **NOT** simplify the equation.) Use only gates of the 74HC00 (or their mixed-logic equivalents). Use the **minimum number of gates** required. Use the appropriate mixed-logic symbols. You are free to choose the activation levels for all signals. Label the parts and pin **numbers** for your circuit design.



$$Congr = (A + \bar{G}) * \overline{\{ [A * (T * \bar{O})] + R * \bar{S} \}}$$

A( )

G( )\_\_

T( )\_\_

\_\_Congr( )

O( )\_\_

R( )\_\_

S( )\_\_

# Exam 1

\_\_\_\_\_  
 Last Name, First Name

[6%] 5. Use only open-collector gates (of any **real** SSI-type gate) to directly implement the below equation. (Do **NOT** simply the equations.) **Show your work!**

(3%) a)  $G = (\bar{O} * U) + \bar{F}$ , with **O(H)** required.



3 min

(3%) b)  $G = (O + \bar{U}) * F$ , with **O(H)** required.

3 min

[5%] 6. Determine the sequence of outputs, for  $Q_1(H)$  and  $Q_0(H)$ , starting at  $Q_1Q_0=00$ . Assume the asynchronous clear,  $CLR(L)$ , is false and a series of clocks ( $CLK$ ) occur to create the sequence of outputs. Show **ALL** work. List the next 6 values in the sequence.

5 min

  

# Exam 1


\_\_\_\_\_  
 Last Name, First Name

[10%] 7. Use the given multiplexers to **design mixed-logic circuit diagrams** that solve each of the below problems. **Be careful to read the equation correctly.** Choose activation levels for each signal (that has not already been assigned) to **minimize** the number of additional parts required. Use the **minimum** number of additional SSI gates. Show all work. (The four below problems are **independent**.)

2 min


3 min

(3%) a)  $Y_0 = A*/B + /B*/C*D + /B*C*D$

 


3 min

 (3%) b)  $Y_1 = A*/B + /B*/C*D + /B*C*D$  (Note the **enable**.)




3 min

 (2%) c)  $Y_2 = A*/B + /B*/C*D + /B*C*D$  (Note the **enable** and **D(L)**.)



(2%) d)  $Y_3 = A*/B + /B*/C*D + /B*C*D$  (Note the mux **size**)

3 min

 

# Exam 1

\_\_\_\_\_  
 Last Name, First Name

[11%] 8. Solve the following Karnaugh Map Boolean Algebraic simplifications problems.

(6%) a) Simply the below equation and put the result in MSOP **and** form MPOS.

5 min

		CD			
		00	01	11	10
AB	00	1	1	0	1
	01	0	0	1	1
	11	1	0	1	1
	10	1	1	0	1

		CD			
		00	01	11	10
AB	00	1	1	0	1
	01	0	0	1	1
	11	1	0	1	1
	10	1	1	0	1

$Y_{MSOP} =$

$Y_{MPOS} =$

(5%) b) If the terms ABCD=0001, 1001, and 1011, i.e., the textbook's d(1,9,11), are **DON'T CAREs (X)**, determine the new MSOP **and** MPOS equations. Are the two **below** solutions equivalent? Explain why or why not.

5 min

		CD			
		00	01	11	10
AB	00	1	X	0	1
	01	0	0	1	1
	11	1	0	1	1
	10	1	X	X	1

		CD			
		00	01	11	10
AB	00	1	X	0	1
	01	0	0	1	1
	11	1	0	1	1
	10	1	X	X	1

$Y_{MSOP} =$

$Y_{MPOS} =$

Are the above equations **Equivalent?** Why or why not?




# Exam 1

Last Name, First Name

[11%] 9. Describe the function of two below circuits in parts a and b. Fill in appropriate mixed-logic signal names to clarify your description, to make the circuits mixed-logic circuit diagrams, and to complete the intended design.


(4%) a) The enables in this problem are **NOT** 3-state.

4 min

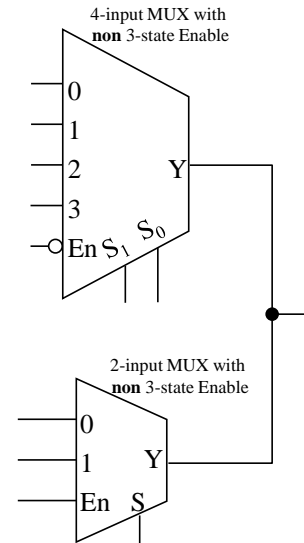

(4%) b) The enables in this problem **ARE** 3-state.

4 min

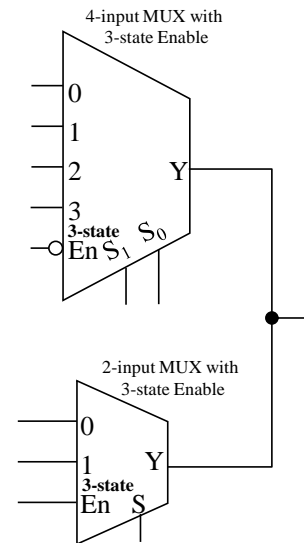

(3%) c) If adding an overall system enable on either the above circuits makes sense, then add (in a box or boxes **above**) SSI circuit(s) to create a system enable of the same type as the MUXes of the given problem (i.e., non 3-state or 3-state).

3 min

# Exam 1


\_\_\_\_\_

Last Name, First Name

[12%] 10. In this problem you will design several decoders.

(4%) a) Determine the truth table for the below **priority** encoder (where a higher subscript has a higher priority)? Also create a **functional** block diagram from the given block diagram.

5 min

 


(4%) b) Determine the equations for the encoder (use space above). Simplify the equations. Design a circuit (use space below) to implement this design. Use only SSI gates.

6 min

(4%) c) Which (if any) of the  $Z_i$  outputs are **true** for each of the following? Choose the normal (matching) activation-levels for the inputs and outputs (as you did in your MSI labs).

3 min

- 1)  $X_3X_2X_1X_0 = 0001$
- 2)  $X_3X_2X_1X_0 = 0000$
- 3)  $X_3X_2X_1X_0 = 1000$
- 4)  $X_3X_2X_1X_0 = 1011$

