

Exam 1

 Last Name, First Name

Instructions:

- Turn off all **cell phones, beepers** and other noise making devices.
- Show **all** work on the **front** of the test papers. **Box** each answer. If you need more room, make a clearly indicated note on the front of the page, "MORE ON BACK", and use the back. The back of the page will **not** be graded without an indication on the front.
- This exam counts for 33% of your total grade.
- Read each question **carefully** and **follow the instructions**.
- You may **not** use any notes, HW, labs, other books, or calculators.
- The point values for problems may be changed at prof's discretion.
- You must pledge and sign this page in order for a grade to be assigned.
- Put your name at the top of **this** test page (and, if you remove the staple, all others). Be sure your exam consists of **11** distinct pages. Sign your name and add the date below.
- For each circuit design, equations must **not** be used as replacements for circuit elements.
- For each mixed-logic circuit diagram, label inputs of each gate with the appropriate logic equations
- Truth tables and voltage tables must be in **counting** order.
- Label the inputs and outputs of each circuit with activation-levels.
- Boolean expression answers must be in **lexical order**, (i.e., /A before A, A before B, & D₃ before D₂).
- For K-maps, label **each** grouping with the appropriate equation.

Good afternoon! Welcome!

Please read carefully.

Good luck & Go Gators!!!

PLEDGE: On my honor as a University of Florida student, I certify that I have neither given nor received any aid on this examination, nor I have seen anyone else do so.

 SIGN YOUR NAME

 DATE (1 July 2010)

Regrade comments below: Give page # and problem # and reason for the petition.

Page	Available	Points
2-3	19	
4	15	
5	10	
6	9	
7	10	
8	8	
9	11	
10-11	18	
TOTAL	100	

Exam 1

Last Name, First Name

[15%] 1. Do the following arithmetic problems. **Remember to show ALL work here and in EVERY problem on this exam.**

(4%) a) Determine the unsigned hexadecimal, octal, binary, and BCD representations of the number 55_{10} .

3 min

Binary: _____

Octal: _____

Hex: _____

BCD: _____

(3%) b) Determine the **7-bit** signed magnitude, 1's complement, and 2's complement representations of the decimal number -55_{10} .

2 min

Signed Mag: _____

1's Comp: _____

2's Comp: _____

(2%) c) What is $60_{10} - 55_{10}$ in **7-bit** 2's complement? You must use binary numbers to **derive** and determine the solution (not decimal). Remember that you must **show all work**.

3 min

$(60_{10} - 55_{10})_2$: _____

Exam 1

Last Name, First Name

- (3%) 1 d) What is $92_{10} - 55_{10}$ in **8-bit** 2's complement? You must use binary numbers to **derive** and determine the solution (not decimal). Remember that you must **show all work**.

3 min

$(92_{10} - 55_{10})_{2 \text{ 8-bit 2's comp}}$: _____

- (3%) 1 e) What is $92_{10} + 55_{10}$ in **8-bit** 2's complement? You must use binary numbers to **derive** and determine the solution (not decimal). Remember that you must **show all work**.

3 min

$(92_{10} + 55_{10})_{2 \text{ 8-bit 2's comp}}$: _____

- [2%] 2. What is the difference in a functional compilation/simulation of a Quartus design and a full compilation/timing simulation?

2 min

- [1%] 3. When designing a circuit in Quartus with an active-low output, what special technique is required? Circle one of the below.

1 min

a) Use an inverter b) Nothing special c) Use a bubble d) Both a and c e) None of these

- [1%] 4. When designing a circuit in Quartus with an active-low input, what special technique is required? Circle one of the below.

1 min

a) Use an inverter b) Nothing special c) Use a bubble d) Both a and c e) None of these

Exam 1

Last Name, First Name

[7%] 5. Use a 2-input NAND gate (drawn as a NAND gate) with inputs A(H) and B(L) and output C(H) for this problem.

(2%) a) Draw the mixed-logic circuit diagram. What is the mixed logic equation?

2 min

(2%) b) Draw the truth table and the voltage table (both in **counting order**).

2 min

(3%) c) Draw the Quartus simulation that would **easily** confirm the correct operation of this 2-input NAND gate.

2 min

A ___

B ___

C ___

[8%] 6. Directly implement the below equation with a mixed-logic circuit diagram. Use only one type gate, i.e., use as many of the **SAME** chips as needed (but with a minimum number of gates). Use the appropriate mixed-logic symbols. Pick whatever activation levels you want for the inputs and output, except **S** and **U** must be **active-high**.

5 min

$$Go = \overline{(\bar{S} * \bar{U} + B)} + \overline{(T * \bar{E})} * (A + M)$$

S(H)___

U(H)___

B()

T()___

_____Go()

E()___

A()___

M()___

Exam 1

 Last Name, First Name

[10%] 7. Use the below circuit for this problem.

(5%)


4 min

- a) Draw the **mixed-logic circuit** diagram to implement the below two equations using parts from the 74'Gator chip show. Also draw the required switch circuits and LED circuits. (These should be **circuit diagrams**, not layout diagrams.) Draw the switches in their **true** positions. A must be active-high, i.e., A(H).

$$X = A * B$$

$$Y = A + B$$

74'Gator

 


(5%)

5 min

- b) Now draw a **layout** of the entire above circuit **including** each of the **switch and LED circuits**. A layout shows each of the parts as they appear on the breadboard. Include the needed switches, resistors (SIP and/or DIP), and LEDs. Label the wires for each of the inputs and outputs (A, B, X and Y) with their activation levels. I suggest that you **use labels** to replace long wires. The dark part of the switches in the figure are the parts that you move to change the switch's closure state. Draw the switches in their **true** positions.


74'Gator

 


Switches



LEDs

 

8-pin Chip

 

Exam 1


 Last Name, First Name

- [9%] 8. Use the given multiplexers to **design mixed-logic circuit diagrams** that solve each of the below problems. **Be careful to read the equation correctly.** Choose activation levels for each signal to **minimize** the number of additional parts required. Use the **minimum** number of additional gates. Show all work. (The two below problems are **independent**.)

2 min


(4%) a) $Y_0 = A*/B + /B*C + /A*/B*D$

3 min

 

(5%) b) $Y_1 = A*/B + /B*C + /A*/B*D$

4 min

 

Exam 1

Last Name, First Name

[4%] 9. Find the MSOP **or** MPOS equivalent of the below Boolean expression. Show **ALL** work.

4 min

$$Y = \overline{(A + \overline{\overline{C}} + D)} * \overline{\overline{\overline{A}} + \overline{\overline{B}} * C * D}$$

Y = _____

[6%] 10. Determine the MSOP **and** MPOS equivalent of the below Boolean expression.

6 min

$$W = (\overline{A} + \overline{C} + D) * (A + \overline{B} + \overline{C}) * (B + C + \overline{D}) * (B + D)$$

$W_{MSOP} =$ _____


$W_{MPOS} =$ _____

Exam 1

 Last Name, First Name

- [8%] 11. Design an 11-input MUX using as many of the given elements as needed. The two given MUXs each have **tri-state** (T.S.) outputs such that if the chip is disabled, the output is tri-stated (high impedance). Note that you need a similar tri-state enable for the 11-input MUX. Use labels instead of wires. First try to minimize number of required components and then minimize the cost. The cost for available single MUXs are: big MUX=37¢ and little MUX=24¢. The cost per single **gates** are Inverter=3¢, 2-input NAND=7¢, and 2-input NOR=13¢. The 11-input MUX must work as expected, e.g., if $S_3S_2S_1S_0 = j$, then $Y = X_j$, $j=0,1,\dots,10$.

8 min

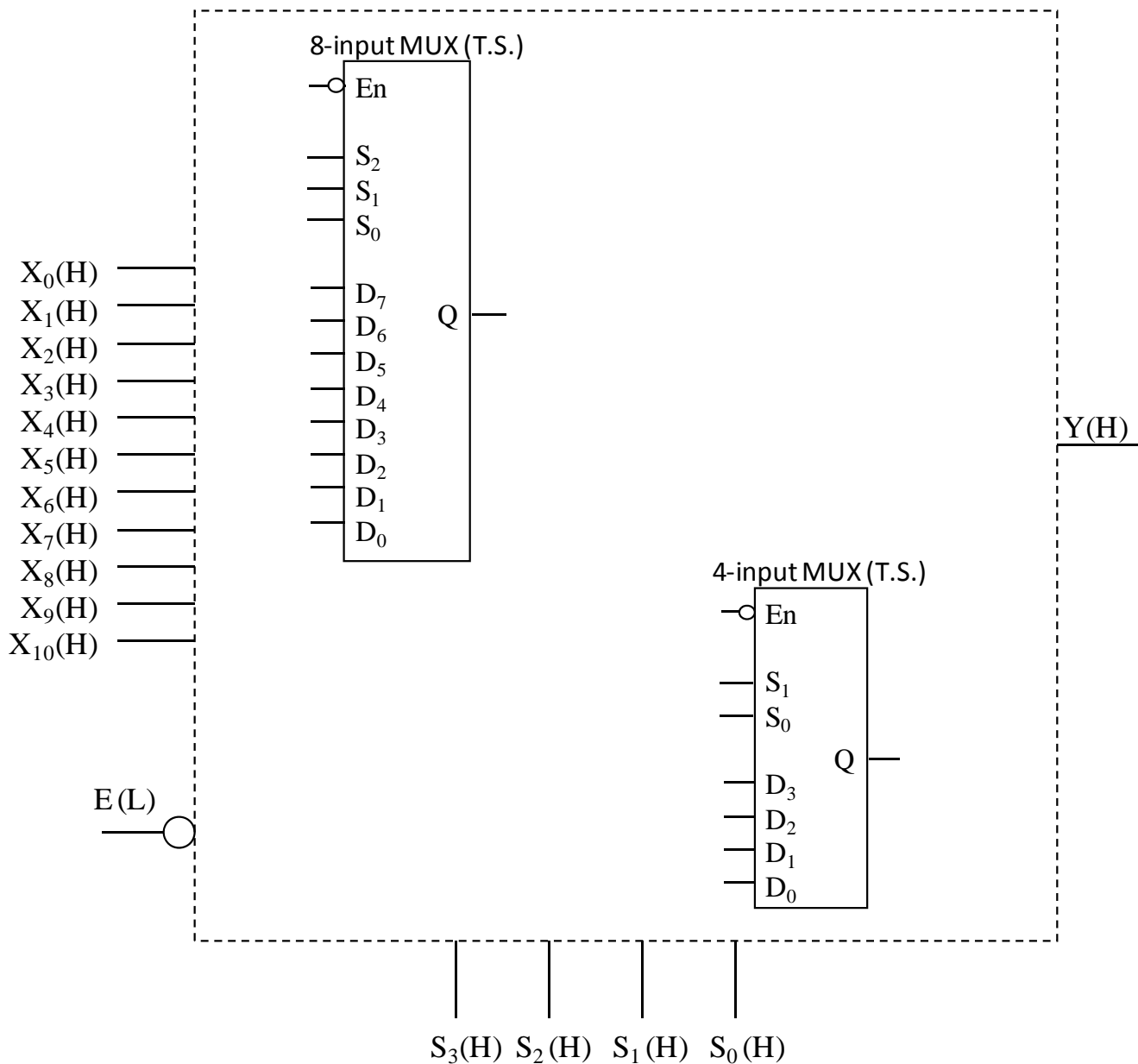

Exam 1

 Last Name, First Name

[11%] 12. What is the **logic equation** of each of the following signals **in terms of the given signals**?
 Put all answers in SOP or POS form in **proper lexical order**. **Show your work!** Reminder:
 There are **no** activation levels in a logic equation.

(2%) a) $E(L) = f_E(A(L), B(H))$

2 min Answer: $E =$ _____

(4%) b) $G(H) = f_G(C(L), D(H), E(L), F(H))$


3 min Answer: $G =$ _____

(4%) c) $K(H) = f_K(G(H), J(L), I(H))$

2 min Answer: $K =$ _____

(1%) d) $N(H) = f_N(I(H), G(H))$


2 min Answer: $N =$ _____

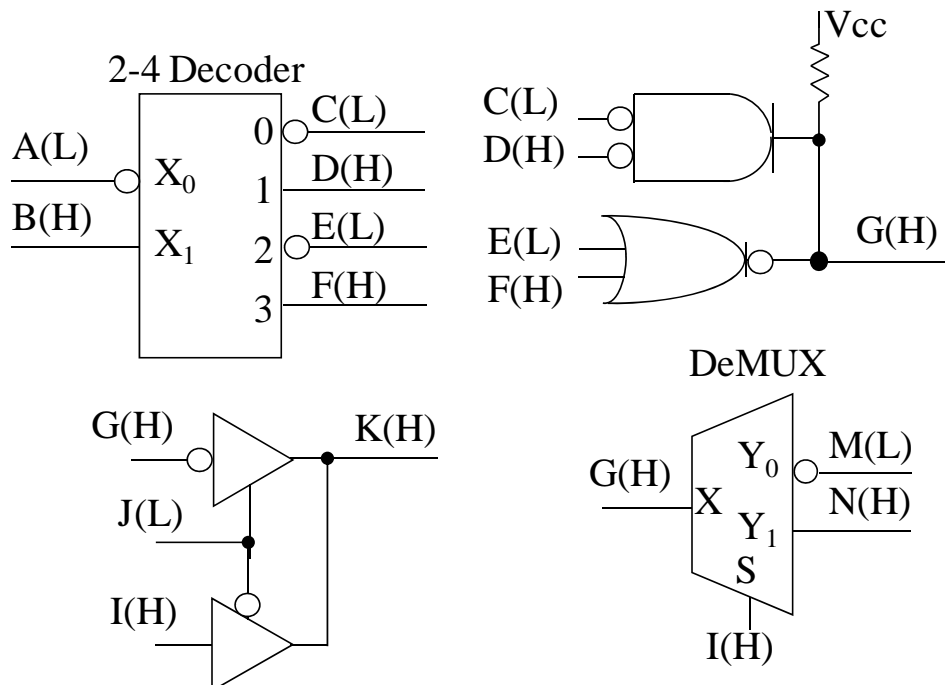

Exam 1


Last Name, First Name

[18%] 13. Design a system that counts as shown. The system must **asynchronously** reset to state “101” when **Start** (active-low) goes true. Use a JK-FF for the **most** significant bit of the counter, a D-FF for the **least** significant bit, and a T-FF for **any other** bits you might need. An output **Bad** (active-high), should be true if the count somehow gets to a value that is not in the sequence. Note: All the given FFs have **asynchronous** clear and set inputs.

 

(1%) a) Determine the excitation tables for a JK-FF and a T-FF.

3 min

 

4 min

(6%) b) Complete the next-state **truth table** (in counting order).

													.
													.
													.
													.
													.
													.
													.
													.
													.
													.
													.
													.
													.
													.
													.

(1%) c) Draw a functional **block diagram** (showing **all** the inputs, **all** the outputs, and the functional blocks). Put your design in a box with the inputs and outputs going into or out of the box, on the left or right, respectively. This is **not** a circuit diagram.

2 min

Exam 1

Last Name, First Name

(6%) 13. d) Find the required **simplified** equations. Show **all** work.

6 min

(4%) e) Design the complete counter circuit, **minimizing** the total number of components, but using the JK-FF and D-FF [and T-FF(s), if necessary] as described above. All inputs and outputs of the circuit should be clearly indicated **coming into or out of the** below box. Your design must include the circuitry necessary to re-start the counter to the required $Q_2Q_1Q_0 = 101$ state **asynchronously**, after the **Start(L)** signal goes true. It should also include **Bad(H)**.

5 min

