


Exam 1

 Last Name. First Name

Instructions:

- Turn off all cell phones and other noise making devices.
- Show all work on the front of the test papers. **Box** each answer. If you need more room, make a clearly indicated note on the front of the page, "MORE ON BACK", and use the back. The back of the page will not be graded without an indication on the front.
- This exam counts for 33% of your total grade.
- Read each question carefully and follow the instructions.
- You may not use any notes, HW, labs, other books, or calculators.
- The point values for problems may be changed at prof's discretion.
- You must pledge and sign this page in order for a grade to be assigned.
- Put your name at the top of this test page (and, if you remove the staple, all others). Be sure your exam consists of 15 distinct pages. Sign your name and add the date below.
- For each circuit design, equations must not be used as replacements for circuit elements.
- For each mixed-logic circuit diagram, label inputs of each gate with the appropriate logic equations
- Truth tables and voltage tables must be in **counting** order.
- Label the inputs and outputs of each circuit with activation-levels.
- Boolean expression answers must be in **lexical order**,(i.e., /A before A, A before B, & D₃ before D₂).
- For K-maps, label each grouping with the appropriate equation.

Please read carefully.

 

PropaGator: UF's Autonomous Surface Vehicle (Robot Boat with quadcopter)

Good luck & Go Gators!!!

PLEDGE: On my honor as a University of Florida student, I certify that I have neither given nor received any aid on this examination, nor I have seen anyone else do so.

 SIGN YOUR NAME

 DATE (2 July 2013)

Regrade comments below: Give page # and problem # and reason for the petition.

Problem	Available	Points
1	11	
2	15	
3	6	
4	4	
5	22	
6	8	
7	10	
8	16	
9	8	
TOTAL	100	

Exam 1

Last Name, First Name

[11%] 1. Solve the following arithmetic problems. **Remember to show ALL work here and in EVERY problem on this exam.**

(4%) a) Determine the unsigned hexadecimal, octal, binary, and BCD representations of the number 311_{10} .

4 min

Binary: _____

Octal: _____

Hex: _____

BCD: _____

(3%) b) Determine the **10-bit** signed magnitude, 1's complement, and 2's complement representations of the decimal number -311_{10} .

2 min

Signed Mag: _____

1's Comp: _____

2's Comp: _____

(2%) c) What is $128_{10} - 311_{10}$ in **10-bit** 2's complement? You must use binary numbers to **derive** and determine the solution (not decimal). Remember that you must **show all work**.

3 min

$(128_{10} - 311_{10})_{2 \text{ 10-bit 2's comp}}$: _____

Exam 1

Last Name, First Name

(2%) 1. d) What is overflow? Explain and give an example.

2 min

[15%] 2. Answer the following short questions. Show **ALL** work.

(1%) a) In a Quartus simulation, what does 0 mean? What does 1 mean?

1 min

(4%) b) Draw a circuit like you would in a Quartus schematic entry [bdf] file to implement the equation $Y = A*/B$, where A and Y are active-low and B is active-high. Use the **minimum** number of gates.

2 min

(3%) c) Draw a **complete** timing diagram, exactly as Quartus would; include 10ns propagation delays, as Quartus would. Label the inputs and output and the time axis.

3 min

A timing diagram grid consisting of a vertical solid line on the left and a series of horizontal dashed lines. Vertical dashed lines are spaced evenly across the grid, representing time intervals. The grid is intended for drawing a timing diagram with 10ns propagation delays.

Exam 1


Last Name, First Name

- (4%) 2. d) Draw the required switch circuits and LED circuit to complete the circuit design for this problem. (These should be **circuit diagrams**, not layout diagrams.) Draw the switches in their **true** positions.




2 min

- (3%) e) Draw a **layout** of the entire above circuit **including** each of the **switch and LED circuits** for **part d** and the logic from **part b**. A layout shows each of the parts as they appear on the breadboard. Include the needed switches, resistors (SIP and/or DIP), and LEDs. I don't know what chip you used, so assume whatever pin numbers you want (for the 14-pin chip), along with the **normal** power and ground pins. Label the pin numbers **in part b**. Label the wires for each of the inputs and outputs (A, B, and Y) with their activation levels. I suggest that you **use labels** to replace long wires. The dark part of the switches in the figure are the parts that you move to change the switch's closure state. Draw the switches in their **true** positions.

5 min

 

14-pin Chip

   

Exam 1

Last Name, First Name

- [6%] 3. Directly implement the below equation with a mixed-logic circuit diagram. (Do **NOT** simplify the equation.) Use only real (as specified in class) gates. Use the **minimum number of gates** required. Use the appropriate mixed-logic symbols. You are free to choose the activation levels for signals that do not already have specified activation-levels.

5 min

$$Propa = \overline{\overline{\overline{(G + \bar{A}) * \bar{T}} * \bar{O} * R}}$$

G(L)___

A()___

T(L)___

___Propa(L)

O(H)___

R()___

- [4%] 4. Find the MSOP **or** MPOS equivalent of the below Boolean expression. Show **ALL** work.

5 min

$$Propa = \overline{\overline{\overline{(G + \bar{A}) * \bar{T}} * \bar{O} * R}}$$

Propa = _____

Exam 1

Last Name, First Name

(~3%) 5. c) Find the required **simplified** (MSOP or MPOS) equations.


4 min

(~4%) 9. d) Design the complete circuit, **minimizing** the total number of components, but using the JK-FF, T-FF, and D-FF(s) (if necessary), as described previously. All **inputs** and **outputs** of the circuit should be **clearly indicated coming into or out of** the below box. Your design must include the circuitry necessary to **asynchronous** re-start the system at “11” when the **Start** (active-low) signal goes true and show the active-high output **Boom** when the output is 00 or 10.

5 min

Inputs

Outputs

 


Exam 1

Last Name, First Name

5. e) **Modify your solution** in parts a) through d) to generate the following sequence of outputs (with all bits active-high). The system must **asynchronously** reset to the state with output 4 when **Start (active-low)** goes true. (The rest of this is identical to part a, except that Boom should be true if the output is 1 or 3.) Repeated from part a: Use a **T-FF** for the **most** significant bit of your design, a **JK-FF** for the **least** significant bit, and a D-FF(s) for **any other** bits you might need. An output, **Boom** (active-high), should be true if the count is 00 or 10. ~~The least significant count bit, Q_0 , should be active-high; all other count bit(s) must be active-low.~~

2 min

 


(~2%)

3 min

- i) Draw a functional **block diagram** (showing **all** the inputs, **all** the outputs, and the functional blocks). Put your design in a box with the inputs and outputs going into or out of the box, on the left or right, respectively. This is **not** a circuit diagram.

Inputs

 

Outputs

(~2%)

5 min

- ii) Complete the next-state **truth table (in counting order)** **or** add columns to the

														.
														.
														.
														.
														.
														.
														.
														.
														.
														.
														.
														.
														.
														.
														.
														.
														.
														.

table in **part b**.

Exam 1

Last Name, First Name

Exam 1

Last Name, First Name

(~2%) 5. iii) Find the required **simplified** (MSOP or MPOS) equations.


3 min

(~3%) iv) Design the complete circuit for the problem in part e or **modify the design** in part d.

3 min

Inputs

Outputs

 

Exam 1


Last Name, First Name

- [8%] 6. Use the given multiplexers to **design mixed-logic circuit diagrams** that solve each of the below problems. **Be careful to read the equation correctly.** Choose activation levels for each signal (that has not already been assigned) to **minimize** the number of additional parts required. For parts a and b, use the **minimum** number of additional SSI gates. Show all work. (The three below problems are **independent**.)

(3%)

3 min

 
- a) $UF_0 = B*/O*/T + /T*S$ (Note the active-low **NON** tri-state enable.)



(3%)

3 min

 
- b) $UF_1 = B*/O*/T + /T*S$ (Note that there is no enable.)




(2%)

3 min

 - c) Use the MUX and up to two of the **open collector** parts shown here, but **no other** components. Note that this is the same equation and MUX as in part b.



$$UF_2 = B*/O*/T + /T*S$$

 

Exam 1

Last Name, First Name

[10%] 7. Use the below equation for this problem.

$$Y = (\bar{A} + B + \bar{C}) * (\bar{A} + B + C + D) * (A + \bar{B} + C) * (A + B + \bar{C}) * (A + B + \bar{D}) * (A + B + D) * (A + \bar{C} + \bar{D})$$

(7%) a) Simply the below equation and put the result in MPOS **and** form MSOP.

7 min

CD
AB _____

CD
AB _____

$Y_{\text{MPOS}} =$

$Y_{\text{MSOP}} =$

(3%) b) If the terms ABCD=0110 and ABCD=1000, i.e., the textbook's d(6,8), are **DON'T CAREs (X)**, determine the new MPOS **and** MSOP equations. Are these solutions equivalent? Explain why or why not.

3 min

CD
AB _____

CD
AB _____

$Y_{\text{MPOS}} =$

$Y_{\text{MSOP}} =$

Equivalent?:

Exam 1

Last Name, First Name

[16%] 8. In this problem you will design several decoders.

(~2%)

2 min

- a) Draw a truth table (with wild cards [-] or don't cares [X], if necessary) and a functional block diagram of a **1-to-2 Decoder** with no enable. The input(s) should be labeled X and the output(s) Y, both with proper subscripts, if necessary. All signals should be active-high.

(~2%)

2 min

- b) Derive the equation(s) and design the circuit for the **1-to-2 Decoder** with no enable. Use only SSI (AND, NAND, OR, etc.) gates.

(~2%)

3 min

- c) Draw a functional block, derive the equation(s), and design the circuit for the **1-to-2 Decoder** with an active-high enable. You must use the decoder from part b. Use the minimum number of additional SSI gates.

Exam 1

Last Name, First Name

- (~2%) 8. d) Draw a truth table (with wild cards [-] or don't cares [X], if necessary) and a functional block diagram of a **2-to-4 Decoder with** an active-high enable. The input(s) should be labeled X and the output(s) Y, both with proper subscripts, if necessary. All signals should be active-high.

3 min

- (~4%) e) Design the circuit for the **2-to-4 Decoder with** an active-high enable. Use only the decoders from part b or c and use SSI gates **ONLY** if necessary.

4 min

- (~4%) 8. f) Design the circuit for a **3-to-8 Decoder with** an active-high enable. Use only **2-to-4 decoders** with **3 enables**, $E_0(L)$, $E_1(H)$, and $E_2(H)$, i.e., one of the enables is active-low and two enables are active-high. Use SSI gates **ONLY** if necessary.

4 min


Exam 1

Last Name, First Name

[8%] 9. What are the (SOP or POS) equations for the outputs of the following circuits?


(1%)

1 min

 


(1%)

1 min

 

(3%)

3 min

 

(3%)

3 min

