

**May the Schwartz
be with you!**


Exam 1



Last Name, First Name

Instructions:

- Turn off all **cell phones** and other noise making devices.
- Show **all** work on the **front** of the test papers. **Box** each answer. If you need more room, make a clearly indicated note on the front of the page, "MORE ON BACK", and use the back. The back of the page will **not** be graded without an indication on the front.
- This exam counts for 33% of your total grade.
- Read each question **carefully** and **follow the instructions**.
- You may **not** use any notes, HW, labs, other books, or calculators, computers, or any electronic devices.
- The point values for problems may be changed at prof's discretion.
- You must pledge and sign this page in order for a grade to be assigned.
- Boolean expression answers must be in **lexical order**, (i.e., /A before A, A before B, & D₃ before D₂).
- **CLEARLY** write your name at the top of **this** test page (and, if you remove the staple, all others). Be sure your exam consists of **13** distinct pages. Sign your name and add the date below. (If we struggle to read your name, you will lose points.)
- Failure to follow the below rules will result in **NO** partial credit
 - The **base** (radix) of all number should be indicated with a subscript or prefix.
 - Truth tables, voltage tables, and timing simulations must be in **counting** order.
 - Label the inputs and outputs of each circuit with activation-levels.
 - For each mixed-logic circuit diagram, label inputs of **each** gate with the appropriate logic equations.
 - For K-maps, label **each** grouping with the appropriate equation.
 - For each circuit design, equations must **not** be used as replacements for circuit elements.
 - Boolean expression answers must be in **lexical order**, (i.e., /A before A, A before B, & D₃ before D₂).

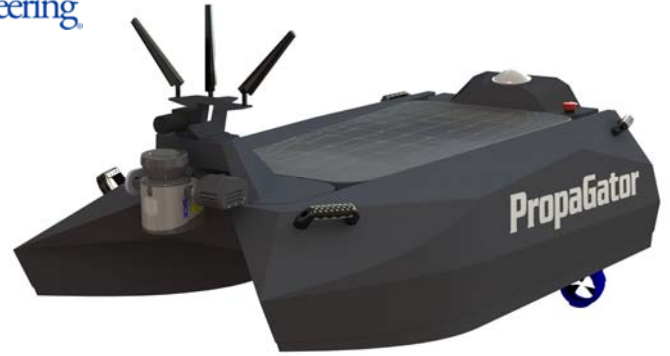

PropaGator 2: UF's PropaGator (Autonomous Surface Vehicle) for RoboBoat competition



PropaGator 2 front view

PLEDGE: On my honor as a University of Florida student, I certify that I have neither given nor received any aid on this examination, nor I have seen anyone else do so.

SIGN YOUR NAME

DATE (30 June 2015)

Regrade comments below: Give page # and problem # and reason for the petition.	Problem	Available	Points
•	1	12	
•	2	14	
•	3	7	
•	4-5	11	
•	6	21	
•	7	5	
•	8	11	
•	9	10	
•	10	9	
•	TOTAL	100	

Exam 1

Last Name, First Name

[12%] 1. Solve the following arithmetic problems. **Remember to show ALL work here and in EVERY problem on this exam.**

(4%) a) Determine the unsigned hexadecimal, octal, binary, and BCD representations of the number 251_{10} .

4 min

Binary: _____

Octal: _____

Hex: _____

BCD: _____

(3%) b) Determine the **10-bit** signed magnitude, 1's complement, and 2's complement representations of the decimal number -251_{10} .

2 min

Signed Mag: _____

1's Comp: _____

2's Comp: _____

(2%) c) What is $511_{10} - 251_{10}$ in **10-bit** 2's complement? You must use binary numbers to **derive** and determine the solution (not decimal). Remember that you must **show all work**. (Hint: $256+255=511$) Please **circle** your answer.

3 min

Exam 1

Last Name, First Name

- (3%) 1. d) What is $511_{10} + 251_{10}$ in **10-bit** 2's complement and **11-bit** 2's complement? You must use binary numbers to **derive** and determine the solution (not decimal). Remember that you must **show all work**. Please **circle** your answers.

3 min

10-bit

11-bit

- [14%] 2. Answer the following short questions. Show **ALL** work.

- (4%) a) Draw a circuit like you would in a Quartus schematic entry [bdf] file to **DIRECTLY** implement (i.e., do **NOT** simplify) the equation $Y = \overline{(\overline{A} * B)}$, where A is active-low, and B and Y are active-high. Use the **minimum** number of gates.

2 min

- (3%) b) Draw a **complete** timing diagram, exactly as Quartus would; include 10ns propagation delays, as Quartus would. Label the inputs and output and the time axis.

3 min



- (4%) c) Draw the required switch circuits and LED circuit to complete the circuit design for this problem. The circuits should do **nothing else**. (These should be **circuit diagrams**, not layout diagrams.) Draw the switches in their **true** positions.

2 min


Exam 1

Last Name, First Name

14-pin Chip




Switches

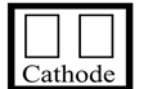

LEDs


(3%)
5 min

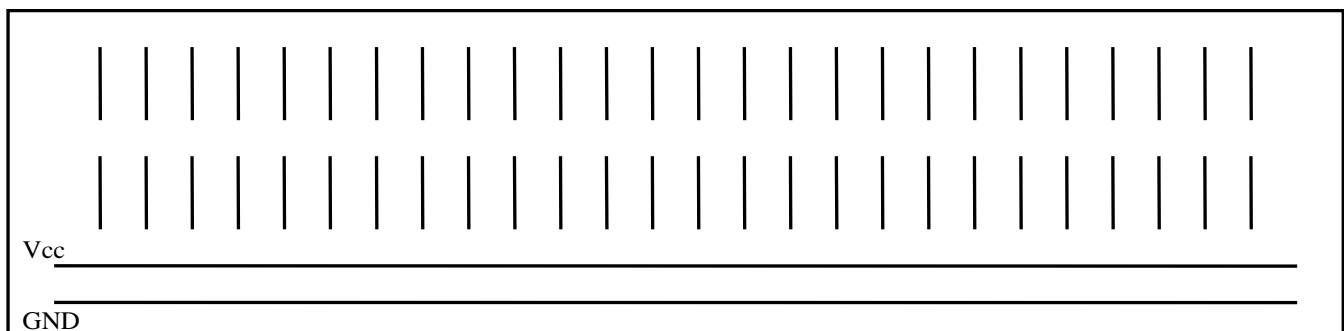2. d) Draw a **layout** of the entire above circuit **including** each of the **switch and LED circuits** for **part c** and the logic from **part a**. A layout shows each of the parts as they appear on the breadboard. Include the needed switches, resistors (SIP and/or DIP), and LEDs. I don't know what chip you used, so assume whatever pin numbers you want (for the 14-pin chip), along with the **normal** power and ground pins. Label the pin numbers **in part a**. Label the wires for each of the inputs and outputs (A, B, and Y) with their activation levels. I suggest that you **use labels** to replace long wires. The dark part of the switches in the figure are the parts that you move to change the switch's closure state. Draw the switches in their **true** positions.



[7%]
5 min

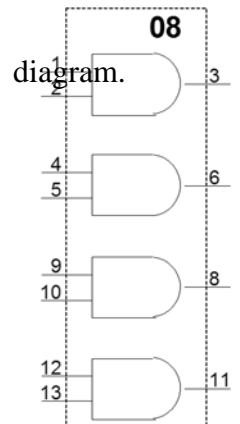3. Directly implement the below equation with a mixed-logic circuit (Do **NOT** simplify the equation.) Use only gates of the 74HC08 (or their mixed-logic equivalents). **Only if necessary**, you can also use other SSI components. Use the **minimum number of gates** required. Use the appropriate mixed-logic symbols. You are free to choose the activation levels that will optimize your solution. (No pin numbers are necessary.)



$$Soccer = \overline{\overline{(G + \overline{O}) * U} + S * \overline{A}}$$

G()__

O()__

U()__

S()__

A()__

_Soccer()

Exam 1

Last Name, First Name

- [4%] 4. Find the MSOP **or** MPOS equivalent of the below Boolean expression. Show **ALL** work. (Please verify that you are correctly reading the equation. Note that Ball, One and the second Num each have 3 bars above them.)

5 min

$$Gators = \left\{ \left[UF + \overline{(Soft * \overline{Ball})} \right] * \overline{(Num + \overline{One})} \right\} + \left[UF * \overline{(Base + \overline{Ball})} * \overline{(\overline{Num} + \overline{Three})} \right]$$


Gators = _____

- [7%] 5. What are the (SOP or POS) equations for the outputs of the following circuits? Lexical order is **NOT** necessary for these problems.

(4%)

4 min


a)

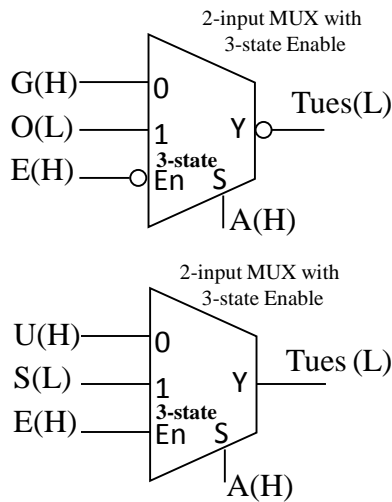

(3%)

4 min

b)

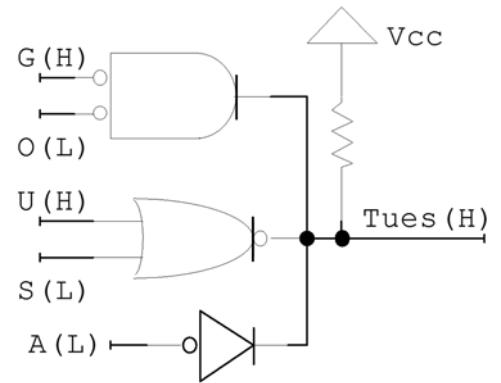

Exam 1

Last Name, First Name

(a-d 10%) 6. c) Find the required **simplified** (MSOP or MPOS) equations.

3 min

(a-d 10%)

5 min

d) Design the complete circuit, **minimizing** the total number of components, but using the T-FF, JK-FF, and D-FF(s) (if necessary), as described previously. All **inputs** and **outputs** of the circuit should be **clearly indicated coming into or out of** the below dashed box. Your design must include the circuitry necessary to **asynchronous** re-start the system at “5” when the **Start** (active-low) signal goes true.

Inputs

Outputs



Exam 1

Last Name, First Name

- (e-f 4%) 6. e) Use the table in part b (or make a new table) to create the same counter, but this time use a **JK-FF** for the **least** significant bit of your design, a **T-FF** for the next more significant bit (if necessary), and a D-FF(s) for **any other** bits you might need. Find the required **simplified** (MSOP or MPOS) equations.

4 min

- (e-f 4%) f) Design the complete circuit as you did in part d, but this time for the design described in part e.

4 min

Inputs

Outputs



Exam 1

 Last Name, First Name

- (g-i 7%) 6. i) Design the complete circuit as you did in part d and f, but this time for the design described in parts g-h.

4 min





- [5%] 7. Use the below equation for this problem.

$$Y = (\bar{A} + \bar{B} + \bar{C})(\bar{A} + \bar{C})(A + B)(\bar{B})(B + C)$$

Use K-maps to simply the equation and put the result in MSOP **and** form MPOS.

5 min

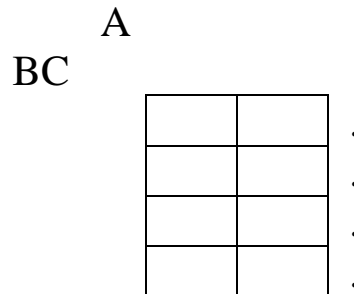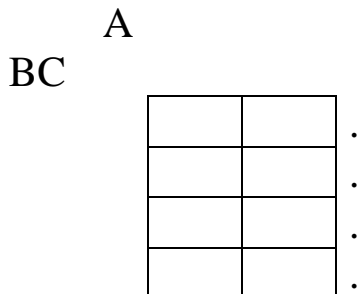

$Y_{MSOP} =$ _____

$Y_{MPOS} =$ _____

Exam 1

Last Name, First Name

[12%] 8. Use the below equation for this problem.

$$Y = \bar{A}BCD + \bar{A}\bar{C}\bar{D} + A\bar{B}\bar{C} + A\bar{B}\bar{D} + ABD + \bar{B}C\bar{D} + B\bar{C}D$$

(6%) a) Use K-maps to simply the equation and put the result in MSOP **and** form MPOS. Are these solutions (in part a) equivalent? Explain why or why not.

7 min

CD
AB _____

CD
AB _____

$Y_{MSOP} =$

$Y_{MPOS} =$

Equivalent?:

(5%) b) If the terms $ABCD=0001$ and $ABCD=1000$, i.e., the textbook's d(1,8), are **DON'T CAREs (X)**, determine the new MSOP **and** MPOS equations. Are these solutions (in part b) equivalent? Explain why or why not.

3 min

CD
AB _____

CD
AB _____

$Y_{MSOP} =$

$Y_{MPOS} =$

Equivalent?:


Exam 1

Last Name, First Name

- [10%] 9. Design a **3-to-8 Decoder with a single enable** using as many of the given **2-to-4 Decoders** with the enables (E1, E2, and E3) as necessary. Use the minimum number of **2-to-4 Decoders** and a minimum number of SSI (AND, NOR, NOT, etc.) gates necessary. (Note that all the enables on the **2-to-4 Decoders** must be true in order for the device to behave like a decoder.)

7 min

2-to-4 Decoder

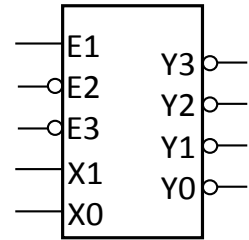

Inputs

A large dashed rectangular box intended for the student to draw their circuit design.

Outputs


Exam 1

Last Name, First Name

[9%] 10. Use the given multiplexers to **design mixed-logic circuit diagrams** that solve each of the below problems. **Be careful to read the equation correctly.** Choose activation levels for each signal (that has not already been assigned) to **minimize** the number of additional parts required. Use the **minimum** number of additional SSI gates. Show all work. (The three below problems are **independent**.)


(4%) a) $UF_0 = G*/A * (T*/O + O*/R*S + T*S)$

4 min

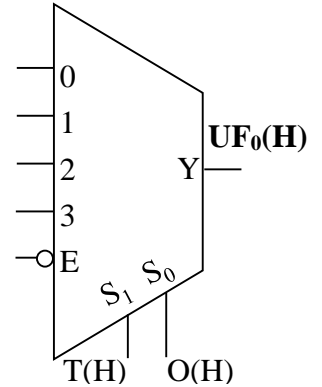

(3%) b) $UF_1 = G*/A * (T*/O + O*/R*S + T*S)$

3 min

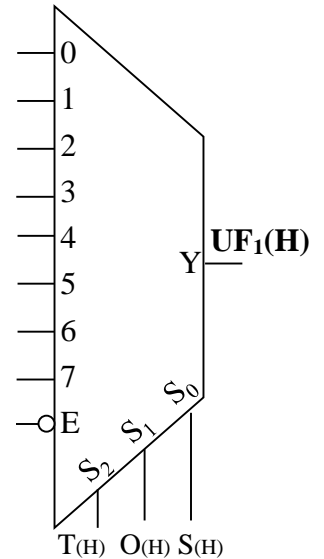

(2%) b) $UF_2 = G*/A * (T*/O + O*/R*S + T*S)$ (Note that the output is **active-low**.)

3 min

