



Exam 1

 Last Name, First Name

May the Schwartz be with you!

Instructions:

- Turn off all **cell phones** and other **noise making devices** and put away **all electronics**.
- Show **all work** on the **front** of the test papers. **Box** each answer. If you need more room, make a clearly indicated note on the front of the page, "MORE ON BACK", and use the back. The back of the page will **not** be graded without an indication on the front.
- This exam counts for 33% of your total grade.
- Read each question **carefully** and **follow the instructions**.
- You may **not** use any notes, HW, labs, other books, or calculators, computers, or any electronic devices.
- The point values for problems may be changed at prof's discretion.
- You must pledge and sign this page in order for a grade to be assigned.
- **CLEARLY** write your name at the top of **this** test page (and, if you remove the staple, all others). Be sure your exam consists of **11** distinct pages. Sign your name and add the date below. (If we struggle to read your name, you will lose points.)
- Failure to follow the below rules will result in **NO** partial credit
 - * The **base** (radix) of all number should be indicated with a **subscript** or **prefix**.
 - * Truth tables, voltage tables, and timing simulations must be in **counting** order.
 - * Label the inputs and outputs of each circuit with activation-levels.
 - * For each mixed-logic circuit diagram, label inputs of **each** gate with the appropriate logic equations.
 - * For K-maps, label **each** grouping with the appropriate equation.
 - * Labels inside of parts must be provided whenever it can be confusing, e.g., they **MUST** be specified for MUXes and Decoders, but not for NANDs and ORs.
 - * For each circuit design, equations must **not** be used as replacements for circuit elements.
 - * Boolean expression answers must be in **lexical order**, (i.e., /A before A, A before B, & D₃ before D₂).



SubjuGator 8 CAD image for the 2016 RoboSub Competition.



PLEDGE: On my honor as a University of Florida student, I certify that I have neither given nor received any aid on this examination, nor I have seen anyone else do so.

 SIGN YOUR NAME

 DATE (28 June 2016)

Regrade comments below: Give page # and problem # and reason for the petition.

Problem	Available	Points
1	12	
2	14	
3	7	
4	9	
5	4	
6	15	
7	18	
8	9	
9	12	
TOTAL	100	

Exam 1

Last Name, First Name

[12%] 1. Solve the following arithmetic problems. **Remember to show ALL work here and in EVERY problem on this exam.**

(4%) a) Determine the unsigned hexadecimal, octal, binary, and BCD representations of the number 311_{10} .

4 min

Binary: _____

Octal: _____

Hex: _____

BCD: _____

(3%) b) Determine the **10-bit** signed magnitude, 1's complement, and 2's complement representations of the decimal number -311_{10} .

2 min

Signed Mag: _____

1's Comp: _____

2's Comp: _____

(2%) c) What is $192_{10} - 311_{10}$ in **10-bit** 2's complement? You must use binary numbers to **derive** and determine the solution (not decimal). You must **show all work**. (Hint: $128+64=192$) Please **circle** your answer.

3 min

$(192_{10} - 311_{10})_{2 \text{ 10-bit 2's comp}}$: _____

Exam 1

Last Name, First Name

- (2%) 1. d) What is $-192_{10} - 311_{10}$ in **10-bit** 2's complement? You must use binary numbers to **derive** and determine the solution (not decimal). You must **show all work**.

3 min

$(-192_{10} - 311_{10})_2$ 10-bit 2's comp: _____


- [14%] 2. Answer the following short questions. Show **ALL** work.

- (4%) a) Draw a circuit like you would in a Quartus schematic entry [bdf] file to **DIRECTLY** implement (i.e., do **NOT** simplify) the equation $Y = \overline{(\overline{A} + B)}$, where A is active-high, and Y is active-low. B's activation level is intentionally unspecified, i.e., your choice. Use the **minimum** number of gates.

2 min

- (3%) b) Draw a **complete** timing diagram, exactly as Quartus would; include 10ns propagation delays, as Quartus would. Label the inputs and output and the time axis.

3 min

 

- (4%) c) Draw the required switch circuits and LED circuit to complete the circuit design for this problem. The circuits should do **nothing else**. (These should be **circuit diagrams**, not layout diagrams.) Draw the switches in their **true** positions.




2 min

Exam 1

Last Name, First Name

(3%)
5 min

   2. d) Draw a **layout** of the entire above circuit **including** each of the **switch and LED circuits** for **part c** and the logic from **part a**. A layout shows each of the parts as they appear on the breadboard. Include the needed switches, resistors (SIP and/or DIP), and LEDs. I don't know what chip(s) you used, so assume whatever pin numbers you want (for the 14-pin chip), along with the **normal** power and ground pins. Label the pin numbers **in part a**. Label the wires for each of the inputs and outputs (A, B, and Y) with their activation levels. I suggest that you **use labels** to replace long wires. The dark part of the switches in the figure are the parts that you move to change the switch's closure state. Draw the switches in their **true** positions.



[7%]
5 min

3. Directly implement the below equation with a mixed-logic circuit diagram. (Do **NOT** simplify the equation.) Use only gates of the 74HC02 (or their mixed-logic equivalents). **Only if necessary**, you can also use other SSI components. Use the **minimum number of gates** required. Use the appropriate mixed-logic symbols. You are free to choose the activation levels that will optimize your solution. (No pin numbers are necessary.)

$$Thx = \{ [(B * \bar{A} + S) * E] + \bar{B} + \bar{A} * L \} * L$$


B()__

A()__

S()__

E()__

L()__

 


__Thx()

Exam 1


Last Name, First Name

[7%] 4. What are the (SOP or POS) equations for the outputs of the following circuits? Please use lexical order.

(4%)
4 min

 

(3%)
4 min

 

(2%)
3 min

c) What is the equation if the two outputs Soft and Ball are connected with a wire? Assume this combined signal is called **Go** and that it is active-high, i.e., **Go(H)**. Put this SOP or POS solution in lexical order.

[4%]
5 min

5. Find the MSOP or MPOS equivalent of the below Boolean expression. Show ALL work. (Please verify that you are correctly reading the equation.) Note that this equation is not identical to the equation in part 3.

$$Thx = \left\{ \overline{\left[(B * \bar{A} + S) * E \right]} + \bar{B} + \bar{A} * L \right\} * L$$

Thx = _____

Exam 1

Last Name, First Name

6. c) Find the required **simplified** (MSOP or MPOS) equations.

5 min

- d) Design the complete circuit, **minimizing** the total number of components, but using the T-FF, JK-FF, and D-FF(s) (if necessary), as described previously. All **inputs** and **outputs** of the circuit should be **clearly indicated coming into or out of** the below dashed box. Your design must include the circuitry necessary to **asynchronous** re-start the system at “3” when the **Start** (active-high) signal goes true. The **Seven** (active-low) output must be true when the “count” is “7.”

5 min

Inputs

Outputs





Exam 1

 Last Name, First Name

[18%] 7. Design the following multiplexers. The select lines must work as they normally do in selecting the proper MUX inputs.



- (4%) a) Design a **5-input MUX** with **no enable** using only MUXes of the two types given. Assume that a 4-input MUX costs 2.5 times more than a 2-input MUX. Design the minimum cost solution. If possible, use **nothing** else! (If this is not possible, use the minimum number of additional SSI gates.)

5 min

  

- (4%) b) Design a **5-input MUX** with **non 3-state enable** using only MUXes of the two types given. Assume that a 4-input MUX costs 2.5 times more than a 2-input MUX. Design the minimum cost solution. If possible, use **nothing** else! (If this is not possible, use the minimum number of additional SSI gates.)

5 min

 
 


Exam 1

 Last Name, First Name



- (5%) 7. c) Design a **6-input MUX** with **non 3-state enable** using only MUXes of the two types given. Assume that a 4-input MUX costs 2.5 times more than a 2-input MUX. Design the minimum cost solution. If possible, use **nothing** else! (If this is not possible, use the minimum number of additional SSI gates.)

5 min

  

- (5%) d) Design a **6-input MUX** with **NO** enable using only MUXes of the two types given. (Note that the activation-level of enable on the 2-input MUX has changed.) Assume that a 4-input MUX costs 2.5 times more than a 2-input MUX. Design the minimum cost solution. If possible, use **nothing** else! (If this is not possible, use the minimum number of additional SSI gates.)

5 min

  

Exam 1

Last Name, First Name

[9%] 8. Use the below equation for this problem.

$$Y = (\bar{A} + B + \bar{C} + D) * (\bar{A} + B + C) * (A + B + \bar{C} + \bar{D}) * (A + B + C) * (\bar{B} + C + \bar{D})$$

(5%) a) Use K-maps to simply the equation and put the result in MPOS **and** form MSOP. Are these solutions (in part a) equivalent? Explain why or why not.

7 min

CD
AB _____

CD
AB _____

$Y_{MPOS} =$

$Y_{MSOP} =$

Equivalent?:

(4%) b) If the terms $ABCD=1000$ and $ABCD=1010$, i.e., the textbook's d(8,10), are **DON'T CARES (X)**, determine the new MPOS **and** MSOP equations. Are these solutions (in part b) equivalent? Explain why or why not.

4 min

CD
AB _____

CD
AB _____

$Y_{MPOS} =$

$Y_{MSOP} =$

Equivalent?:



Exam 1

Last Name, First Name


[12%] 9. Use the given multiplexers to **design mixed-logic circuit diagrams** that solve each of the below problems. **Be careful to read the equation correctly.** Choose activation levels for each signal (that has not already been assigned) to **minimize** the number of additional parts required. Use the **minimum** number of additional SSI gates. Show all work. (The three below problems are **independent**.)

2 min

(4%)

4 min

 
- a) $X_0 = (\overline{U + \overline{F}}) * S + \overline{(U + \overline{B} + J)} = /(\overline{U + F}) S + /(\overline{U + B} + J)$
Please note that the MUX has a **tri-state enable**.



(4%)

4 min

 - b) $X_1 = (\overline{U + \overline{F}}) * S + \overline{(U + \overline{B} + J)} = /(\overline{U + F}) S + /(\overline{U + B} + J)$
Please note that the MUX has a **NON** tri-state enable.



(4%)

3 min

- c) $X_2 = (\overline{U + \overline{F}}) * S + \overline{(U + \overline{B} + J)} = /(\overline{U + F}) S + /(\overline{U + B} + J)$
Please note that **J is active-low** and the MUX has a **NON** tri-state enable.

