

*Note: Late HW is **not** accepted!*

1. Use a Quartus simulation to show that an S-R latch can be made using two NAND gates.
2. Use a Quartus simulation to show that an S-R latch can be made using two NOR gates.
3. Derive the characteristic equations and excitation tables for each type of flip-flop. See Table 12-9 in your Roth textbook.
4. Roth textbook problems:
 - 5th, 6th and 7th edition: 11.1, 11.3, 11.8, 11.9
 - 5th edition: 11.21
 - 6th and 7th edition: 11.26