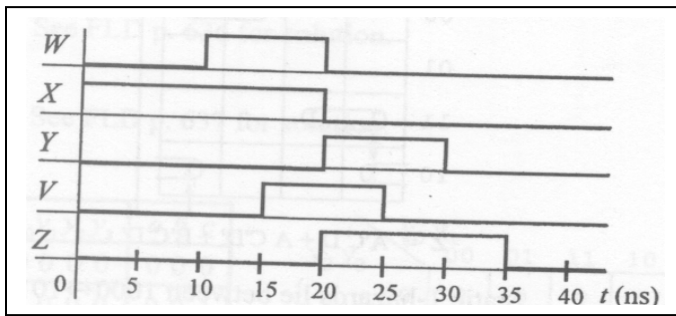



Homework 11 Solutions

Roth Book Problems


8.1



8.3 (a)

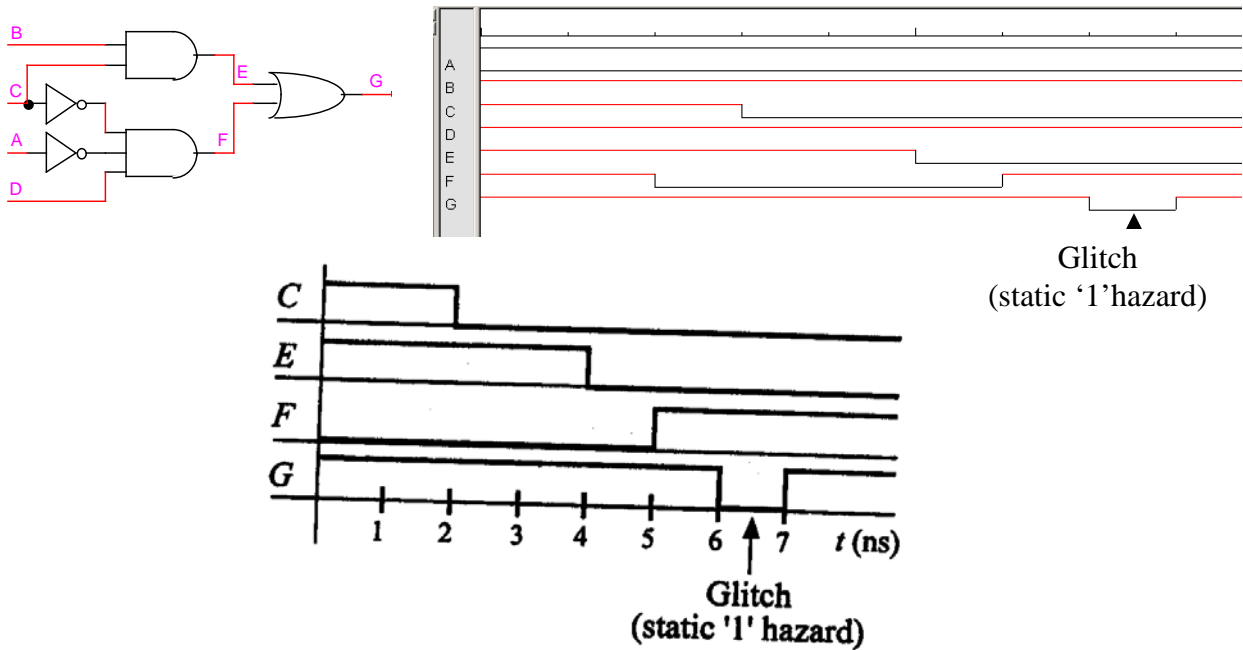

8.3 (b).

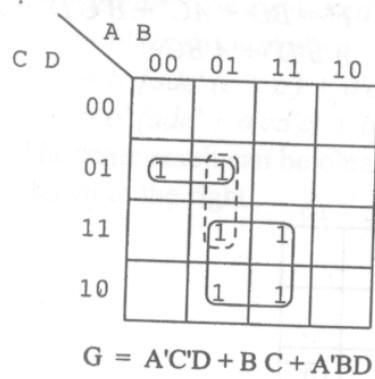

Homework 11 Solutions

Lam Book Problems


4.20

of CS inputs that can be driven when low = $I_{OL(74LS02)} / -I_{IL(Mem)} = 8mA/40\mu A = 200$

of CS inputs that can be driven when high = $-I_{OH(74LS02)} / I_{IH(Mem)} = 0.4mA/40\mu A = 10$

FAN OUT = $\min(F_{OL}, F_{AH}) = \underline{10}$

4.23

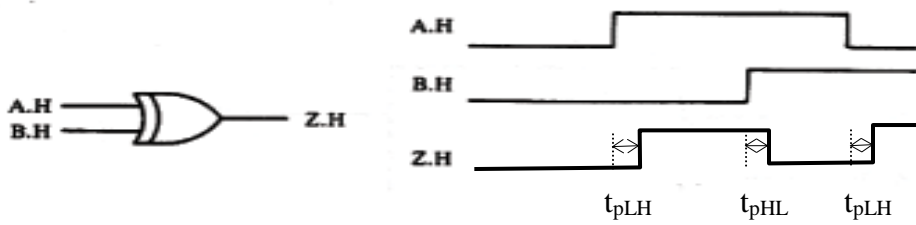

4.24

