

12.7 using JK for Q2, T for Q1, and D for Q0

C	B	A	C ⁺	J	K
0	0	0	X	X	X
0	0	1	0	0	X
0	1	0	1	1	X
0	1	1	0	0	X
1	0	0	0	X	1
1	0	1	1	X	0
1	1	0	1	X	0
1	1	1	1	X	0

J	C	0	1
B	A	X	X
0	0	X	X
0	1	0	X
1	1	0	X
1	0	1	X

$J = A$

K	C	0	1
B	A	X	1
0	0	X	1
0	1	X	0
1	1	X	0
1	0	X	0

$K = \bar{A}\bar{B}$

$T_B = \bar{C}\bar{B} + CBA$ (from (b))

$A^+ = \bar{C}\bar{B} + CB + \bar{B}\bar{A}$ (from (a))

12.9

12.9 (a)

$Q Q^+$	MN
00	00
	01
01	10
	11
10	10
	00
11	01
	11

Groupings: $00, 01 \rightarrow 0X$; $01, 11 \rightarrow 1X$; $10, 00 \rightarrow X0$; $11, 11 \rightarrow X1$

12.9 (b)

CBA	$C^+B^+A^+$
000	001
001	011
011	111
111	101
101	100
100	000

C^+

$B A$	C	0	1
00	0	0	0
01	0	0	1
11	1	1	1
10	X	X	X



$M_C = B$

$B A$	C	0	1
00	0	0	X
01	0	0	X
11	1	X	X
10	X	X	X

$N_C = A$

$B A$	C	0	1
00	0	X	0
01	0	X	1
11	1	X	1
10	X	X	X

B^+

$B A$	C	0	1
00	0	0	0
01	1	0	0
11	1	0	0
10	X	X	X



$M_B = C'A$

$B A$	C	0	1
00	0	0	0
01	1	1	0
11	X	X	X
10	X	X	X

$N_B = C'$

$B A$	C	0	1
00	0	X	X
01	1	X	X
11	1	1	0
10	X	X	X

A^+

$B A$	C	0	1
00	0	1	0
01	1	0	0
11	1	1	1
10	X	X	X



$M_A = C'$

$B A$	C	0	1
00	0	1	0
01	1	X	X
11	X	X	X
10	X	X	X


$N_A = C' + B$

$B A$	C	0	1
00	0	X	X
01	1	1	0
11	1	1	1
10	X	X	X

Homework 8 Solutions

Problem 3

5.20

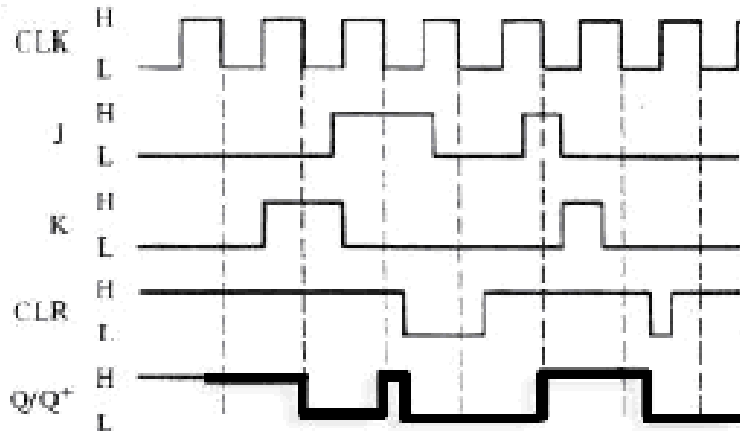


5.28

5.28 a) Truth Table:

X1	X2	Q1	Q0	Q1+	Q0+	J1	K1	J0	K0
0	0	0	0	0	1	0	X	1	X
0	0	0	1	1	0	1	X	X	1
0	0	1	0	1	1	X	0	1	X
0	0	1	1	0	0	X	1	X	1
0	1	0	0	1	1	1	X	1	X
0	1	0	1	0	0	0	X	X	1
0	1	1	0	0	1	X	1	1	X
0	1	1	1	1	0	X	0	X	1
1	0	0	0	1	0	1	X	0	X
1	0	0	1	0	0	0	X	X	1
1	0	1	0	1	1	X	0	1	X
1	0	1	1	0	1	X	1	X	0
1	1	0	0	0	1	0	X	1	X
1	1	0	1	1	1	1	X	X	0
1	1	1	0	0	0	X	1	0	X
1	1	1	1	1	0	X	0	X	1

5.28 b) Functional Block Diagram

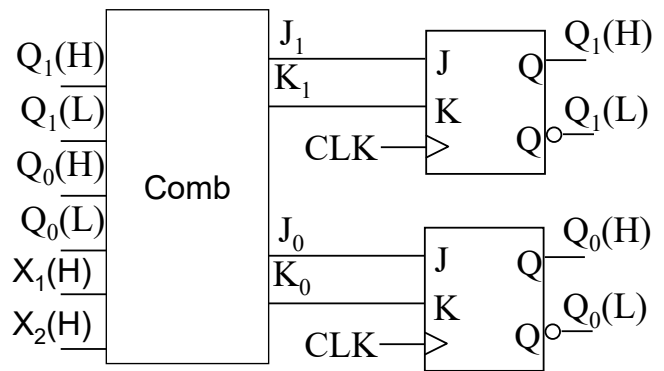

5.28 b) Logic Equations (from the Truth Table and K-maps [not shown]):

$$J1 = /Q0 /X2 X1 + /Q0 X2 /X1 + Q0 /X2 /X1 + Q0 X2 X1 = Q0 \oplus X1 \oplus X2$$

$$K1 = J1$$

$$J0 = /Q1 X2 + Q1 /X2 + /X1 = Q1 \oplus X2 + /X1$$

$$K0 = /Q1 /X2 + Q1 X2 + /X1 = Q1 \otimes X2 + /X1 = /(Q1 \oplus X2) + /X1$$