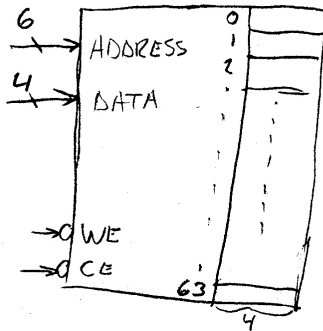


Homework 9 Solutions

Lam Book Problems
 6.17




a)

$$64 \times 4 = 2^6 \times 4$$

$$n=6$$

$$m=4$$

$$2^n - 1 = 63$$

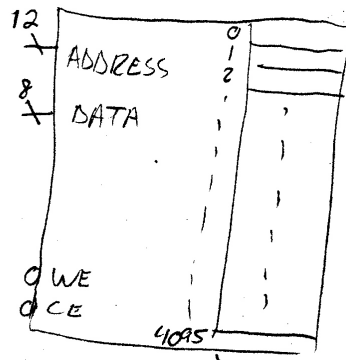


b)

$$4096 \times 8$$

$$2^{12} \times 8$$

$$n=12$$

$$m=8$$

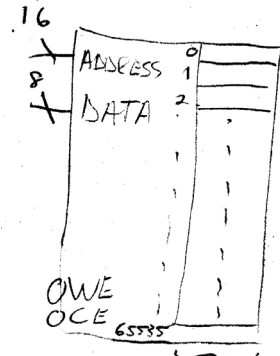

c)

$$64k \times 8$$

$$2^{16} \times 8$$

$$n=16$$

$$m=8$$

6.18)

a) 7 address 8 data

$$2^7 \cdot 8 = 128 \times 8 = 1k = 1024 \text{ bits}$$

b) 14 address 4 data


$$2^{14} \cdot 4 = 16k \times 4 = 64k = 65536 \text{ bits}$$

c) 10 address 16 data

$$2^{10} \cdot 16 = 1k \times 16 = 16k = 16384 \text{ bits}$$

Homework 9 Solutions

6.19 This is a 2k x 8 RAM.

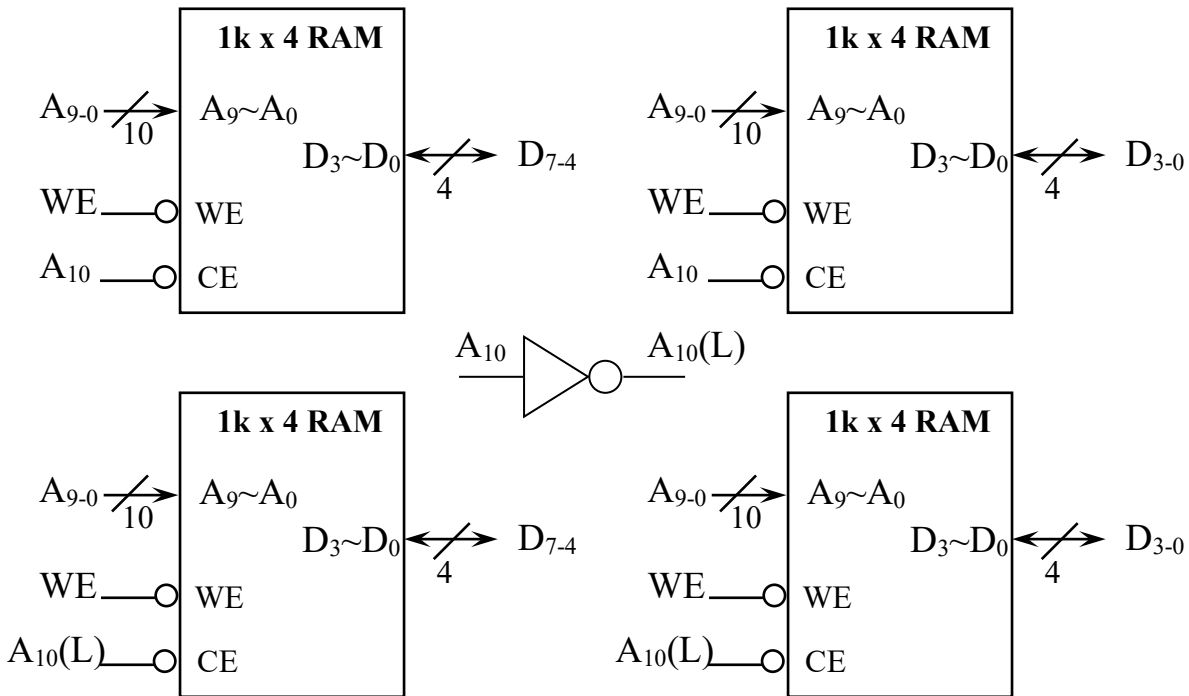

Question 1: How would you add a CE for the entire circuit?

Question 2: What if one you wanted a 2k x 8 memory module that had a 1k x 8 RAM and a 1k x 8 ROM? How would you be assured that no data collisions would occur?

Homework 9 Solutions

6.29 Construct a 128x8 ROM:

a) 8 inputs 6 outputs

no, with a 128 ROM, the max # of input lines is 7.
 This one has 8 input lines required.

b) 6 inputs, 8 outputs

yes, can handle both inputs and outputs.

6.30

6.30

