


 EEL4744 Menu

- LED Array
 - > Raster Scan output device
 - > Example device
 - > Algorithm





University of Florida, EEL 3744 – File 00
© Dr. Eric M. Schwartz

1

 EEL4744

8x8 LED Array as a Graphic Display

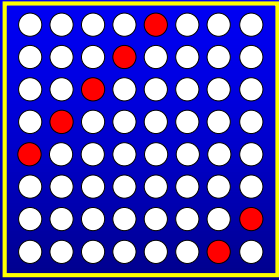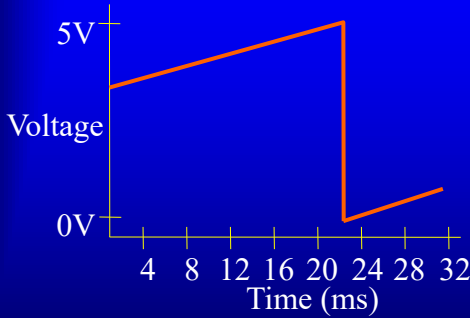

8x8 LED Array

University of Florida, EEL 3744 – File 00
© Dr. Eric M. Schwartz

2

EEL4744
8x8 LED Array as a Graphic Display

Part number is here

University of Florida, EEL 3744 – File 00
© Dr. Eric M. Schwartz

3

3

EEL4744
8x8 LED Array as a Graphic Display

OUTPUT PORT 1


33Ω

OUTPUT PORT 2

University of Florida, EEL 3744 – File 00
© Dr. Eric M. Schwartz

4

4

 **EEL4744** Raster Scan LED Array
Example: Column Displays

Step 1
Row 0: 1, 0, 0
Column 0: 0, 1, 1

Step 2
Row 0: 0, 1, 1
Column 0: 1, 0, 1


Step 3
Row 0: 1, 0, 0
Column 0: 1, 1, 0

- Only **one** column is on at a time.
- Appearance while looping from steps 1-3,
- The LEDs are dimmer here than in steps 1-3,

X X X

University of Florida, EEL 3744 – File 00
© Dr. Eric M. Schwartz

5

 **EEL4744**

The End!

University of Florida, EEL 3744 – File 00
© Dr. Eric M. Schwartz

6